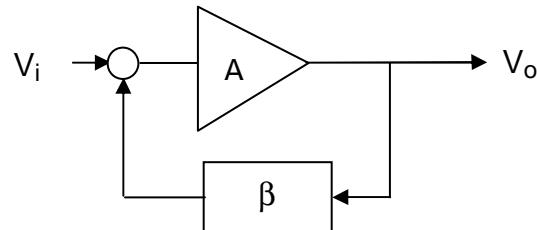


# Understanding VCO Concepts

## OSCILLATOR FUNDAMENTALS

An oscillator circuit can be modeled as shown in Figure 1 as the combination of an amplifier with gain  $A(j\omega)$  and a feedback network  $\beta(j\omega)$ , having frequency-dependent open-loop gain  $H(j\omega) = \beta A$ .

**Figure 1** An oscillator may be modeled as the combination of an amplifier and a feedback loop




$$\text{The general expression for closed-loop gain is } \frac{V_o}{V_i} = \frac{A}{1 - \beta A}$$

which states that the system will oscillate, provided  $\beta A = 1$ . At the frequency of oscillation, the total phase shift around the loop must be 360 degrees, and the magnitude of the closed loop gain must be unity. A common emitter circuit provides 180 degree phase shift. If the circuit is used with feedback from collector to base, the feedback circuit must provide additional 180 degree phase shift. If a common base circuit is used, there is no phase shift between the emitter and collector signals, and the feedback circuit must provide either 0 degree or full 360 degree phase shift.

Although the model shown in Figure 1 can be used to analyze and determine the necessary and sufficient conditions for oscillation, it is easier to use the model shown in Figure 2 where the analysis is performed in terms of a negative resistance concept. This is based on the principle that a resonator such as an inductor-capacitor tuned circuit, once excited, will oscillate continuously if no resistive element is present to dissipate the energy. It is the function of the amplifier to generate the negative resistance and maintain oscillation by supplying an amount of energy equal to that dissipated. The selection of the circuit topology is dictated by several factors:

- (a) Frequency of oscillation
- (b) Tuning range
- (c) Choice of transistor, and
- (d) Type of resonator.


**Figure 2** An oscillator may be modeled using a negative resistance concept

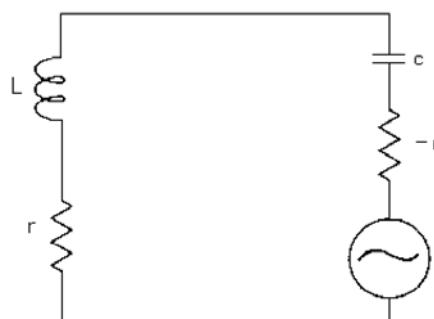

## EXAMPLES OF OSCILLATOR DESIGN


A bipolar transistor with capacitances between the base and emitter, and the emitter and ground, can be used to generate a negative resistance. Examples of these circuits are shown in Figure 3.

**Figure 3** *Forms of oscillator circuit discussed (RF equivalent)*

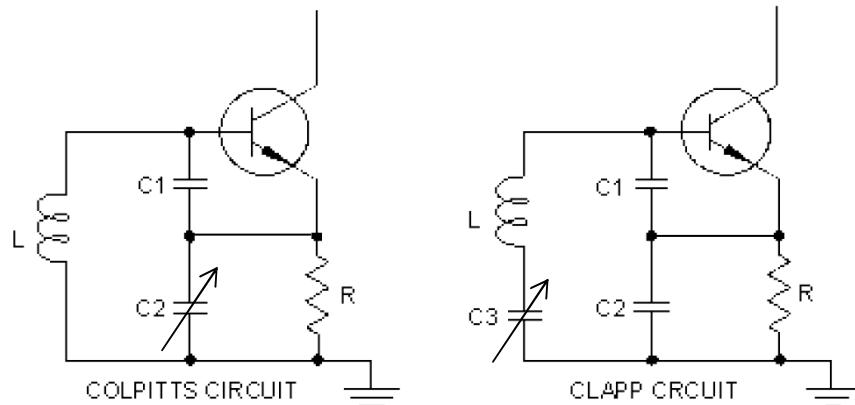

An inductive resonator may be used in any parallel resonant oscillator circuit. The signal is generated at the frequency where the inductor resonates with the load capacitance. The circuits of Figure 3 are preferred for high stability oscillator circuits because of the ease with which the resonator may be isolated from the load, which is in the collector circuit. In a VCO the variable capacitor is implemented using a varactor diode. The Clapp circuit has the advantage of better constancy of feedback because the ratio of  $C_1$  to  $C_2$  does not vary over the tuning range.

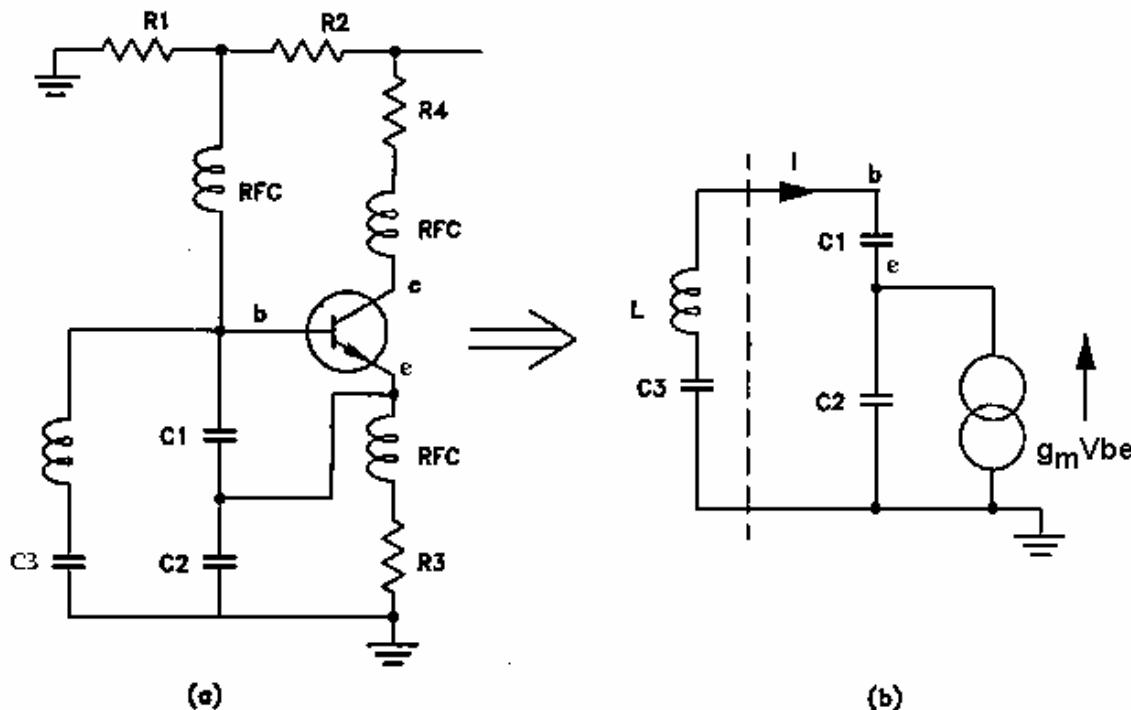Consider the more detailed schematic diagram in Figure 4a, and the equivalent circuit of its resonator in Figure 4b that is used to derive the design equations below.



**Figures 4a and 4b**

*Oscillator design evaluation for CLAPP circuit*

The input impedance looking into the part of the circuit to the right of the dashed line in Figure 4b is given by:

$$V = \frac{i}{j\omega C_1} + \frac{i + g_m V_{be}}{j\omega C_2}$$

where  $V_{be} = \frac{i}{j\omega C_1}$

$$\frac{V}{i} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} - \frac{g_m}{\omega^2 C_1 C_2}$$

The quantity  $-(g_m/\omega^2 C_1 C_2)$  is negative indicating a negative resistive component. Therefore, in order to maintain oscillation we must have


$$r < \frac{g_m}{\omega^2 C_1 C_2}$$

where  $r$  is the series resistance of the resonator. The frequency of oscillation is given by


$$(\omega^2)L = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

The ratio  $C_1/C_2$  is selected to be greater than 1 so that the circuit has sufficient loop gain for start-up condition at the lowest operating temperature. A VCO is implemented by replacing a fixed capacitor such as  $C_3$  with a varactor.

In another circuit that can generate a negative resistance, Figure 5 shows a bipolar transistor with an inductive reactance between the base and the ground. This common-base topology is preferred at higher frequencies. Adding an inductive resonator and a variable capacitor to form a tank circuit as shown in Figure 6 completes the oscillator.

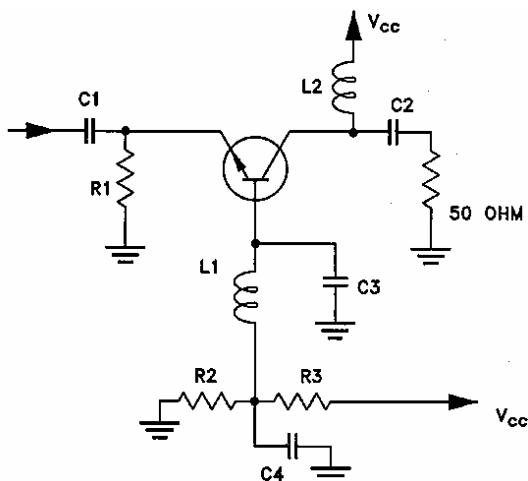

**Figure 5** Common base circuit configured for generating negative resistance

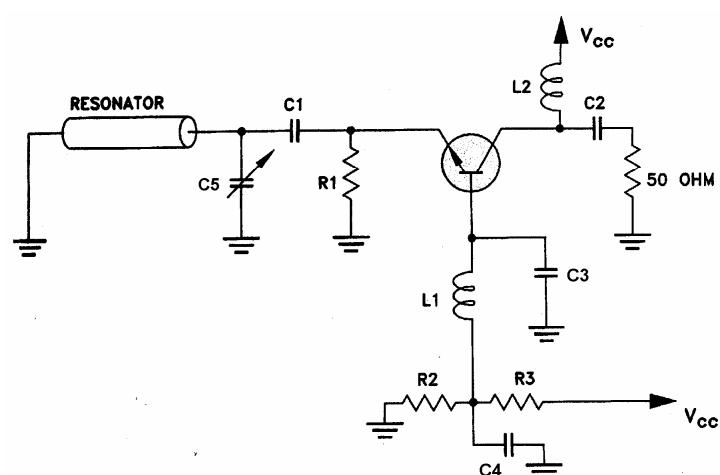

**Figure 6** Common base circuit with resonator added to form an oscillator

## TUNING SENSITIVITY CHARACTERISTICS

There are two basic types of varactors: abrupt and hyperabrupt. The abrupt tuning diodes have very high Q and will operate over a very wide tuning voltage range (0V to 60V). The abrupt tuning diode provides the best phase noise performance because of its high quality factor.

Hyperabrupt tuning diodes, having capacitance inversely proportional to the square of the voltage, will provide a much more linear tuning characteristic than the abrupt diodes. These are the best choice for wide band tuning VCOs. An octave frequency range can be covered with less than 20V tuning voltage range. Their disadvantage is that they have a much lower Q and therefore provide a phase noise characteristic higher than that provided by the abrupt diodes.

For a varactor diode, the capacitance is related to the bias voltage by the following equation:

$$C = \frac{A}{(V_R + \Phi)^n} \quad \dots \dots \dots (1)$$

where A is a constant,  $V_R$  is the applied reverse bias voltage, and  $\Phi$  is the built-in potential which is 0.7V for silicon diodes and 1.2V for gallium arsenide diodes. For the analysis that follows, we may write

$$C = \frac{A}{V^n} \quad \dots \dots \dots (2)$$

where A is the capacitance of the diode when V is one volt and n is a number between 0.3 and 0.6, but can be as high as 2 for a hyperabrupt junction. The tank circuit of a typical VCO has a parallel tuned circuit consisting of an inductance L, a fixed capacitance  $C_f$ , and a varactor diode C. The frequency of oscillation can be written as

$$\frac{1}{\omega^2} = L(C_f + AV^{-n}) \quad \dots \dots \dots (3)$$

Let  $\omega_0$  be the angular frequency of the unmodulated carrier, and let  $V_0$  and  $C_0$  be the corresponding values of V and C. Then from Equation (3) we have

$$L = \frac{1}{\omega_0^2 (C_f + C_0)} \quad \dots \dots \dots (4)$$

If  $V_0$  is modulated by a small voltage  $\Delta V$ , the carrier will be deviated by a small frequency difference  $\Delta\omega$ .

$$(\omega_0 + \Delta\omega)^{-2} = L [C_f + A(V_0 + \Delta V)^{-n}]$$

Substituting for L and rearranging, we have

$$\left(1 + \frac{\Delta\omega}{\omega_0}\right)^{-2} = \frac{C_f + C_0 \left(1 + \frac{\Delta V}{V_0}\right)^{-n}}{C_f + C_0}$$

The oscillator tuning sensitivity  $K_1$  can therefore be written as

$$K_1 = \frac{d\omega}{dV} = \frac{n\omega_0}{2V_0} \left( \frac{C_0}{C_f + C_0} \right)$$

The units of  $K_1$  are radian/second/volt. For tuning sensitivity in Hz/volt, divide the right side of the equation by  $2\pi$ .

## 射 频 和 天 线 设 计 培 训 课 程 推 荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立，致力并专注于微波、射频、天线设计研发人才的培养；我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com))，现已发展成为国内最大的微波射频和天线设计人才培养基地，成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程，广受客户好评；并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书，帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司，以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表：<http://www.edatop.com/peixun/rfe/129.html>




### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材；旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习，能够让学员完全达到和胜任一个合格的射频工程师的要求…

课程网址：<http://www.edatop.com/peixun/rfe/110.html>
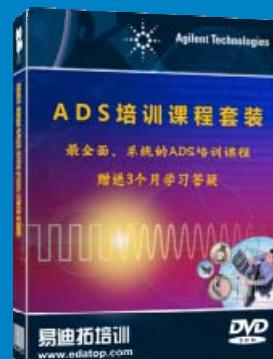
### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程，共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解，并多结合设计实例，由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS，迅速提升个人技术能力，把 ADS 真正应用到实际研发工作中去，成为 ADS 设计专家…



课程网址：<http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程，是迄今国内最全面、最专业的 HFSS 培训教程套装，可以帮助您从零开始，全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装，更可超值赠送 3 个月免费学习答疑，随时解答您学习过程中遇到的棘手问题，让您的 HFSS 学习更加轻松顺畅…

课程网址：<http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出, 是最全面、系统、专业的 CST 微波工作室培训课程套装, 所有课程都由经验丰富的专家授课, 视频教学, 可以帮助您从零开始, 全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装, 还可超值赠送 3 个月免费学习答疑…



课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书, 课程从基础讲起, 内容由浅入深, 理论介绍和实际操作讲解相结合, 全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程, 可以帮助您快速学习掌握如何使用 HFSS 设计天线, 让天线设计不再难…

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程, 培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合, 全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作, 同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习, 可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试…



详情浏览: <http://www.edatop.com/peixun/antenna/116.html>

## 我们的课程优势:

- ※ 成立于 2004 年, 10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养, 更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授, 结合实际工程案例, 直观、实用、易学

## 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>