

# Flyback Transformer Design For **TOPSwitch®** Power Supplies

## Application Note AN-17



When developing **TOPSwitch** flyback power supplies, transformer design is usually the biggest stumbling block. Flyback transformers are not designed or used like normal transformers. Energy is stored in the core. The core must be gapped. Current effectively flows in either the primary or secondary winding but never in both windings at the same time.

Why use the flyback topology? Flyback power supplies use the least number of components. At power levels below 75 watts,

total flyback component cost is lower when compared to other techniques. Between 75 and 100 Watts, increasing voltage and current stresses cause flyback component cost to increase significantly. At higher power levels, topologies with lower voltage and current stress levels (such as the forward converter) may be more cost effective even with higher component counts.

Flyback transformer design, which requires iteration through a set of design equations, is not difficult. Simple spreadsheet iteration reduces design time to under 10 minutes for a transformer

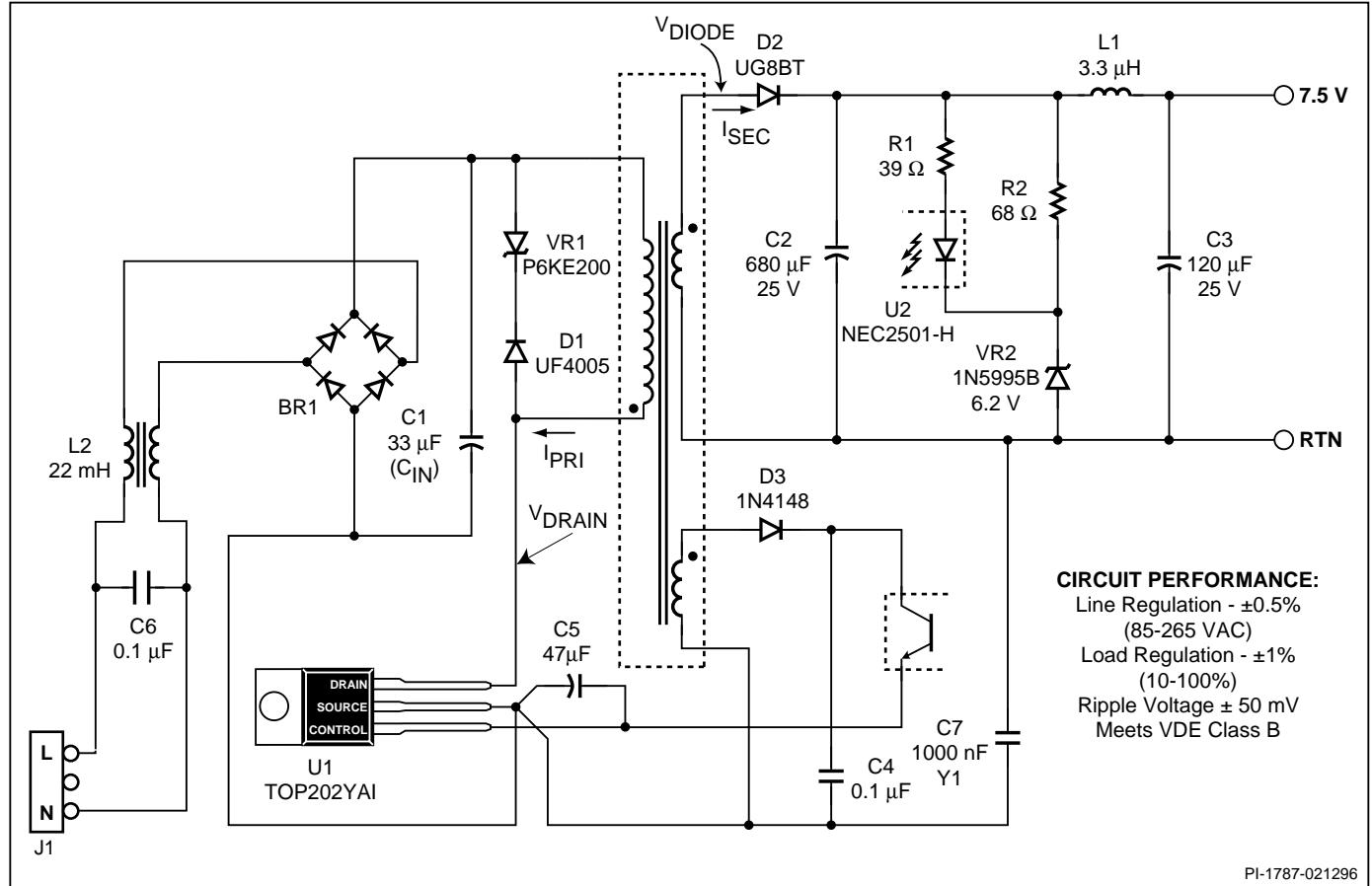


Figure 1. ST202A Power Supply Operates from Universal Input Voltage and Delivers 15 Watts.

that usually works the first time. This method, used for continuous mode as well as discontinuous mode designs, has three distinct steps:

- 1) Identify and estimate a set of independent variables (input) depending on application details, transformer core, and selected *TOPSwitch*.
- 2) Identify and calculate a set of dependent parameters (output).
- 3) Iterate specified independent variables until selected dependent parameters fall within defined limits for a practical flyback transformer.

A simple PC spreadsheet (available from Power Integrations for Excel or compatible spreadsheet programs) automates the transformer design method presented in this application note. (Note: this improved version has been completely revised and may give slightly different answers compared to earlier versions. Refer to the last page of this application note for a complete description of the changes.)

A new parameter, the ratio of primary ripple current to peak current ( $K_{RP}$ ), is introduced to describe the *TOPSwitch* drain current waveform shape and simplify subsequent calculations such as RMS current and AC flux density.

Application specific independent variables include minimum and maximum AC input voltage, line frequency, *TOPSwitch* switching frequency, output and bias voltages, output power, bridge rectifier conduction time, size of input energy storage capacitor, power supply efficiency and power loss allocation between primary and secondary circuitry. Variables depending on the transformer core and construction include effective core cross sectional area and magnetic path length, ungapped effective inductance, bobbin physical winding width, margin width (for creepage distance and safety isolation), number of primary layers, and number of secondary turns. Variables depending on *TOPSwitch* include switching frequency, reflected output voltage, ripple to peak current ratio, and *TOPSwitch* voltage drop.

For a given application and transformer core, 20 of these 23 independent variables will be calculated or estimated once and then remain fixed during iteration. Only three variables, number of secondary turns  $N_s$ , ripple to peak current ratio  $K_{RP}$ , and number of primary winding layers  $L$  will be changed during the iteration process.

Dependent parameters are divided into four groups: DC input voltage, primary current waveform shape, transformer design, and voltage stress. DC input voltage parameters are simply the minimum and maximum DC input voltage after the AC mains have been rectified and filtered. Primary current waveform

shape parameters include maximum duty cycle, average current, peak current, ripple current, and RMS current to completely define transformer primary current and determine operation in either continuous or discontinuous mode. Transformer design parameters include primary inductance, number of primary turns, number of bias winding turns, gapped effective inductance, maximum flux density, AC flux density, ungapped core relative permeability, estimated gap length, effective bobbin width, insulated primary wire diameter, insulation thickness, bare conductor cross section, primary current capacity, and secondary design parameters. Voltage stress parameters determine the maximum *TOPSwitch* off-state drain voltage and output rectifier peak inverse voltage.

Of all these dependent parameters, only three require examination and comparison within limits during iteration. Maximum flux density  $B_M$ , gap length  $L_G$ , and primary current capacity  $CMA$  are checked with each iteration until all three parameters are within specified limits. The remaining dependent parameters are either intermediate calculations or parameters used by the manufacturer for construction or the designer for specifying components.

Understanding primary and secondary current waveform shape in both continuous and discontinuous mode operation is necessary before beginning transformer design.

Figure 1 shows a typical flyback power supply using the TOP202 *TOPSwitch* from Power Integrations, Inc. *TOPSwitch* combines an integrated high voltage MOSFET switch with a complete switching power supply controller and protection circuitry in a single 3 pin TO220 package. The *TOPSwitch* power supply operates from 85 to 265 VAC and delivers 15 Watts at 7.5 Volt output. AC power is rectified and filtered by BR1 and C1 ( $C_{IN}$ ) to create the high voltage DC bus applied to the primary winding of T1. The other side of the transformer primary is driven by *TOPSwitch*. D1 and VR1 clamp voltage spikes caused by transformer leakage inductance. D2, C2, L1, and C3 rectify and filter the power secondary. *TOPSwitch* bias voltage is provided by D3 and C4 which rectify and filter the bias winding. EMI filter components L2, C6, and C7 reduce conducted emission currents. Bypass capacitor C5 filters internal *TOPSwitch* gate charge current spikes and also compensates the control loop. Regulation is achieved when the output voltage rises sufficiently above Zener diode voltage (VR2) to cause optocoupler photodiode current to flow. Optocoupler phototransistor current flows into the *TOPSwitch* control pin to directly control the duty cycle and output voltage. R1 together with series impedances of VR2 and *TOPSwitch* determine the control loop DC gain. R2 and VR2 provide a slight preload to improve regulation at light loads.

Figures 2 and 3 show typical voltage and current waveforms taken from the same power supply delivering 15 Watts from 110 VAC input voltage but with different flyback transformer



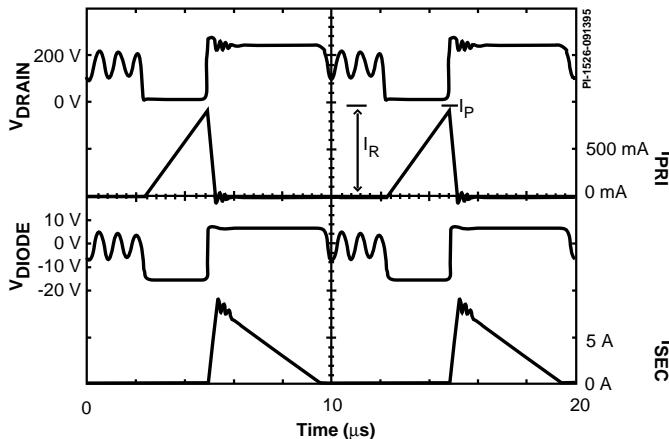


Figure 2. Voltage and Current Waveforms for Transformer Primary and Secondary in Discontinuous Mode.

primary inductance. *TOPSwitch* turns on to effectively apply the DC input voltage across the transformer winding with the “dot” side at lower potential than the “no-dot” side. Primary current  $I_{PRI}$  increases linearly with a rate of change ( $di/dt$ ) that varies directly with DC input voltage and inversely with primary inductance. Ripple current  $I_R$  is defined as the incremental linear current rise ( $di$ ) over the entire *TOPSwitch* on time ( $t_{ON}$ ). Peak primary current  $I_p$  is the final value occurring as *TOPSwitch* turns off. Energy, proportional to the square of peak current  $I_p$ , is stored by magnetic field in the transformer core as if the primary winding were a simple inductor. The secondary winding carries a reflected voltage proportional to primary voltage by turns ratio with the same “dot” polarity. While *TOPSwitch* is on, output diode D2 and bias diode D3 are reverse biased which prevents secondary current flow. When *TOPSwitch* turns off, the decreasing magnetic field induces an abrupt voltage reversal on all transformer windings such that the “dot” side is now higher potential than the “no-dot” side. Diode D2 and D3 become forward biased and secondary current rises quickly to a peak value (proportional by the inverse turns ratio to primary peak current  $I_p$ ). Primary current immediately drops to zero. *TOPSwitch* drain voltage quickly rises to a voltage equal to the sum of the DC input voltage and reflected output voltage. Secondary winding current now linearly decreases at a rate that varies directly with output voltage and inversely with secondary inductance. Duty cycle is defined as the ratio of *TOPSwitch* on time  $t_{ON}$  to switching period T. D can also be calculated from  $t_{ON}$  and switching frequency  $f_s$  as shown.

$$D = \frac{t_{ON}}{T} = t_{ON} \times f_s$$

Figure 2 shows *TOPSwitch* and output diode triangular current waveforms which define “discontinuous” mode of operation resulting from low primary inductance. The secondary current linearly decreases to zero before *TOPSwitch* turns on again.

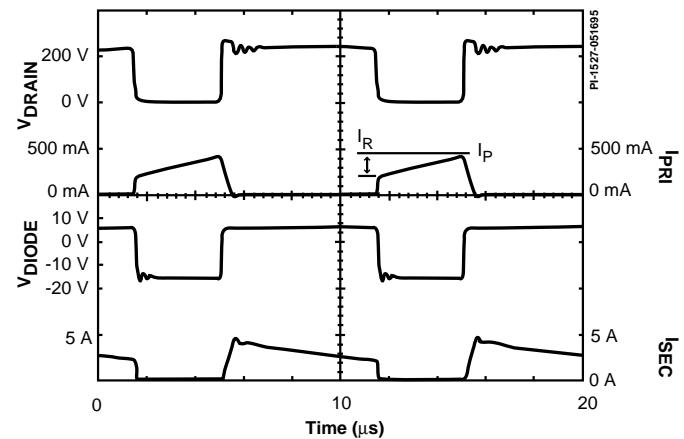


Figure 3. Voltage and Current Waveforms for Transformer Primary and Secondary in Continuous Mode.

The stored energy is completely delivered to the load. *TOPSwitch* drain voltage  $V_{DRAIN}$  relaxes and rings back towards the DC bus voltage when no current is flowing in either primary or secondary.

Figure 3 shows trapezoidal current waveforms which define “continuous” mode of operation resulting from high primary inductance. Secondary current is still flowing when *TOPSwitch* turns on at the beginning of the next cycle. The stored energy is not completely delivered to the load. Energy (due to non-zero magnetic field) remains in the core when *TOPSwitch* turns on again which causes the initial step in *TOPSwitch* current. Note that *TOPSwitch* drain voltage  $V_{DRAIN}$  stays at a high value equal to the sum of the DC input voltage and reflected output voltage until *TOPSwitch* turns on again.

Current never flows in the primary and secondary winding at the same time. Neither primary or secondary current is actually continuous. In flyback power supplies, continuous/discontinuous mode refers to magnetic field continuity in the transformer core over one complete switching cycle. (The flyback power supply is an isolated version of the simple buck-boost converter where continuous and discontinuous modes are easily defined by inductor current continuity.)

Each primary current waveform has a peak value ( $I_p$ ), a ripple current value ( $I_R$ ), an average or DC value ( $I_{AVG}$ ), and an RMS value ( $I_{RMS}$ ).  $I_p$  determines the number of primary turns and the core size necessary to limit peak flux density and must also be below *TOPSwitch* peak current limit.  $I_{AVG}$  is the average or DC primary current (as well as the power stage DC input current) which is proportional to output power.  $I_{RMS}$  causes power losses due to winding resistance and *TOPSwitch*  $R_{DS(on)}$ . The ratio ( $K_{RP}$ ) of ripple current  $I_R$  to peak current  $I_p$  defines the continuous or discontinuous waveform.  $K_{RP}$  also simplifies subsequent calculations. Transformers designed for discontinuous operation have a higher peak current and a ripple current to peak current ratio  $K_{RP}$  of one. Practical continuous designs have lower peak

currents and a ripple to peak current ratio  $K_{RP}$  of less than one but typically greater than 0.4.  $K_{RP}$  is inversely proportional to primary inductance so a continuous design with lower  $K_{RP}$  will have a higher inductance. Continuous transformer designs have a practical primary inductance upper limit approximately four times that of a discontinuous design at the same input voltage and output power due to the difference in peak currents and value of  $K_{RP}$ .

The primary current waveforms shown in Figures 2 and 3 deliver the same output power and therefore (assuming equal efficiency) must have equal  $I_{AVG}$ . The discontinuous current waveform has a higher peak value and therefore must have a higher RMS current value. Discontinuous mode requires less inductance and reduces transformer size but operates with higher losses and lower efficiency due to higher RMS currents. Continuous mode requires higher inductance and larger transformer size but offers improved efficiency and lower power losses. The trade-off between transformer size and power supply efficiency depends on the packaging and thermal environment in each application.

Some control loop comments regarding continuous mode are in order here. Most designers tend to avoid the continuous mode whenever possible because the feedback control loop is more difficult to analyze. Discontinuous mode power supplies are modeled with a single pole response and are simple to stabilize. Continuous mode offers improved efficiency, reduced losses, lower component temperatures, or higher output power but analysis is more difficult because a right half plane zero and complex pole pair all shift with duty cycle. However, stabilizing a continuous mode *TOPSwitch* power supply is quite straightforward. Adequate phase margins are achievable over all line and load combinations because the 70% maximum *TOPSwitch* duty cycle  $DC_{MAX}$  (from the data sheet) limits right half plane zero and complex pole pair migration. Phase margin is generally higher than expected once the damping effect of effective series power path resistance and output capacitor ESR is taken into account. Crossover bandwidths of 1 KHz (or wider) are easily achievable with phase margins of at least 45 degrees. Refer to AN-14 for circuit techniques to use in continuous mode designs.

Transformer core, winding, and safety issues must also be discussed before beginning design.

Transformer core and construction parameters depend on the selected core and winding techniques used in assembly. Physical height and cost are usually most important when selecting cores. This is especially true in AC mains adapter power supplies normally packaged in sealed plastic boxes. Applications allowing at least 0.75 inches of component height can use low cost EE or EI cores from Magnetics, Inc., Japanese vendors TDK and Tokin, or European vendors Philips, Siemens, and

Thomson. Applications requiring lower profile can benefit from EFD cores available from the European vendors. EER cores offer a large window area, require few turns, and have bobbins available with high pin counts for those applications requiring multiple outputs. ETD cores are useful in the higher power designs when space is not a problem. PQ cores are more expensive but take up slightly less PC board space and require less turns than E cores. Safety isolation requirements make pot cores, RM cores, and toroids generally not suitable for flyback power supplies operating from the AC mains.

Flyback transformers must provide isolation between primary and secondary in accordance with the regulatory agencies of the intended market. For example, information technology equipment must meet the requirements of IEC950 in Europe and UL1950 in the U.S. These documents specify creepage and clearance distances as well as insulation systems used in transformer construction. 5 to 6 mm creepage distance is usually sufficient between primary and secondary (check with the appropriate agency and specification). Isolation is usually specified by electric strength and is tested with a voltage of typically 3000 VAC applied for 60 seconds. Two layers of insulation (Basic and Supplementary) can be used between primary and secondary if each layer exceeds the electric strength requirement. Three layers of insulation (reinforced) can also be used if all combinations of two layers (out of total three layers) meets the electric strength requirement.

Figure 4a shows the margin winding technique used in most flyback transformers. The margin is usually constructed with layers of tape slit to the width of the desired margin and wrapped in sufficient layers to match the winding height. The margin is generally half the required primary to secondary creepage distance (2.5 mm in this example). Cores and bobbins should be selected large enough that the actual winding width is at least twice the total creepage distance to maintain transformer coupling and reduce leakage inductance. The primary is wound between the margins. To reduce the risk of interlayer voltage breakdown due to insulation abrasion, improve layer to layer insulation, and decrease capacitance, the primary layers should be separated by at least one layer of UL listed polyester film tape (3M 1298) cut to fit between the margins. Impregnation with varnish or epoxy can also improve the layer to layer insulation and electric strength but does not reduce capacitance. The bias winding may then be wound over the primary. Supplementary or reinforced insulation consisting of two or three layers of UL listed polyester film tape cut to the full width of the bobbin may then be wrapped over the primary and bias windings. Margins are again wound. The secondary winding is wound between the margins. Another two or three layers of tape is added to secure the windings. Insulation sleeving may be needed over the leads of one or all windings to meet creepage distance requirements at lead exits. Nylon or



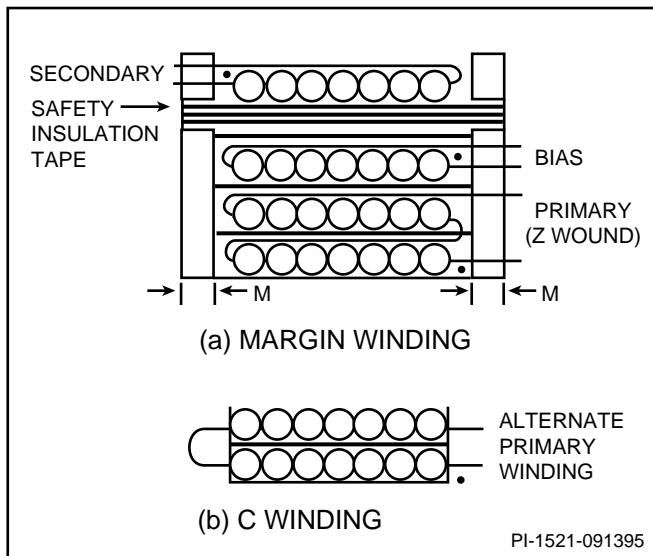


Figure 4. Margin Wound Transformer.

Teflon sleeving with a minimum wall thickness of 0.41 mm should be used to meet the safety agency requirements. Consider the core as isolated dead metal (which means the core is conductive but not part of any circuit and safely insulated from the consumer). The sum of distance from primary winding (or lead exits) to the core added to the distance from the core to the secondary (or lead exits) must be equal to or greater than the required creepage distance.

Both Z winding (Figure 4a) and C winding (Figure 4b) techniques for multiple primary layers are shown. Note that the “dot” side which connects to *TOPSwitch* is buried under the second layer for self shielding to reduce EMI (common mode conducted emission currents). Z winding decreases transformer capacitance, decreases AC *TOPSwitch* losses, and improves efficiency but is more difficult and costly to wind. The C winding is easier and lower cost to wind but at the expense of higher loss and lower efficiency.

Figure 5 shows a new technique using double or triple insulated wire on the secondary to eliminate the need for margins (insulated wire sources can be found at the end of this application note). In double insulated wire, each layer is usually capable of meeting the electric strength requirement of the safety agency. In triple insulated wire, all three combinations of two layers taken together must usually meet the electric strength requirement. Special care is necessary to prevent insulation damage during winding and soldering. This technique reduces transformer size and eliminates the labor cost of adding margins but has higher material cost and may increase winding costs. The primary winding is wound over the full width of the bobbin flange. The bias winding can be wound if desired over the primary. One layer of tape is usually necessary between primary or bias and secondary to prevent abrasion of the

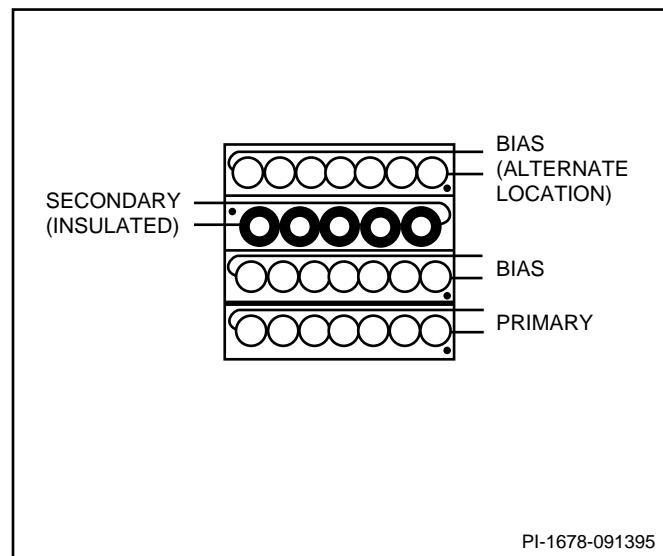


Figure 5. Triple Insulated Wire Wound Transformer.

insulated wire. The double or triple insulated wire is then wound. Another layer of tape is added to secure insulated winding.

Figure 5 also shows an alternate position for the bias winding wound directly over the secondary to improve coupling to the secondary winding and reduce leakage inductance (to improve load regulation in bias winding feedback circuits). Note that because the bias winding is a primary circuit, margin wound transformers must have another layer of supplementary or reinforced insulation between the secondary and alternate bias winding.

Refer to AN-18 for more information regarding transformer construction guidelines.

Flyback transformer design now begins by specifying the three groups of independent variables shown in the spreadsheet (Figure 6).

#### Application Variables:

Output power  $P_o$ , output voltage  $V_o$ , AC mains frequency  $f_L$ , *TOPSwitch* switching frequency  $f_s$  (100KHz), minimum ( $V_{ACMIN}$ ), and maximum ( $V_{ACMAX}$ ) AC mains voltage come directly from the application.

For efficiency ( $\eta$ ), start with an estimate based on measurements in similar power supplies (or use a value of 0.8 if data is unavailable).

Efficiency can be used to calculate total power loss  $P_L$  in the power supply as shown below. Some power losses occurring in series primary components such as the bridge rectifier, common

A	B	C	D	E	F
<b>1</b>					
<b>2</b>					
<b>3</b> <b>ENTER APPLICATION VARIABLES</b>					
3 VACMIN	85	Volts	Volts	Volts	Minimum AC Input Voltage
4 VACMAX	265	Volts	Volts	Volts	Maximum AC Input Voltage
5 fL	60	Hertz	Hertz	Hertz	AC Mains Frequency
6 fS	100000	Hertz	Hertz	Hertz	TOPSwitch Switching Frequency
7 VO	7.5	Volts	Volts	Volts	Output Voltage
8 PO	15	Watts	Watts	Watts	Output Power
9 n	0.8				Efficiency Estimate
10 Z	0.5				Loss Allocation Factor
11 VB	10.4	Volts	Volts	Volts	Bias Voltage
12 tC	3.2	mSeconds	mSeconds	mSeconds	Bridge Rectifier Conduction Time Estimate
13 CIN	33	uFarads	uFarads	uFarads	Input Filter Capacitor
14					
<b>15</b> <b>ENTER TOPSWITCH VARIABLES</b>					
16 VOR	85	Volts	Volts	Volts	Reflected Output Voltage
17 VDS	10	Volts	Volts	Volts	TOPSwitch on-state Drain to Source Voltage
18 VD	0.4	Volts	Volts	Volts	Output Winding Diode Forward Voltage Drop
19 VDB	0.7	Volts	Volts	Volts	Bias Winding Diode Forward Voltage Drop
20 KRP	0.92				Ripple to Peak Current Ratio (0.4 < KRP < 1.0)
21					
<b>22</b> <b>ENTER TRANSFORMER CORE/CONSTRUCTION VARIABLES</b>					
23	EE22-Z				Core Type
24 AE	0.41	cm^2	cm^2	cm^2	Core Effective Cross Sectional Area
25 LE	3.96	cm	cm	cm	Core Effective Path Length
26 AL	2400	nH/T^2	nH/T^2	nH/T^2	Ungapped Core Effective Inductance
27 BW	8.43	mm	mm	mm	Bobbin Physical Winding Width
28 M	0	mm	mm	mm	Safety Margin Width (Half the Primary to Secondary Creepage Distance)
29 L	2				Number of Primary Layers
30 NS	5				Number of Secondary Turns
31					
<b>32</b> <b>DC INPUT VOLTAGE PARAMETERS</b>					
33 VMIN		93 Volts	93 Volts	93 Volts	Minimum DC Input Voltage
34 VMAX		375 Volts	375 Volts	375 Volts	Maximum DC Input Voltage
35					
<b>36</b> <b>CURRENT WAVEFORM SHAPE PARAMETERS</b>					
37 DMAX		0.51	0.51	0.51	Duty Cycle at Minimum DC Input Voltage (VMIN)
38 IAVG		0.20 Amps	0.20 Amps	0.20 Amps	Average Primary Current
39 IP		0.74 Amps	0.74 Amps	0.74 Amps	Peak Primary Current
40 IR		0.68 Amps	0.68 Amps	0.68 Amps	Primary Ripple Current
41 IRMS		0.32 Amps	0.32 Amps	0.32 Amps	Primary RMS Current
42					
<b>43</b> <b>TRANSFORMER PRIMARY DESIGN PARAMETERS</b>					
44 LP		623 uHenries	623 uHenries	623 uHenries	Primary Inductance
45 NP		54	54	54	Primary Winding Number of Turns
46 NB		7	7	7	Bias Winding Number of Turns
47 ALG	215	nH/T^2	nH/T^2	nH/T^2	Gapped Core Effective Inductance
48 BM		2085 Gauss	2085 Gauss	2085 Gauss	Maximum Flux Density (2000 < BM < 3000)
49 BAC	959	Gauss	Gauss	Gauss	AC Flux Density for Core Loss Curves (0.5 X Peak to Peak)
50 ur	1845				Relative Permeability of Ungapped Core
51 LG		0.22 mm	0.22 mm	0.22 mm	Gap Length (Lg >> 0.051 mm)
52 BWE	16.86	mm	mm	mm	Effective Bobbin Width
53 OD		0.31 mm	0.31 mm	0.31 mm	Maximum Primary Wire Diameter including insulation
54 INS	0.05	mm	mm	mm	Estimated Total Insulation Thickness (= 2 * film thickness)
55 DIA		0.26 mm	0.26 mm	0.26 mm	Bare conductor diameter
56 AWG		30 AWG	30 AWG	30 AWG	Primary Wire Gauge (Rounded to next smaller standard AWG value)
57 CM	102	Cmils	Cmils	Cmils	Bare conductor effective area in circular mils
58 CMA		321 Cmils/Amp	321 Cmils/Amp	321 Cmils/Amp	Primary Winding Current Capacity (200 < CMA < 500)
59					
<b>60</b> <b>TRANSFORMER SECONDARY DESIGN PARAMETERS</b>					
61 ISP		7.95 Amps	7.95 Amps	7.95 Amps	Peak Secondary Current
62 ISRMS		3.36 Amps	3.36 Amps	3.36 Amps	Secondary RMS Current
63 IO		2.00 Amps	2.00 Amps	2.00 Amps	Power Supply Output Current
64 IRIPPLE		2.70 Amps	2.70 Amps	2.70 Amps	Output Capacitor RMS Ripple Current
65					
66 CMS	1079	Cmils	Cmils	Cmils	Secondary Bare Conductor minimum circular mils
67 AWGS		19 AWG	19 AWG	19 AWG	Secondary Wire Gauge (Rounded up to next larger standard AWG value)
68 DIAS		0.91 mm	0.91 mm	0.91 mm	Secondary Minimum Bare Conductor Diameter
69 ODS		1.69 mm	1.69 mm	1.69 mm	Secondary Maximum Insulated Wire Outside Diameter
70 INSS	0.39	mm	mm	mm	Maximum Secondary Insulation Wall Thickness
71					
<b>72</b> <b>VOLTAGE STRESS PARAMETERS</b>					
73 VDRAIN		573 Volts	573 Volts	573 Volts	Maximum Drain Voltage Estimate (Includes Effect of Leakage Inductance)
74 PIVS		42 Volts	42 Volts	42 Volts	Output Rectifier Maximum Peak Inverse Voltage
75 PIVB		59 Volts	59 Volts	59 Volts	Bias Rectifier Maximum Peak Inverse Voltage
76					
<b>77</b> <b>ADDITIONAL OUTPUTS</b>					
78 VX	12	Volts	Volts	Volts	Auxiliary Output Voltage
79 VDX	0.7	Volts	Volts	Volts	Auxiliary Diode Forward Voltage Drop
80 NX		8.04	8.04	8.04	Auxiliary Number of Turns
81 PIVX		68 Volts	68 Volts	68 Volts	Auxiliary Rectifier Maximum Peak Inverse Voltage
82					

Figure 6. Spreadsheet for ST202A Flyback Transformer Design.



mode choke, and *TOPSwitch* are not associated directly with energy stored in the flyback transformer core. The remaining power losses, occurring in the output rectifier and clamp Zener diode when energy is released from the flyback transformer, are now defined as secondary loss  $P_{LS}$ . Loss Allocation Factor Z, defined below as the ratio of secondary loss  $P_{LS}$  to total loss  $P_L$ , is a scaling factor which distributes the losses between primary and secondary. Loss allocation factor Z is typically between 0.4 and 0.6 which means that secondary loss  $P_{LS}$  is usually 40% to 60% of total power supply loss  $P_L$ .

$$P_L = P_O \times \left( \frac{1 - \eta}{\eta} \right)$$

$$Z = \frac{P_{LS}}{P_L}$$

Bias voltage  $V_B$  is determined by the feedback control circuit and is usually between 10 volts and 30 volts (see AN-16).

For bridge rectifier conduction time  $t_c$ , 3 milliSeconds is typical (measure on a similar power supply or set equal to zero for a conservative first design).

For input filter capacitor  $C_{IN}$ , start with a standard value in microFarads between two and three times the output power in Watts (appropriate for universal or 115 VAC input). For example: 30 $\mu$ F to 45 $\mu$ F is a suitable capacitance range for a 15 Watt supply. 33 $\mu$ F is the lowest standard value within the range.

### ***TOPSwitch* Variables:**

Reflected output voltage  $V_{OR}$  appears across the transformer primary when *TOPSwitch* is off and current is flowing through the secondary and output rectifier diode. Transformers optimized for *TOPSwitch* applications should be designed with a maximum reflected voltage  $V_{OR}$  of 60V or less for the TOP1XX series and 135V or less for the TOP2XX series. For more information, refer to AN-16.

$V_{DS}$  is the on-state *TOPSwitch* voltage from the data sheet (typically 10 volts) at the specified value for peak *TOPSwitch* drain current  $I_P$ .

Output rectifier forward voltage drop  $V_D$  depends on output voltage. For lower output voltages (typically 8 Volts and below) a Schottky diode is commonly used and  $V_D$  is typically 0.4 Volts. In some cases, a Schottky diode can be used for output voltages as high as 12V depending on input voltage range and transformer turns ratio. For higher output voltage, an ultrafast recovery PN junction diode is

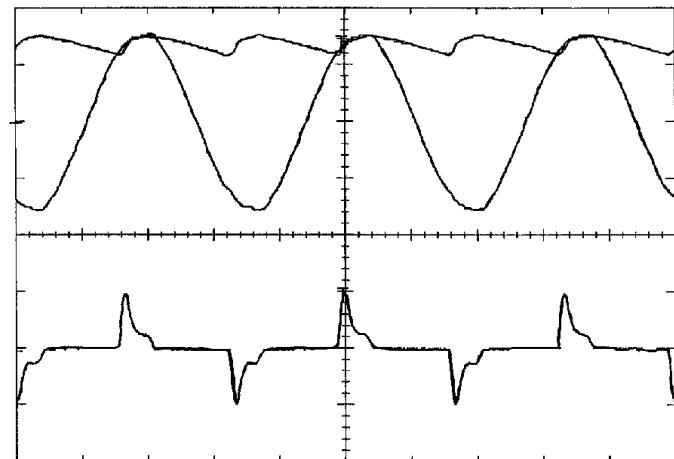


Figure 7. Bridge AC Current, AC Voltage, and DC Voltage Waveforms.

normally used and  $V_D$  is typically 0.7 Volts.

Bias winding diode forward voltage drop ( $V_{DB}$ ) is also typically 0.7 Volts

Ripple current to peak current ratio  $K_{RP}$  determines how far into the continuous mode a flyback transformer will operate. Continuous mode transformers optimized for *TOPSwitch* applications operating from 100/115 VAC or universal input voltage should have a minimum  $K_{RP}$  of 0.4. Applications operating from 230 VAC input voltage should have a minimum  $K_{RP}$  of 0.6. Discontinuous mode transformers optimized for *TOPSwitch* applications always have a  $K_{RP}$  equal to 1.0.

$$K_{RP} = \frac{I_R}{I_P}$$

### **Transformer Core/Construction Variables:**

The following effective parameters are specified by the core and bobbin manufacturer in data sheets: cross sectional area  $A_e$  ( $\text{cm}^2$ ), path length  $L_e$  (cm), ungapped inductance  $A_L$  (specified in either  $\text{mH}/(1000 \text{ turns})^2$  or  $\text{nH}/\text{T}^2$ ), and physical bobbin winding width  $B_w$  (mm).

Margin width  $M$ , determined by insulation methods and regulatory requirements discussed above, is usually between 2.5 to 3.0 mm for margin wound or set to zero for insulated wire wound transformers.

For number of layers  $L$ , one or two layers of primary winding are normally used. Higher number of layers increase cost, increase capacitance, reduce coupling, and increase leakage inductance.

Number of secondary turns  $N_s$  is a key iteration variable. One turn per Volt of output voltage is a good value to begin with for  $N_s$  (for example: start with 5 turns for a +5V output).

The four groups of dependent parameters can now be calculated.

### DC Input Voltage Parameters:

Minimum DC input voltage  $V_{MIN}$  depends on the AC input voltage, bridge rectifier, and energy storage capacitor. Figure 7 shows how  $C_{IN}$  charges to the peak of the AC input voltage during a short conduction time  $t_c$ . Because of full wave rectification,  $C_{IN}$  has a ripple voltage at twice line frequency.  $C_{IN}$  must supply the entire average primary current during the discharge time between the peaks of the AC input voltage. Minimum DC voltage  $V_{MIN}$  can be found from the following equation where  $P_o$  is the power supply output power,  $\eta$  is an estimate of efficiency,  $f_L$  is line voltage frequency,  $V_{ACMIN}$  is the minimum AC mains voltage,  $C_{IN}$  is the value of the filter capacitor, and  $t_c$  is an estimate for conduction time. As an example, for 60 Hz, 85 VAC input voltage, efficiency of 0.8, 15 Watt output power, 33  $\mu$ F input filter capacitance, and estimated conduction time of 3.2 mS,  $V_{MIN}$  is 93 Volts DC.

$$V_{MIN} = \sqrt{\left(2 \times V_{ACMIN}^2\right) - \left(\frac{2 \times P_o \times \left(\frac{1}{2 \times f_L} - t_c\right)}{\eta \times C_{IN}}\right)}$$

$$= \sqrt{\left(2 \times 85^2\right) - \left(\frac{2 \times 15 \times \left(\frac{1}{2 \times 60} - 3.2mS\right)}{0.8 \times 33\mu F}\right)} = 93V$$

Maximum DC input voltage  $V_{MAX}$  is simply the peak value of the highest AC input voltage ( $V_{ACMAX}$ ) expected in the application. Operation from 265 VAC input results in a maximum DC bus voltage  $V_{MAX}$  of 375 Volts DC.

$$V_{MAX} = V_{ACMAX} \times \sqrt{2} = 265 \times \sqrt{2} = 375V$$

### Current Waveform Shape Parameters:

$D_{MAX}$  is the actual duty cycle occurring when the *TOPSwitch* power supply delivers maximum output power from minimum input voltage.  $D_{MAX}$  has an upper limit equal to the minimum value of the *TOPSwitch* Data Sheet parameter  $DC_{MAX}$  (64%).  $D_{MAX}$  is calculated from reflected voltage  $V_{OR}$ , minimum DC input voltage  $V_{MIN}$ , and *TOPSwitch* on-state Drain to Source

voltage  $V_{DS}$ :

$$D_{MAX} = \frac{V_{OR}}{V_{OR} + (V_{MIN} - V_{DS})}$$

Average current  $I_{AVG}$  is calculated from minimum DC input voltage  $V_{MIN}$ , output power  $P_o$ , and efficiency  $\eta$ :

$$I_{AVG} = \frac{P_o}{\eta \times V_{MIN}}$$

Peak primary current  $I_p$  is calculated from average current  $I_{AVG}$ , ripple to peak current ratio  $K_{RP}$ , and maximum duty cycle  $D_{MAX}$ :

$$I_p = I_{AVG} \times \frac{2}{(2 - K_{RP}) \times D_{MAX}}$$

Ripple current  $I_R$  is calculated from average current  $I_{AVG}$ , peak primary current  $I_p$ , and maximum duty cycle  $D_{MAX}$ :

$$I_R = 2 \times (I_p - \frac{I_{AVG}}{D_{MAX}})$$

RMS current  $I_{RMS}$  is calculated from maximum duty cycle  $D_{MAX}$ , peak primary current  $I_p$ , and ripple to peak ratio  $K_{RP}$ .  $I_{RMS}$  can also be calculated directly from  $D_{MAX}$ ,  $I_p$ , and ripple current  $I_R$ .

$$I_{RMS} = I_p \times \sqrt{D_{MAX} \times \left(\frac{K_{RP}^2}{3} - K_{RP} + 1\right)}$$

$$= \sqrt{D_{MAX} \times \left(I_p^2 - (I_p \times I_R) + \frac{I_R^2}{3}\right)}$$

### Transformer Design Parameters:

Primary inductance  $L_p$  (in  $\mu$ H) is determined by the flyback transformer energy equation defined below. The flyback transformer stores energy proportional to the square of primary current. When *TOPSwitch* is on, primary current linearly ramps up over a current range, defined earlier as ripple current  $I_R$ , and increases the energy stored in the flyback transformer core. When *TOPSwitch* turns off, the stored energy increment associated with ripple current  $I_R$  is delivered to the load and secondary losses (rectifier and clamp). Inductance  $L_p$  can now be calculated from output power  $P_o$ , efficiency  $\eta$ , loss allocation factor  $Z$ , peak current  $I_p$ , switching frequency  $f_s$ , and ripple current to peak current ratio  $K_{RP}$  (which determines  $I_R$ ).

$$L_p = 10^6 \times \frac{P_o \times \left( \frac{(Z \times (1 - \eta)) + \eta}{\eta} \right)}{f_s \times I_p^2 \times K_{RP} \times \left( 1 - \frac{K_{RP}}{2} \right)}$$

Primary inductance  $L_p$  (in  $\mu\text{H}$ ) can also be determined from a simple function of ripple current  $I_r$ , effective primary voltage ( $V_{MIN} - V_{DS}$ ), maximum duty cycle  $D_{MAX}$ , and switching frequency  $f_s$  as shown below but the resulting value for primary inductance may be slightly different due to the selected value for loss allocation factor  $Z$  and *TOPSwitch* on-state Drain to Source voltage  $V_{DS}$ . The energy equation given above is preferred for selecting the value of inductance  $L_p$  while the ripple current equation given below is best for verifying the  $L_p$  value using in-circuit measurements.

$$L_{p(MEASURED)} = 10^6 \times \frac{(V_{MIN} - V_{DS}) \times D_{MAX}}{I_r \times f_s}$$

Number of primary turns  $N_p$  depends on number of secondary turns  $N_s$ , output voltage  $V_o$ , diode forward voltage drop  $V_d$ , effective primary voltage ( $V_{MIN} - V_{DS}$ ), and maximum duty cycle  $D_{MAX}$ :

$$N_p = N_s \times \frac{V_{MIN} - V_{DS}}{V_o + V_d} \times \frac{D_{MAX}}{1 - D_{MAX}}$$

The number of bias winding turns  $N_B$  is calculated from the output voltage  $V_o$ , output diode voltage  $V_d$ , secondary number of turns  $N_s$ , target bias voltage  $V_B$ , and bias diode voltage  $V_{BD}$ :

$$N_B = \frac{V_B + V_{BD}}{V_o + V_d} \times N_s$$

$A_{LG}$  is the effective inductance for the gapped core in  $\text{nH/T}^2$ . Some core vendors offer standard gapped core sets with specified  $A_{LG}$ . The transformer manufacturer either procures the gapped core for the given  $A_{LG}$  value or grinds the gap to meet the inductance specification in the finished transformer.  $A_{LG}$  is also used to simplify subsequent calculations.  $A_{LG}$  is calculated from primary inductance  $L_p$  (in  $\mu\text{H}$ ) and number of primary turns  $N_p$ . Note that  $A_{LG}$  is specified in  $\text{nH}/(\text{turn})^2$ .

$$A_{LG} = 1000 \times \frac{L_p}{N_p^2}$$

Maximum flux density  $B_M$  is a dependent iteration variable to be manipulated between the limits of 2000 and 3000 Gauss by varying number of secondary turns  $N_s$  which directly varies number of primary turns  $N_p$  as previously shown.  $B_M$  is calculated from peak current  $I_p$ , number of primary turns  $N_p$ , effective gapped inductance  $A_{LG}$ , and effective core cross sectional area  $A_e$ .  $B_M$  can also be calculated from effective primary voltage ( $V_{MIN} - V_{DS}$ ), output voltage  $V_o$ , output diode voltage  $V_d$ , and maximum duty cycle  $D_{MAX}$ :

$$B_M = \frac{N_p \times I_p \times A_{LG}}{10 \times A_e}$$

$$= N_s \times \frac{I_p \times A_{LG}}{10 \times A_e} \times \frac{V_{MIN} - V_{DS}}{V_o + V_d} \times \frac{D_{MAX}}{1 - D_{MAX}}$$

$B_{AC}$  is the AC flux density component. The equation gives peak AC flux density (rather than peak to peak) to use with core loss curves provided by the core vendor.  $B_{AC}$  can be calculated from maximum flux density  $B_M$  and ripple to peak current ratio  $K_{RP}$ .  $B_{AC}$  can also be calculated from effective primary voltage ( $V_{MIN} - V_{DS}$ ), duty cycle, frequency, effective core cross sectional area, and number of primary turns  $N_p$ :

$$B_{AC} = \frac{B_M \times K_{RP}}{2} = \frac{(V_{MIN} - V_{DS}) \times D_{MAX} \times 10^8}{2 \times f_s \times A_e \times N_p}$$

Relative permeability  $\mu_r$  of the ungapped core must be calculated to estimate the gap length  $L_g$ .  $\mu_r$  is found from core parameters  $A_e$  ( $\text{cm}^2$ ),  $L_e$  (cm), and ungapped effective inductance  $A_L$ :

$$\mu_r = \frac{A_L \times L_e}{0.4 \times \pi \times A_e \times 10}$$

Gap length  $L_g$  is the air gap ground into the center leg of the transformer core. Grinding tolerances and  $A_{LG}$  accuracy place a minimum limit of 0.051 mm on  $L_g$ .  $L_g$  (in mm) is calculated from number of primary turns  $N_p$ , core effective cross sectional area  $A_e$ , primary inductance  $L_p$  (in  $\mu\text{H}$ ), core effective path length  $L_e$ , and relative permeability  $\mu_r$ :

$$L_g = \left( \frac{0.4 \times \pi \times N_p^2 \times A_e}{L_p \times 100} - \frac{L_e}{\mu_r} \right) \times 10$$

Effective bobbin width  $BW_E$  takes into account physical bobbin width  $BW$ , margins  $M$ , and number of layers  $L$ :

$$BW_E = L \times (BW - (2 \times M))$$

Primary insulated wire diameter OD in mm is found from effective bobbin width  $BW_E$  and number of primary turns  $N_p$ :

$$OD = \frac{BW_E}{N_p}$$

The bias winding is usually wound with the same wire diameter as the primary to reduce the number of different wire gauges necessary for production.

Actual magnet wire outside diameter OD is slightly larger than the diameter DIA of the bare copper conductor. Insulation thickness varies inversely with bare copper conductor American Wire Gauge (AWG) size which means that smaller diameter conductors have thinner insulation thickness. Data from several different manufacturers were tabulated to generate an empirical expression for total insulation thickness INS (in mm) as a function of heavy insulated magnet wire outside diameter (in mm).

$$INS = (0.0594 \times \text{LOG}(OD)) + 0.0834$$

$$DIA = OD - INS$$

Another empirical equation determines the AWG for magnet wire with a given bare conductor diameter DIA. Integer AWG values are the standard sizes of available wire so the calculated AWG value should always be rounded up to the next integer or standard value (the next smaller standard conductor diameter) before proceeding with the current capacity or CMA calculation.

$$AWG = 9.97 \times (1.8277 - (2 \times \text{LOG}(DIA)))$$

Magnet wire for transformer winding usually has the cross sectional area specified in circular mils. A circular mil is the cross sectional area of a wire with a diameter of 1 mil (or 0.0254 mm). The effective cross sectional area in circular mils (CM) of a standard AWG size bare conductor wire is found from the following simple expression.

$$CM = 2^{\left(\frac{50-AWG}{3}\right)}$$

“Circular mils per Amp” or CMA is a convenient way to specify winding current capacity. CMA, which is the inverse of current density, is simply the ratio of cross sectional area in circular mils to the RMS value of primary current. CMA should be between 200 and 500 and is calculated from cross sectional wire area in CM and RMS primary current  $I_{RMS}$ .

$$CMA = \frac{CM}{I_{RMS}}$$

This completes all calculations necessary for the primary winding. Secondary peak current, RMS current, average output current, output capacitor ripple current, and secondary minimum and maximum conductor diameter must also be calculated.

Peak secondary current  $I_{SP}$  is a simple function of peak primary current  $I_p$ , primary turns  $N_p$ , and secondary turns  $N_s$ .

$$I_{SP} = I_p \times \frac{N_p}{N_s}$$

Secondary RMS current  $I_{SRMS}$  is found from maximum duty cycle  $D_{MAX}$ , secondary peak current  $I_{SP}$ , and ripple to peak current ratio  $K_{RP}$  ( $K_{RP}$  is identical for primary and secondary).

$$I_{SRMS} = I_{SP} \times \sqrt{(1 - D_{MAX}) \times \left(\frac{K_{RP}^2}{3} - K_{RP} + 1\right)}$$

Output current  $I_o$  is simply the ratio of output power  $P_o$  to output Voltage  $V_o$ :

$$I_o = \frac{P_o}{V_o}$$

Output capacitor ripple current  $I_{RIPPLE}$  is not a true transformer parameter but is needed for capacitor selection and easy to calculate from other transformer parameters.  $I_{RIPPLE}$  is found from secondary RMS current  $I_{SRMS}$  and output current  $I_o$ .

$$I_{RIPPLE} = \sqrt{I_{SRMS}^2 - I_o^2}$$

Minimum secondary bare conductor diameter  $DIA_s$  (in mm) based on previously calculated current capacity CMA and secondary RMS current must be determined.

From the primary CMA and secondary RMS current  $I_{SRMS}$ , the minimum secondary bare conductor  $CM_s$  is calculated.

$$CM_s = CMA \times I_{SRMS}$$

Minimum secondary AWG<sub>s</sub> is then calculated from another empirical equation. Secondary calculated wire gauge AWG<sub>s</sub> is always rounded down to the next integer value which selects the next larger standard wire size.

$$AWG_S = 9.97 \times (5.017 - LOG(CM_S))$$

(Secondary conductors larger than 26 AWG should not be used due to skin effects. Refer to AN-18 for suggestions on parallel conductor techniques.)

Bare conductor diameter (in mm) is now determined.

$$DIA_S = \sqrt{\frac{4 \times 2^{\left(\frac{50-AWG_S}{3}\right)}}{1.27 \times \pi}} \times \frac{25.4}{1000}$$

The maximum wire outside diameter  $OD_S$  (in mm) for a single layer based on number of secondary turns and bobbin width must also be calculated:

$$OD_S = \frac{BW - (2 \times M)}{N_S}$$

Secondary wire insulation thickness can now be calculated from the bare conductor outside diameter (determined by CMA) and the insulated wire outside diameter (determined by number of turns and effective bobbin width). Note that secondary insulation thickness  $INS_S$  (in mm) is the insulation wall thickness rather than the total insulation thickness used in the primary winding calculation.

$$INS_S = \frac{OD_S - DIA_S}{2}$$

Obviously, if insulation thickness  $INS_S$  is not a positive number, another transformer design iteration is necessary with either more secondary layers, a smaller number of secondary turns, or a transformer core with a wider bobbin.

For insulated wire secondaries,  $INS_S$  must be equal to or greater than insulation thickness of the selected wire.

Parallel combinations of wire with half the diameter may be easier to wind and terminate but the effective secondary CMA will be half the value of the single winding.

### Voltage Stress Parameters:

Maximum drain voltage is the sum of maximum DC input voltage  $V_{MAX}$ , an estimated drain clamp voltage term based on  $V_{OR}$ , and an estimated voltage term related to typical blocking diode forward recovery. Refer to AN-16 for more detail.

$$V_{DRAIN} = V_{MAX} + (1.4 \times 1.5 \times V_{OR}) + 20V$$

Maximum peak inverse voltage  $PIV_S$  for the output rectifier is determined by transformer primary and secondary number of turns  $N_P$  and  $N_S$ , maximum DC input voltage  $V_{MAX}$ , and output voltage  $V_o$ .

$$PIV_S = V_o + (V_{MAX} \times \frac{N_S}{N_P})$$

Maximum peak inverse voltage  $PIV_B$  for the bias rectifier is determined from a similar equation using number of bias turns  $N_B$ .

$$PIV_B = V_B + (V_{MAX} \times \frac{N_B}{N_P})$$

Additional or auxiliary output winding number of turns  $N_X$  and rectifier diode peak inverse voltage  $PIV_X$  can be determined from the desired value for auxiliary output voltage  $V_X$ , auxiliary rectifier diode forward voltage drop  $V_{DX}$ , output voltage  $V_o$ , output rectifier diode forward voltage drop  $V_D$ , and number of secondary turns  $N_S$ .

$$N_X = \frac{V_X + V_{DX}}{V_o + V_D} \times N_S$$

$$PIV_X = V_X + (V_{MAX} \times \frac{N_X}{N_P})$$

Iteration can now be used to reach a final and acceptable solution for the flyback transformer design.

Iterate number of secondary turns  $N_S$  or primary ripple to peak current ratio  $K_{RP}$  until maximum flux density  $B_M$  is between indicated limits and check that gap length  $L_g$  is higher than indicated minimum value.  $B_M$  will decrease and  $L_g$  will increase as  $N_S$  or  $K_{RP}$  is increased.

Examine primary current capacity in Circular Mils per Amp (CMA). If CMA is below the specified lower limit of 200, consider increasing number of primary layers from one to two or use the next larger core size and perform new iteration. If CMA is greater than 500, consider using the next smaller core size. (CMA greater than 500 simply means that the wire diameter is oversized for the expected RMS current).

The transformer design is now complete. The transformer



manufacturer needs the following information:

Core part number and gapped effective inductance  $A_{LG}$   
 Bobbin part number  
 Wire gauge and insulation style on all windings  
 Safety or Electric strength and Creepage distance  
 specifications  
 Primary Inductance  $L_p$   
 Number of turns ( $N_p$ ,  $N_s$ ,  $N_b$ , etc.) for each winding  
 Bobbin pin connections  
 Winding layer placement and winding instructions  
 Temperature class of operation (class A is 105 °C, class B  
 is 130 °C, etc.)

### Spreadsheet Improvements

The order of the spreadsheet has been changed to simplify the iteration process. Reflected voltage  $V_{OR}$  and ripple to peak current ratio  $K_{RP}$  are now independent variables which make peak current  $I_p$  and duty cycle  $D_{MAX}$  dependent variables. Loss allocation factor  $Z$  is introduced to distinguish between power losses occurring before energy is stored in the transformer (primary losses) and power losses occurring after energy is released from the transformer (secondary losses). Primary inductance  $L_p$  is now calculated from output power  $P_o$ ,  $K_{RP}$ , efficiency  $\eta$ , and loss allocation factor  $Z$ . The spreadsheet now takes into account primary magnet wire insulation thickness as well as the discrete steps of standard AWG wire sizes. Metric dimensions are used throughout (with the exception of Circular mils for wire cross sectional area). Drain Voltage  $V_{DRAIN}$  now includes an estimate for the effect of leakage inductance induced voltage spikes on typical primary clamp circuits.

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others.

PI Logo and **TOPSwitch** are registered trademarks of Power Integrations, Inc.  
 ©Copyright 1994, Power Integrations, Inc. 477 N. Mathilda Avenue, Sunnyvale, CA 94086

### References

Bisci, J., Part IV: Magnet Wire: Selection Determines Performance, PCIM, October 1994, pp. 37.

Leman, B., Finding the Keys to Flyback Power Supplies Produces Efficient Design, EDN, April 13, 1995, pp. 101-113.

McLyman, C., Transformer and Inductor Design Handbook, Marcel Dekker, Inc. 1978

### Insulated Wire Sources

Rubudue Wire Company  
 5150 E. LaPalma Ave, Suite 108  
 Anaheim Hills, CA 92807 USA  
 (714) 693-5512  
 (714) 693-5515 FAX

Furukawa Electric America, Inc.  
 200 Westpark Dr., Suite 190  
 Peachtree City, GA 30269 USA  
 (770) 487-1234  
 (770) 487-9910 FAX

The Furukawa Electric Co., Ltd.  
 6-1, Marunouchi 2-chome,  
 Chiyoda-ku, Tokyo 100, Japan  
 81-3-3286-3226  
 81-3-3286-3747 FAX

### WORLD HEADQUARTERS

Power Integrations, Inc.  
 477 N. Mathilda Avenue  
 Sunnyvale, CA 94086  
 USA  
 Main: 408•523•9200  
 Customer Service:  
 Phone: 408•523•9265  
 Fax: 408•523•9365

### AMERICAS

For Your Nearest Sales/Rep Office  
 Please Contact Customer Service  
 Phone: 408•523•9265  
 Fax: 408•523•9365

### EUROPE & AFRICA

Power Integrations (Europe) Ltd.  
 Mountbatten House  
 Fairacres  
 Windsor SL4 4LE  
 United Kingdom  
 Phone: 44•(0)•1753•622•208  
 Fax: 44•(0)•1753•622•209

### JAPAN

Power Integrations, Inc.  
 Keihin-Tatemono 1st Bldg.  
 12-20 Shin-Yokohama 2-Chome.Kohoku-ku  
 Yokohama-shi, Kanagawa 222  
 Japan  
 Phone: 81•(0)•45•471•1021  
 Fax: 81•(0)•45•471•3717

### ASIA & OCEANIA

For Your Nearest Sales/Rep Office  
 Please Contact Customer Service  
 Phone: 408•523•9265  
 Fax: 408•523•9365

### APPLICATIONS HOTLINE

World Wide 408•523•9260

### APPLICATIONS FAX

Americas	408•523•9361
Europe/Africa	44•(0)•1753•622•209
Japan	81•(0)•45•471•3717
Asia/Oceania	408•523•9364

## 射 频 和 天 线 设 计 培 训 课 程 推 荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立，致力并专注于微波、射频、天线设计研发人才的培养；我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com))，现已发展成为国内最大的微波射频和天线设计人才培养基地，成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程，广受客户好评；并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书，帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司，以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表：<http://www.edatop.com/peixun/rfe/129.html>




### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材；旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习，能够让学员完全达到和胜任一个合格的射频工程师的要求…

课程网址：<http://www.edatop.com/peixun/rfe/110.html>
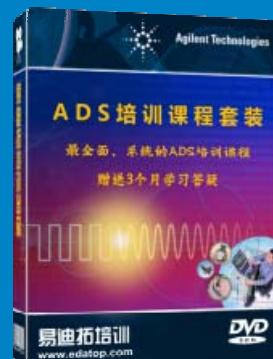
### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程，共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解，并多结合设计实例，由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS，迅速提升个人技术能力，把 ADS 真正应用到实际研发工作中去，成为 ADS 设计专家…



课程网址：<http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程，是迄今国内最全面、最专业的 HFSS 培训教程套装，可以帮助您从零开始，全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装，更可超值赠送 3 个月免费学习答疑，随时解答您学习过程中遇到的棘手问题，让您的 HFSS 学习更加轻松顺畅…

课程网址：<http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出, 是最全面、系统、专业的 CST 微波工作室培训课程套装, 所有课程都由经验丰富的专家授课, 视频教学, 可以帮助您从零开始, 全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装, 还可超值赠送 3 个月免费学习答疑…



课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书, 课程从基础讲起, 内容由浅入深, 理论介绍和实际操作讲解相结合, 全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程, 可以帮助您快速学习掌握如何使用 HFSS 设计天线, 让天线设计不再难…

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程, 培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合, 全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作, 同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习, 可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试…



详情浏览: <http://www.edatop.com/peixun/antenna/116.html>

## 我们的课程优势:

- ※ 成立于 2004 年, 10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养, 更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授, 结合实际工程案例, 直观、实用、易学

## 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>