


## Measurement and Control of RF Power (Part I)

By Eamon Nash

Applications Engineer, Analog Devices, Inc.

### Introduction

Fig. 1. shows a typical modern communications signal chain. The signal to be transmitted is generated at baseband by a digital-to-analog converter (DAC.) This signal is then mixed up to an intermediate frequency (IF) where it is filtered before being mixed up to the final radio frequency (RF.) On the receive side the inverse transformation takes place. The received signal is amplified, mixed down to IF and filtered before being mixed down to baseband where it is digitized.

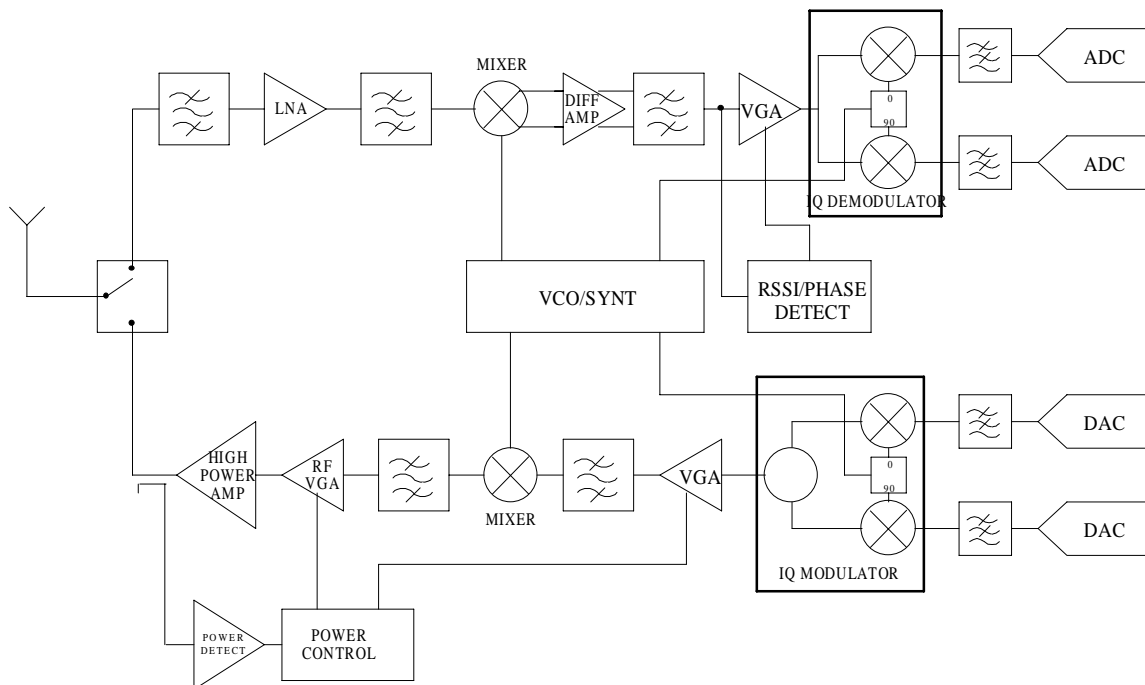

**Fig. 1: A Modern RF Signal Chain**

While signal chains such as these come in all shapes and sizes, there is a universal need in communications applications for measurement and control of signal power. On the transmit side we must ensure that the power amplifier (PA) is meeting regulatory emissions requirements. We must also ensure that the PA is not transmitting above some power level that will cause it damage by overheating.

On the receive side, the input signal level will generally vary over some dynamic range. This may be due to weather conditions or to the source of the received signal moving away from the receiver (e.g. a mobile handset being operated in a fast car.) In general, we

want to present a constant signal level to the analog-to-digital converter (ADC) as this will maximize the signal-to-noise ratio (SNR.) To do this receive signal chains typically use one or more variable gain amplifiers (VGAs) which are controlled by power measurement devices which complete the automatic gain control (AGC) loop. Note that while transmit power control can happen either at RF or IF, receive-side signal processing generally is done at IF.

In both cases, the precision of the signal strength measurement may be critical. For example, consider a base station which transmits an average power of +50 dBm (100 W.) If the detector which regulates the transmitted power from the base station has an unpredictable error over temperature of  $\pm 3$  dB, it is possible that the base station may at some point be directed to transmit 53 dBm (200 W.) This is clearly unacceptable as it would add excessive cost to the additional thermal dimensioning of the unit.

On the receive side, an imprecise measurement circuit will result in poor leveling of the signal that is presented to the ADC. This will either overdrive the ADC (input signal too large) or waste valuable dynamic range (input signal too small.)

This series deals with many of the issues associated with measuring and controlling RF power levels. Various power measurement techniques such as diode, thermal, rms-to-dc and log amps will be examined. Issues such as response time, dynamic range, resolution, varying crest factor, temperature stability, size and cost will also be examined.

### **Power**

Power in Watts can be expressed in a number of ways, i.e.

$$\text{Power} = V^2/R = VI = I^2R,$$

where V is the rms voltage, I is the rms current and R is the resistance in which the power is dissipated. Since most communications systems have constant load and source impedances, usually  $50 \Omega$ , it follows that we only need to know the rms voltage to calculate the power. As a result, many practical power measurement circuits rely on measuring rms voltage.

### **Converting between dBm, dBmV, W, rms and peak-to-peak voltage**

Signal levels in wired communications applications are usually specified in dBm. However for those "power" detectors which are voltage responding, we really should specify the output voltage with respect to its input *voltage*. This can be quite confusing for people who live in a dB world. The matter is further complicated by the changing response of many detectors in the presence of a changing peak-to-average ratio on the input signal.

The dBm unit is defined as the power level in dB referenced to 1 mW, i.e.

$$\text{Power(dBm)} = 10\log_{10}(\text{Power}/0.001 \text{ W})$$

where the power is specified in watts.

Since power in watts is equal to the rms voltage squared, divided by impedance, we can also write this as


$$\text{Power(dBm)} = 10\log_{10}((V_{\text{rms}}^2/R)/1 \text{ mW})$$

It follows that 0 dBm is equal to 1 mW, +10 dBm is equal to 10 mW, +30 dBm is equal to 1 W, etc. Because impedance is a component of this equation, we should generally specify line impedance when talking about dBm levels (e.g. 20 dBm: Re 50 Ω.)

The dBV unit is defined as the voltage level, in dB, referenced to 1 Vrms, i.e.

$$\text{Voltage(dBV)} = 20\log_{10}(V_{\text{rms}}/1 \text{ V})$$

Therefore, 0 dBV is equal to 1 Vrms. Fig. 2 shows how rms volts, peak-to-peak volts, dBV, dBm and mW relate to each other. This is however only valid for a load impedance of 50 Ω and a crest factor of 1.4142 (i.e. a sine wave where  $V_{\text{rms}} = V_{\text{peak-peak}}/2/1.4142$ .) Note that in a 50 Ω system, there is a constant offset of 13 dB between dBV and dBm (dBm = dBV + 13.)

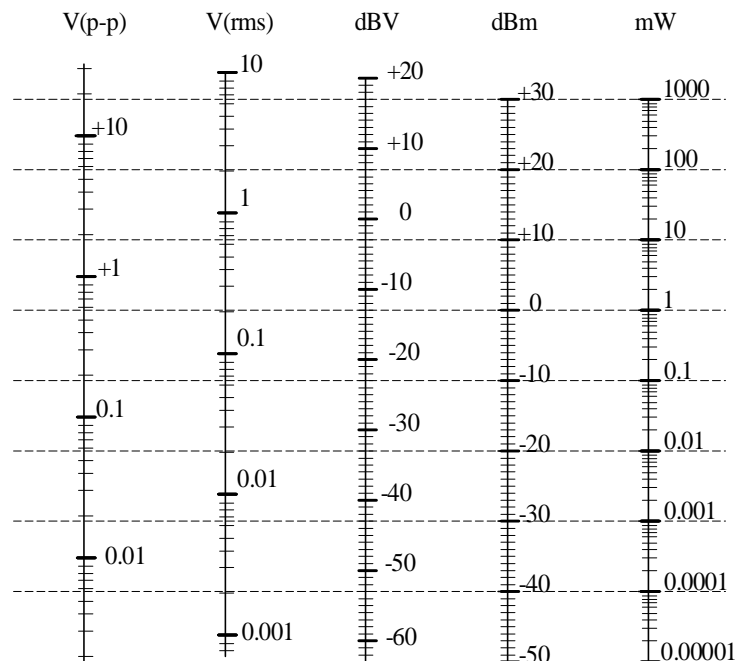

**Fig. 2: Converting between Power and Voltage**

### Definition of RMS<sup>1</sup>

RMS (or root-mean-square) is a fundamental measurement of the magnitude of an ac signal. Its definition can be both practical and mathematical. Defined practically: The rms value assigned to an ac signal is the amount of dc required to produce an equivalent amount of heat in the same load. For example, an ac signal of 1 V<sub>rms</sub> will produce the same amount of heat in a resistor as a 1 V<sub>dc</sub> signal. Defined mathematically, the rms value of a voltage is,

$$E_{\text{rms}} = \sqrt{\text{AVG}(V^2)}$$

This involves squaring the signal, taking the average, and obtaining the square root. The averaging time must be sufficiently long to allow filtering at the lowest frequencies of operation desired.

### Definition of Crest Factor

The crest factor of a waveform is the ratio of its peak value to its rms value. Signals such as amplitude-symmetrical square waves, or dc levels, have a crest factor of one. Other waveforms, more complex in nature, have higher crest factors. A sine wave has a crest factor of  $\sqrt{2}$  (i.e. 1.4142.) So a sine wave with an rms level of 1 V has a peak-to-peak amplitude of 2.8284 V.)

### Signal Magnitude Measurement Techniques

#### I Diode Detection

Fig. 3 shows the schematic of a popular diode detection circuit. This is a simple half-wave rectifier with output filtering. A 68  $\Omega$  resistor at the input creates a nominal 50  $\Omega$  input match.

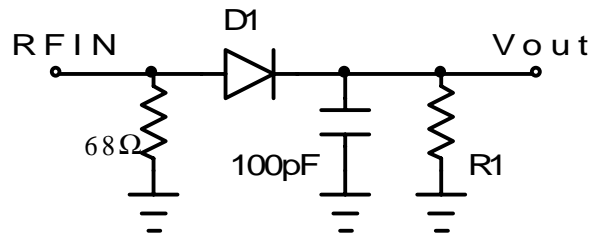
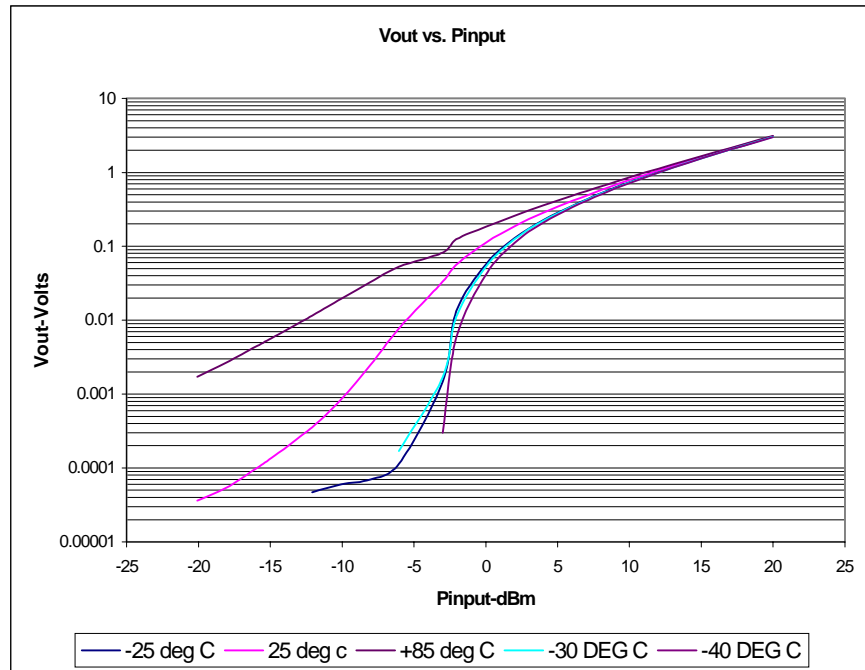


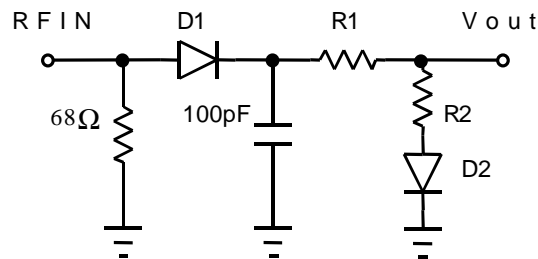
Fig. 3: A Simple Diode Detector

Fig. 4 shows the output voltage as a function of input signal in dBm.

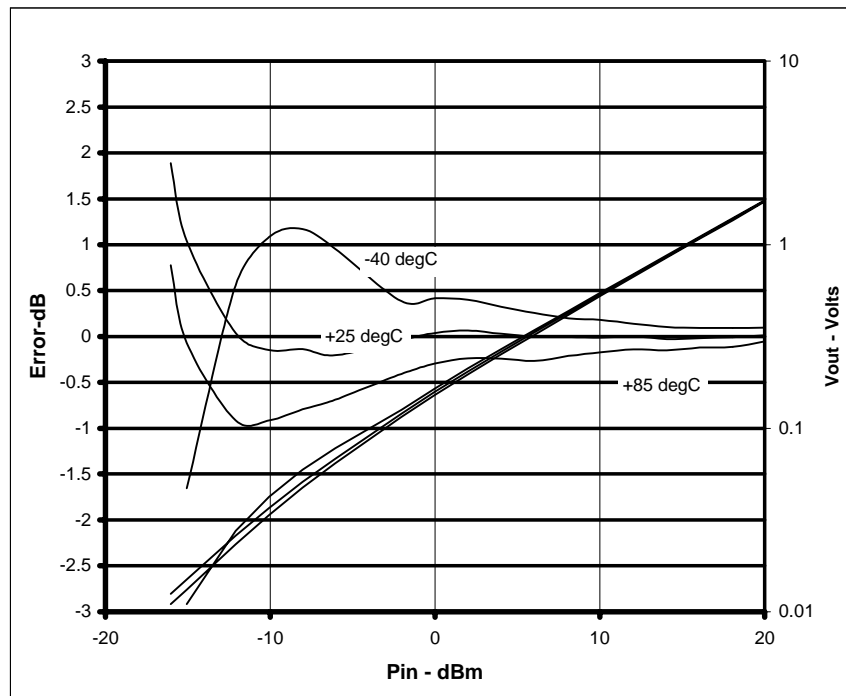


**Fig. 4: Vout Vs. Pin for a simple diode detector circuit**

While the transfer function of this circuit at 25°C is reasonably linear, performance degrades significantly at low input levels and over temperature. Fig. 5 shows a modified diode detector circuit which incorporates some temperature compensation. In this circuit the temperature dependence of the diode voltage is compensated by a second diode. So as the voltage drop across D1 increases with temperature, an identical voltage is maintained across D2. This keeps the voltage at the center of the resistor divider, which is used as an output, constant.



**Fig. 5: A Temperature-Compensated Diode Detector**



**Fig. 6: Vout and Error Vs. Pin for a Temperature-Compensated Diode Detector**

Fig. 6 shows the transfer function of this temperature-compensated circuit. To take a closer look at the improved linearity and temperature stability linear regression can calculate the best straight-line fit for these points; that is, an equation with the form,

$$V_{out} = \text{Slope} \times V_{in} + \text{Intercept}$$


Note that in order to make this calculation, it is necessary to convert power numbers in dBm to voltage (a voltage in/voltage out transfer function gives a nominally linear relationship.) Using this ideal straight line we can plot the linearity of the response over its dynamic range. In practical applications we would like to calibrate the circuit at room temperature but not over temperature. Therefore we calculate the error over temperature with respect to the best straight line, measured at room temperature. This gives us a good measure of the system-level precision of this solution.

Fig. 6 shows that the temperature-compensated diode detector has good temperature stability at high power levels but still becomes less temperature stable and less linear at low input levels. It is important to note that the circuit's output cannot be loaded with any significant resistance. At low temperatures, this circuit has an extremely high output impedance. In fact driving anything less than a FET buffer amplifier will result in the temperature-compensating algorithm failing, giving performance similar to that in Fig. 4.

Diode detector circuits do not measure true rms signal strength, with the output voltage from these detectors changing as a function of input-signal crest factor, even as the input rms signal strength stays constant (higher crest factor gives lower output voltage.) However, in a system where the signals have a constant crest factor this may not matter as long as the detector has been correctly calibrated. So if a radio link, for example, uses just one modulation scheme (e.g. QPSK), accurate power measurements can be made. However in systems with varying crest factors, such as CDMA or WCDMA, true rms measurements become difficult. One solution to this problem is to use different look-up tables based upon the call loading in the base station (it is the call loading in a particular channel that alters the crest factor.) This, however, requires calibration of the base station for every call loading scenario. The problem gets even worse in multi-carrier systems where the crest factor of multiple carriers is changing independent of one another.

## II Thermal Detection<sup>2</sup>

Thermal detection essentially involves the practical implementation of the classic definition of rms that we previously looked at. This is the simplest true rms measurement technique in theory; yet in practice it is difficult and expensive to implement. It involves comparing the heating value of an unknown ac signal to the heating value of a known calibrated dc reference voltage (see Fig. 7.) When the calibrated voltage reference is adjusted to null the temperature difference between the reference resistor (R2) and the signal resistor (R1), the power dissipated in these two matched resistors will be equal. Therefore, by the basic definition of rms, the value of the dc reference voltage will equal the rms value of the unknown signal voltage.

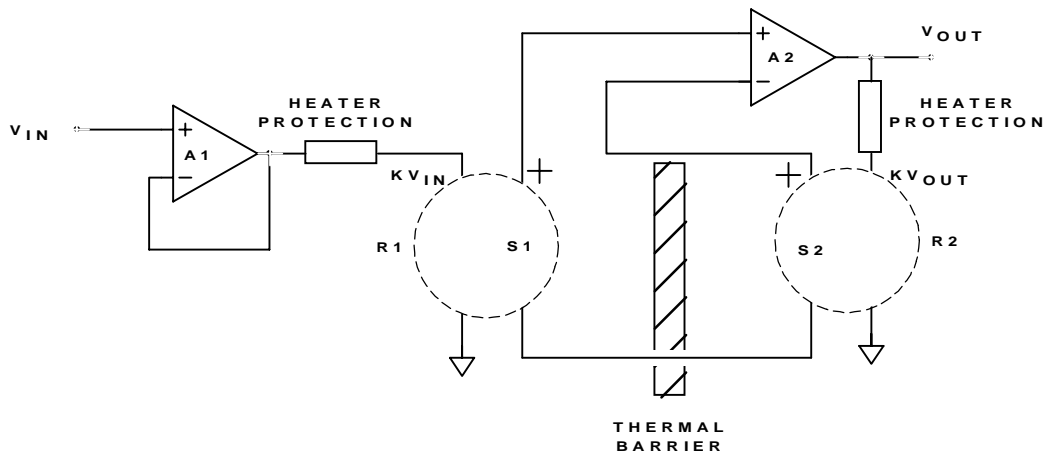

**Fig. 7: Thermal Detection**

Each thermal unit contains a stable, low-TC resistor (R1,R2) which is in thermal contact with a linear temperature-to-voltage converter (S1,S2) an example of which would be a thermocouple. The output voltage of S1/S2 varies in proportion to the mean square of  $V_{in}$ ; the first order temperature/voltage ratio will vary as  $K V_{in}/R1$ .

The circuit of Fig. 7 typically has very low error (approximately 0.1%) as well as wide bandwidth. However, the fixed time constant of the thermal unit (R1S1, R2S2) limits the low frequency effectiveness of this rms computational scheme.

In addition to this basic type, there are also variable gain thermal converters available which can overcome the dynamic range limitations of fixed-gain converters at the expense of increased complexity and cost.

[Part II of this series will introduce log amps and detail how they can be used in control loops.]

### **References**

1. RMS to DC Conversion Application Guide. Available from Analog Devices, p1
2. RMS to DC Conversion Application Guide. Available from Analog Devices, p2

### **Biography**

Eamon Nash is an Applications Engineer at Analog Devices. He has worked at Analog Devices for 10 years, first as a Field Applications Engineer, based in Germany, covering mixed signal and DSP products, then as a Product-Line Applications Engineer at ADI's Advanced Linear Products Group, specializing in building-block components for instrumentation and telecommunications applications. He earned a Bachelor of Engineering degree (BEng) in Electronics from University of Limerick, Ireland. He can be contacted at 781-937-1239 ([eamon.nash@analog.com](mailto:eamon.nash@analog.com))

*Analog Devices, Inc., 804 Woburn Street, Wilmington, MA 01887.*  
<http://www.analog.com>



## 射频和天线设计培训课程推荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com)),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



### 我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

### 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>