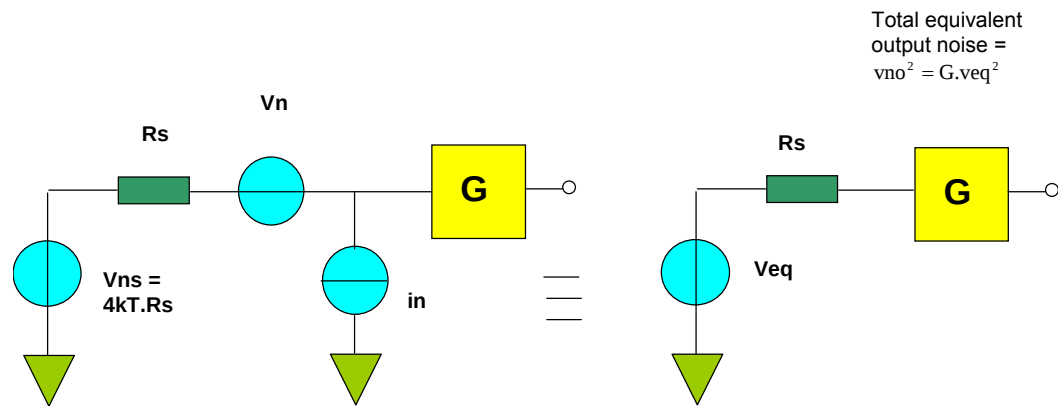


Noise Matching

From the noise tutorial the equivalent noise at the input of the device was given by:



Total equivalent input noise voltage =

$$v_{eq}^2 = v_{ns}^2 + v_n^2 + i_n^2 R_s^2 \quad \text{where } v_{ns}^2 = 4kTRs$$

and noise factor F

$$F = \frac{\text{Total equivalent input noise power}}{\text{Input noise power due to the source only}} \approx \frac{v_{eq}^2}{v_{ns}^2} = \frac{1 + v_n^2 + i_n^2 R_s^2}{v_{ns}^2}$$

Ideally $F = 1$


To minimise the noise factor, set $dF/dR_s = 0$

$$F = \frac{1 + v_n^2 + i_n^2 R_s^2}{v_{ns}^2} \quad \text{differentiate w.r.t to } R_s = \frac{i_n^2 R_s}{v_{ns}^2} = 0$$

$$\text{Rearrange to get } R_s = \frac{v_{ns}^2}{i_n^2}$$

Usually R_s is given and v_n^2 and i_n^2 are optimised for best noise. Sometimes we must find a suitable value for R_s .

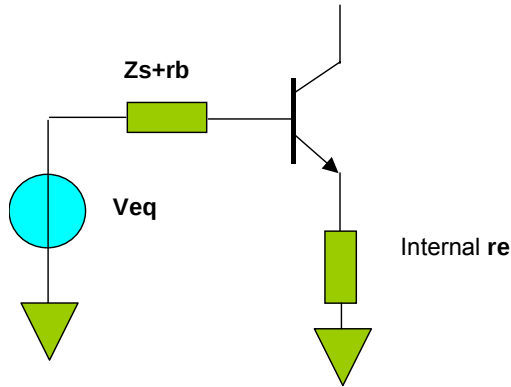CE stage + series source impedance (Broadband)



The equivalent noise voltage (V_{eq}) is given by:-

$$V_{eq}^2 = 4kT\Delta f \left[\text{Re}(Z_s) + r_b + \frac{r_e}{2} + \frac{|r_b + Z_s|^2}{2\beta \cdot r_e} \left(1 + \frac{f_L}{f} \right) \right] \quad \text{Where } \text{Re}(Z_s) \text{ is the real part of } Z_s = R_s$$

Where $V_n^2 = 4kT \left(r_b + \frac{r_e}{2} \right)$ and $I_n^2 = \frac{2kT}{\beta \cdot r_e} \left(1 + \frac{f_L}{f} \right)$

If we assume that Z_s is resistive and ignore the flicker noise contribution the above equation simplifies to:-

$$V_{eq}^2 = 4kT\Delta f \left[R_s + r_b + \frac{r_e}{2} + \frac{|r_b + R_s|^2}{2\beta \cdot r_e} \right] \quad \text{differentiate w.r.t } r_e = 4kT\Delta f \left[1 - \frac{|r_b + R_s|^2}{2\beta \cdot r_e^2} \right] = 0$$

Therefore, $r_{e(opt)} = \frac{r_b + R_s}{\sqrt{\beta}}$

$$v_{eq}^2_{(min)} = 4kT\Delta f [R_s + r_b + r_{e(opt)}] = 4kT\Delta f (R_s + r_b) \left(1 + \frac{1}{\sqrt{\beta}} \right)$$

$$v_{ns}^2 = 4kT \cdot R_s$$

Therefore $F_{min} = \frac{v_{eq}^2}{v_{ns}^2} = \frac{4kT\Delta f [R_s + r_b + r_{e(opt)}]}{4kT \cdot R_s} = \frac{1[R_s + r_b + r_{e(opt)}]}{R_s} = 1 + \frac{r_b + r_{e(opt)}}{R_s}$



$$F = 1 + \frac{r_b + r_{e(opt)}}{R_s} = 1 + \frac{r_b + \frac{r_b + R_s}{\sqrt{\beta}}}{R_s} = 1 + \frac{r_b}{R_s} + \frac{1}{R_s} \left(\frac{r_b}{\sqrt{\beta}} + \frac{R_s}{\sqrt{\beta}} \right) = 1 + \frac{r_b}{R_s} + \frac{r_b}{R_s \sqrt{\beta}} + \frac{1}{\sqrt{\beta}}$$

Therefore, $F_{min} = \left(1 + \frac{1}{\sqrt{\beta}} \right) \left(1 + \frac{r_b}{R_s} \right)$

If $r_b \ll R_s$ then

$$F_{min} = \left(1 + \frac{1}{\sqrt{\beta}} \right) \text{ and } NF = 10 \log_{10} \left(1 + \frac{1}{\sqrt{\beta}} \right) \text{ dB}$$

Eg

β	NF(dB)
10	1.19
50	0.57
100	0.41

If r_b is not $\ll R_s$ then assuming $\beta=100$


$$NF_{min} = 10 \log_{10} \left[\left(1 + \frac{1}{\sqrt{\beta}} \right) \left(1 + \frac{r_b}{R_s} \right) \right] \text{ dB}$$

r_b/R_s	NF(dB)
2	5.18
1	3.42
0.5	2.17
0.1	0.82

To minimise the noise factor we need to make $r_s \ll R_s$

We could decrease the value of r_b by adding transistors in parallel, however the value of c_{be} will double lowering the frequency response of the amplifier.

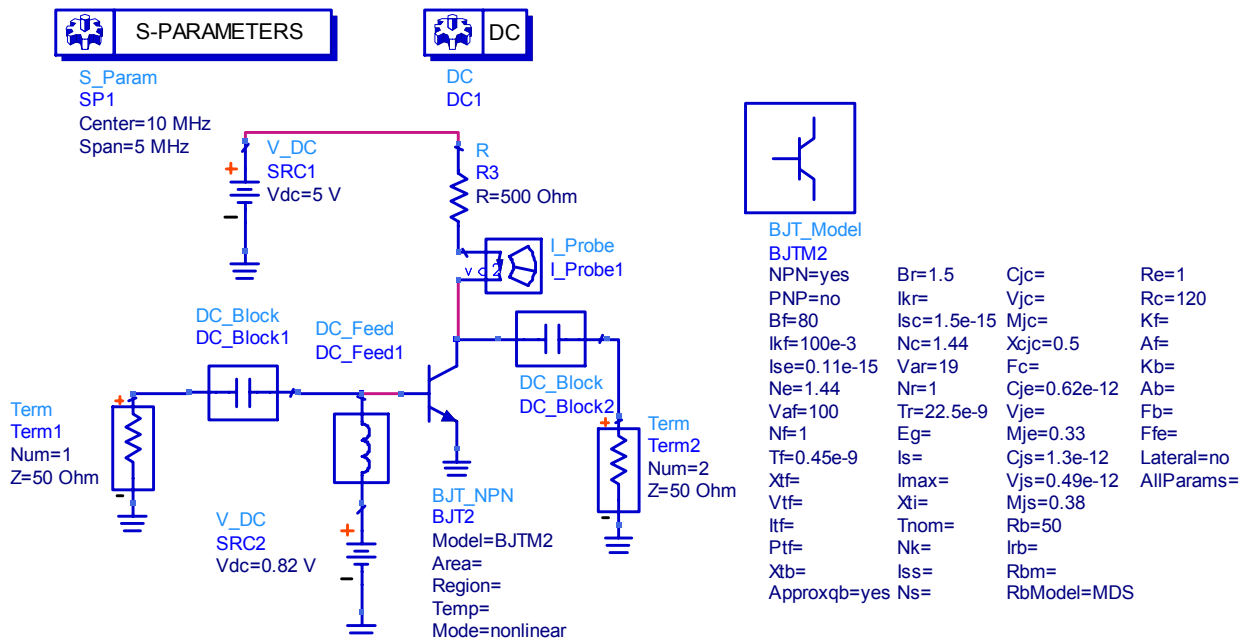As an example consider the following Bipolar amplifier circuit. The device is biased at 5mA (The 500 ohm resistor thus dropping 2.5V). Initially a 50-ohm source resistor is connected to the amplifier input. (Note the DC blocks & feeds are ideal). The plot shows the noise figure (dB) at 10MHz resulting from a r_b/R_s ratio of 50 ohms ($r_b = 50$ ohms).



I_Probe1.i	nf(2)
4.860mA	3.844
	3.857
	3.873

If we decrease the source resistor R_s to 25ohms (ie r_b/R_s ratio of 2) then the noise figure degrades to :-

I_Probe1.i	nf(2)
4.860mA	5.545
	5.555
	5.567

These results seem to agree with the theory. Theory suggests that increasing R_s will decrease the noise figure. However in reality this is not the case.

Repeating the simulation with r_b/R_s ratio of 0.5 ie $R_s = 100$ we obtain the following data:-

I_Probe1.i	nf(2)
4.860mA	2.775
	2.793
	2.816


An improvement on $R_s = 50$ ohms but not the predicted 2.2dB noise figure. The optimum noise figure of the device is limited by the device process.



The one thing this example shows is that if you want to use a source with a low source impedance then some form of low-loss matching is required. For example assume we want to connect a 10ohm source to our amplifier. The resulting simulation results in:-


I_Probe1.i	nf(2)
4.860mA	11.182
	11.190
	11.199

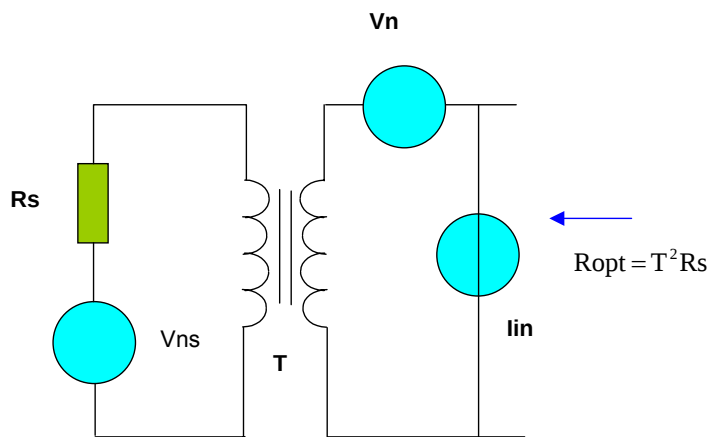However, we could use a transformer to match 10ohms to say 100 ohms to improve our noise figure ie



$$R_{opt} = T^2 \cdot R_s \quad \text{so} \quad R_{opt} = 100 \text{ and } R_s = 5 \text{ then } \sqrt{T} = \sqrt{\frac{100}{5}} ; T = 4.4$$

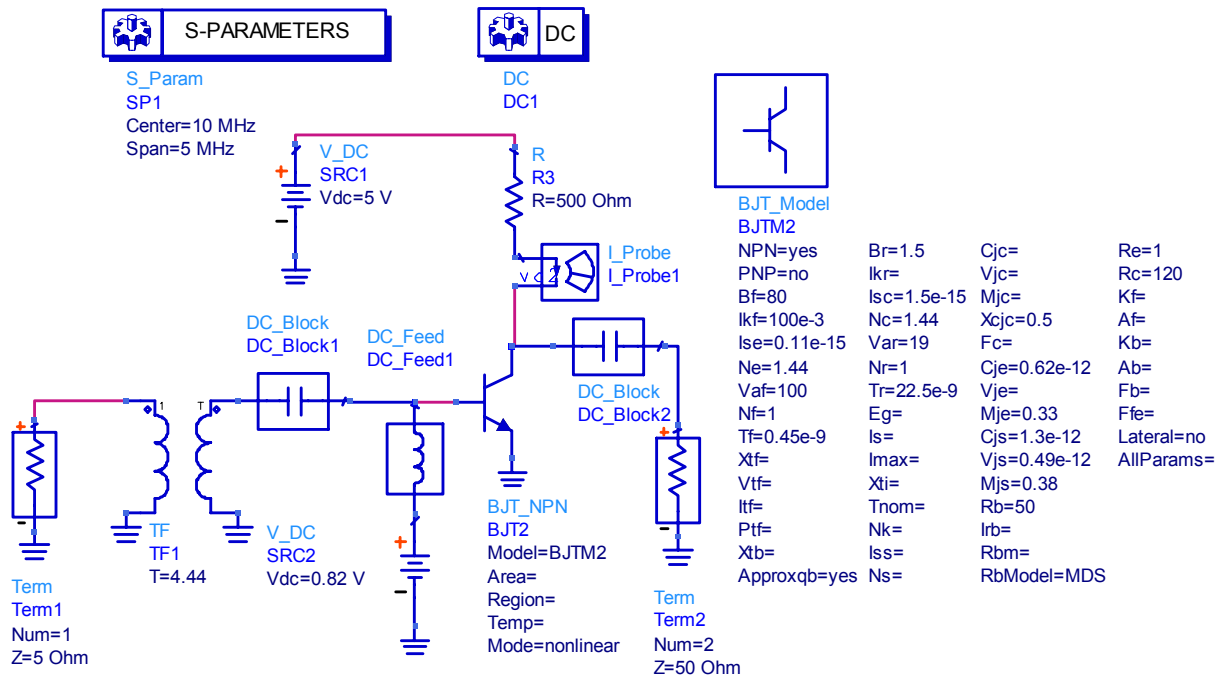So the circuit is modified with an input transformer with a turns ration of ~4.4




We now obtain the following noise figure:-

I_Probe1.i	nf(2)
4.860mA	2.790
	2.808
	2.831



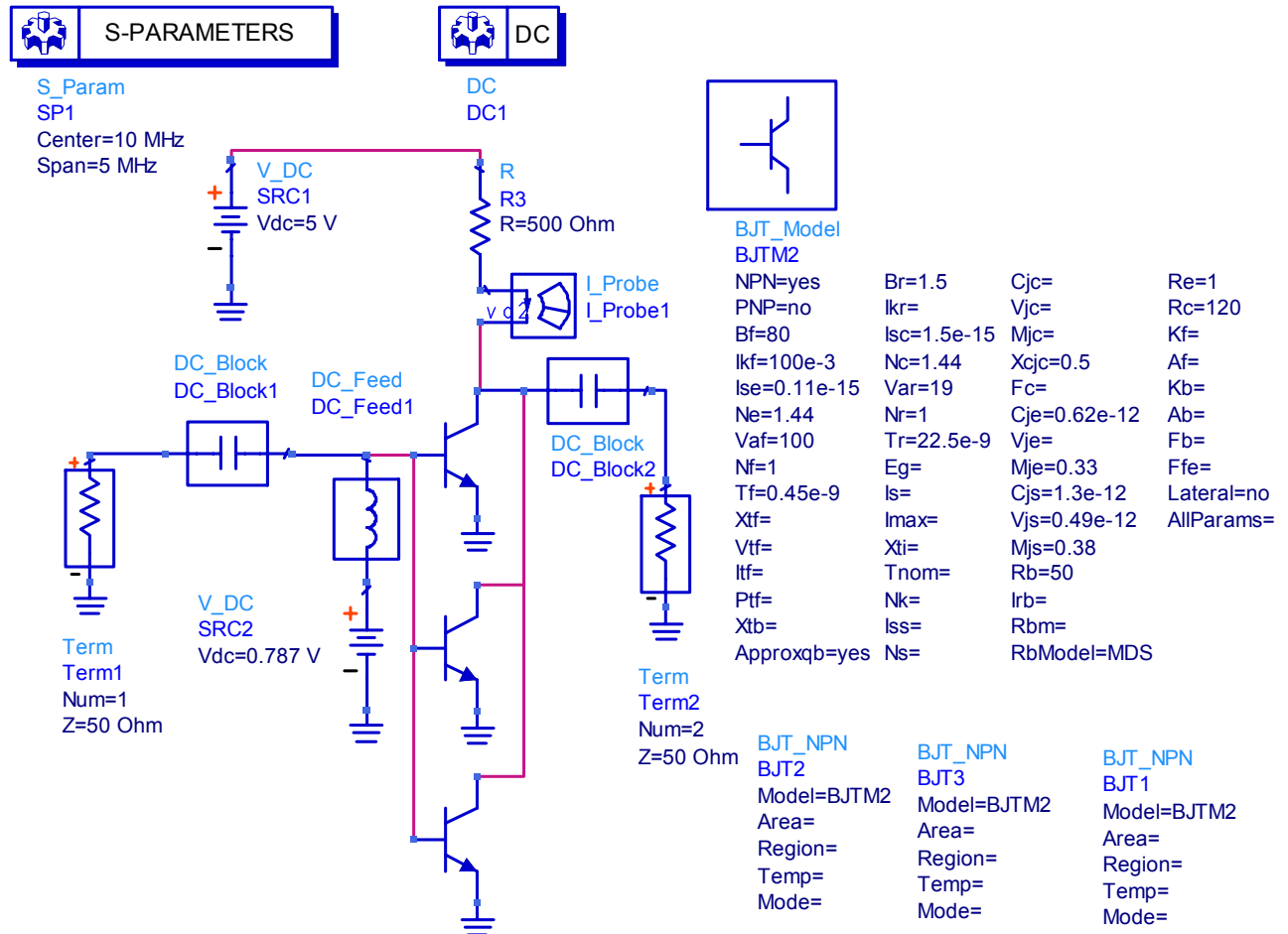Also the noise figure can be reduced, by adding more transistors in parallel. The basic amplifier with $R_s = 50$ ohms yielded a noise figure of 3.8. Adding two more transistors (and readjusting the bias to maintain 5mA in the load) improves the noise figure to:-



freq	I_Probe1.i	freq	nf(2)
0.0000 ...	5.153mA	7.500M...	1.902
		10.00M...	1.912
		12.50M...	1.925



Single-frequency noise matching

The previous example was a broad-band LNA as the matching was purely resistive, however for frequency matching we need to add frequency dependant components in the matching circuit ie inductance and capacitance.

$$V_{eq}^2 = 4kT\Delta f \left[R_s + r_b + \frac{r_e}{2} + \frac{(r_b + (R_s + j\omega.L_s))^2}{2\beta.r_e} \right] \text{ neglecting flicker noise contribution}$$

$$= 4kT\Delta f \left[R_s + r_b + \frac{r_e}{2} + \frac{r_b^2 + R_s^2 + \omega.^2.L_s^2}{2\beta.r_e} \right] = 4kT\Delta f \left[R_s + r_b + \frac{r_e}{2} + \frac{(r_b + R_s)^2 + (2\pi.f.L_s)^2}{2\beta.r_e} \right] V^2/Hz$$

To minimise the input noise at a single frequency , we set $d(V_{eq}^2)/dr_e = 0$.

$$4kT\Delta f \left[R_s + r_b + \frac{r_e}{2} + \frac{(r_b + R_s)^2 + (2\pi.f.L_s)^2}{2\beta.r_e} \right] \Delta f = 1 \text{ (Single frequency)}$$

$$4kT \left[\frac{1}{2} - \frac{(r_b + R_s)^2 + (2\pi.f.L_s)^2}{2\beta.r_e^2} \right] = 0 \text{ Eliminate constants}$$


$$\frac{(r_b + R_s)^2 + (2\pi.f.L_s)^2}{2\beta.r_e^2} = 0$$

$$\text{Rearrange to get } r_{e(opt)} = \sqrt{\frac{(r_b + R_s)^2 + (2\pi.f.L_s)^2}{2\beta}}$$


To minimise the noise over a given bandwidth $(f_2 - f_1)$ we perform a similar process to obtain:-

$$r_{e(opt)} = \frac{1}{\sqrt{\beta}} \left\{ (r_b + R_s)^2 + \frac{(2\pi.L_s)^2}{3} \left(\frac{f_2^3 - f_1^3}{f_2 - f_1} \right) \right\}^{1/2}$$

CS stage with Series Source Impedance

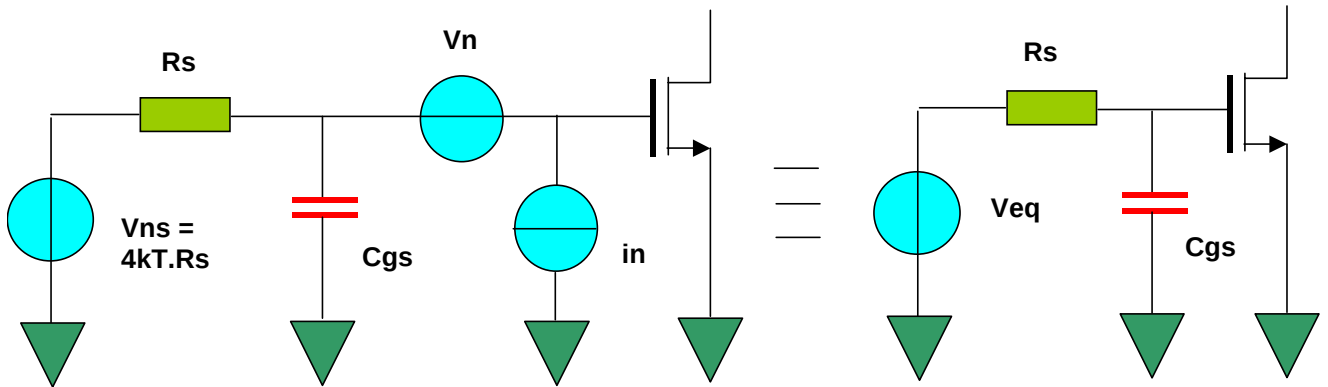

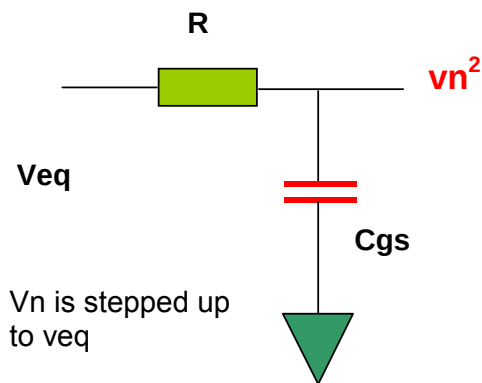For this case we refer back to the input ie



Ignoring effects of in^2

$$veq^2 = vns^2 + vn^2 \left| \frac{1 + Zs}{Xcgs} \right|^2$$


Assuming that the source is resistive

$$veq^2 = \left(4kTRs + \frac{4kT \cdot \gamma}{gm} \left(\frac{1 + f_1}{f} \right) (1 + \omega^2 \cdot Cgs^2 \cdot Rs^2) \right) V^2 / Hz$$


We can see from the above equation that making gm as large as possible will minimise the second noise contribution and is achieved by making the **W/L** ratio large. (There is little we can do about the first contribution ie the source noise). However making W/L large will increase Cgs and hence lower the operating bandwidth of the device.

Inductive Source Degeneration Input matching

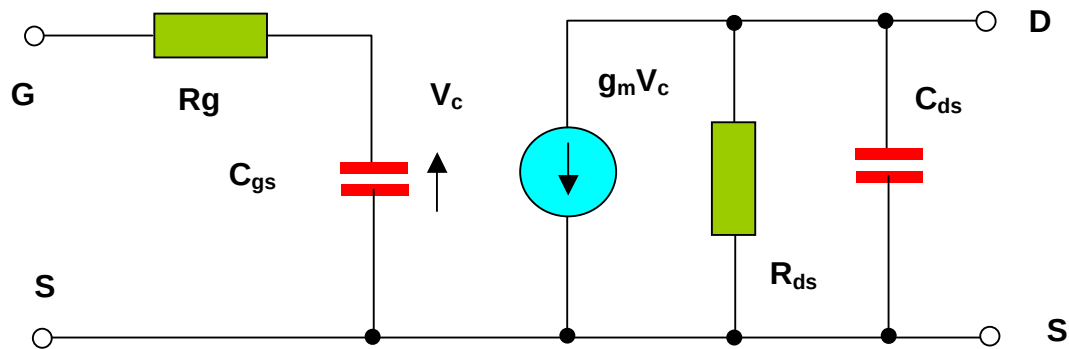
Previous design examples have assumed that the input is resistive and offered the best value of source resistance (R_s) to obtain best noise match. In reality the input of the device is reactive with a real and capacitive impedance. The circuit below shows the equivalent model of a MOSFet:-



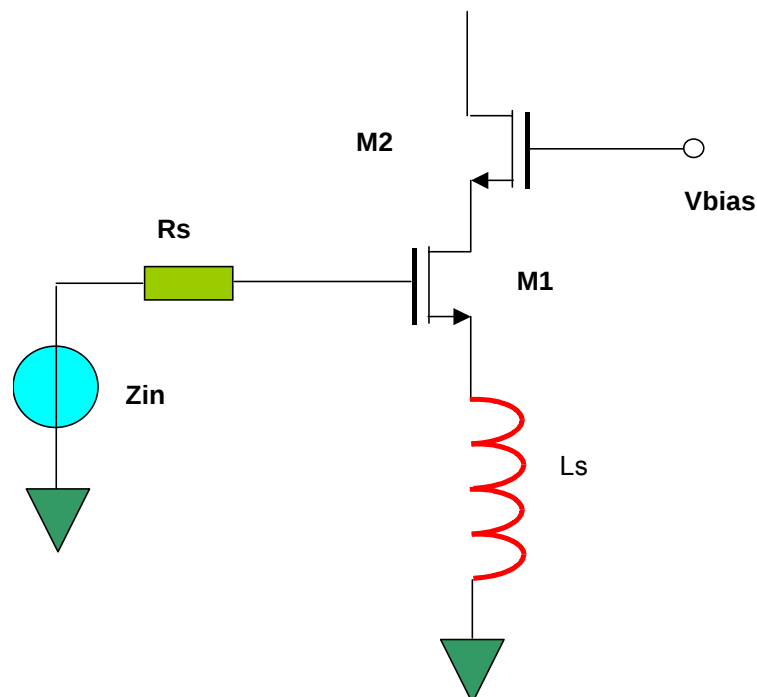What we would like to do is remove the capacitive reactance (and therefore restore the FET input to a pure resistance) and one way of achieving this is to add inductive feedback to the source. The input impedance of the MOSFet circuit below will be capacitive due to the gate-source capacitance.



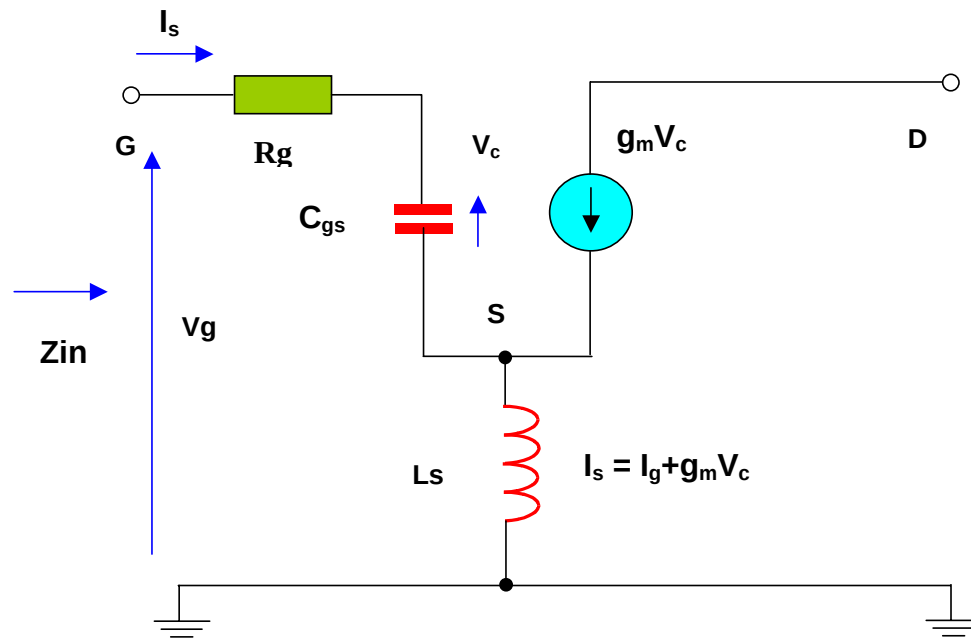If we add lossless inductive feedback to the source the above circuit is again re-drawn as shown below:



$$Z_{in} = \frac{V_g}{I_g} = \frac{(I_g R_g + V_c + j\omega L_s)}{I_g} \quad - (1)$$

$$V_c = \frac{I_g}{S \cdot C_{gs}} \quad \text{and} \quad I_s = I_g + g_m V_c \quad \text{sub into (1)}$$

$$\text{Let } S = j\omega$$



$$Z_{in} = \frac{\left(I_g R_g + \frac{I_g}{S \cdot C_{gs}} + S \cdot \left(I_g + g_m \frac{I_g}{S \cdot C_{gs}} \right) \cdot L_s \right)}{I_g} \quad \text{Divide through by } I_g$$

$$Z_{in} = \frac{I_g R_g}{I_g} + \frac{I_g}{I_g \cdot S \cdot C_{gs}} + S \cdot \left(I_g + g_m \frac{I_g}{S \cdot C_{gs}} \right) \cdot \frac{L_s}{I_g} =$$

$$= R_g + \frac{1}{S \cdot C_{gs}} + S \cdot L_s + S \cdot L_s \cdot g_m \frac{1}{S \cdot C_{gs}}$$

$$= R_g + \frac{1}{S \cdot C_{gs}} + S \cdot L_s + \frac{S \cdot L_s \cdot g_m}{S \cdot C_{gs}} = R_g + \frac{1}{S \cdot C_{gs}} + S \cdot L_s + \frac{L_s \cdot g_m}{C_{gs}}$$

$$R_{in} = R_g + \frac{L_s \cdot g_m}{C_{gs}} + S \left(\frac{1}{S^2 \cdot C_{gs}} + L_s \right) \quad \text{Sub in } S = j\omega$$

$$R_{in} = R_g + \frac{L_s \cdot g_m}{C_{gs}} + j\omega \left(\frac{1}{j\omega^2 \cdot C_{gs}} + L_s \right) = R_g + \frac{L_s \cdot g_m}{C_{gs}} + j\omega \left(L_s - \frac{1}{\omega^2 \cdot C_{gs}} \right)$$

$$R_{in} = R_g + \frac{L_s \cdot g_m}{C_{gs}} + j \left(\omega L_s - \frac{\omega}{\omega^2 \cdot C_{gs}} \right)$$

$$R_{in} = R_g + \frac{L_s \cdot g_m}{C_{gs}} + j \left(\omega L_s - \frac{1}{\omega C_{gs}} \right) \quad \text{Can be re-written as}$$

$$R_{in} = R_g + R_a + j[X_{LS} - X_{CGS}] \quad \text{Where } R_a = \frac{L_s \cdot g_m}{C_{gs}}$$

Therefore, the impedance of the MOSFET without feedback is:-

$$R_{in} = R_g - jX_{CGS}$$

Adding series feedback adds the following term to the original input impedance:-

$$R_a + jX_{LS}$$

Additionally, another inductor is added in series with the gate **L_g** that is selected to resonate with the **C_{gs}** Capacitor.

射频和天线设计培训课程推荐

易迪拓培训(www.edatop.com)由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网(www.mweda.com),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...

课程网址: <http://www.edatop.com/peixun/ads/13.html>



HFSS 学习培训课程套装



该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>