

AN145715

PN544 Antenna Design Guide

Rev. 1.5 — 28th August 2009

Application Note

Document information

Info	Content
Keywords	NFC, PN544, Antenna Design, RF Design
Abstract	This application notes provides guidance on antenna and RF design for NFC device PN544.

Revision history

Rev	Date	Description
1.0	18/02/2008	Initial Release
1.1	14/05/2008	Updates on demo board antenna default matching
1.2	27/02/2009	Update on antenna topology
1.3	12/03/2009	Minor Updates
1.4	30/06/2009	Appendix B added
1.5	28/08/2009	U_{RX} max changed to 1.7V

Contact information

For additional information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

1.1 Purpose and scope

This application draft is intended to give a practical guide to estimate and tune antenna components for the PN544 antenna topology. The PN544 is capable of performing Reader/Writer (R/W) as well as target mode functionalities. This guide is not primarily based on a strong mathematical background but on a practical approach towards PN544 antenna tuning. Therefore it is recommended to read and use this document as described in the chapter 3 "Tuning Procedure".

To get hands-on experience it is recommended to use an antenna which has approximately the same outlines as the one used throughout this document.

This document will be adapted for upcoming versions and may contain a modification of the following topology or even contain further antenna topologies.

2. PN544 Topology

The PN544 topology is outlined in Fig 1. It can be seen that only one antenna (Z_{ant}) is used for Reader/Writer-and Card mode. The number of turns for this antenna topology using the PN544 demo board is six.

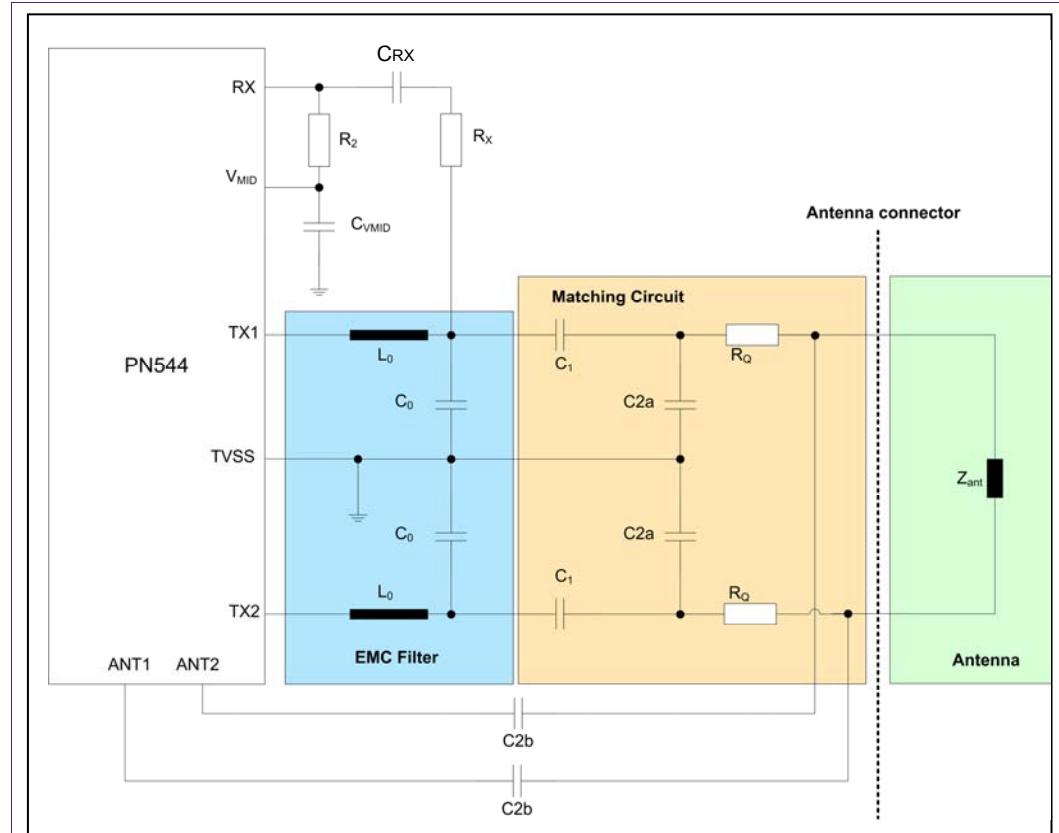


Fig. 1 PN544 antenna topology

The following component tolerances (maximum values) are required for an appropriate tuning:

Component	Maximum tolerance	Component	Maximum tolerance
L0	5%	RQ	5%
C0	5%	Rx	5%
C1	2%	R2	5%
C2a	2%	CRX	5%
C2b	2%	CVMID	5%

The antenna size used throughout this document is 3 cm x 5 cm. Refer also to Table 1 for more details. Fig 2 shows the PCB-schematic of the antenna which is used in this

document. The MatchTX1 and MatchTX2 points are connected to the damping resistors R_q as well as to the capacitors C2b for the ANT1 and ANT2 pins (see also Fig 1).

For the sake of simplicity Fig 2 is a sketch of a possible PN544 demo board antenna.

Connections MatchTX1, MatchTX2 and ANT1, ANT2 on the provided NXP PN544 demo board are routed differently.

This has no impact on the tuning procedure described.

MatchTX1
MatchTX2

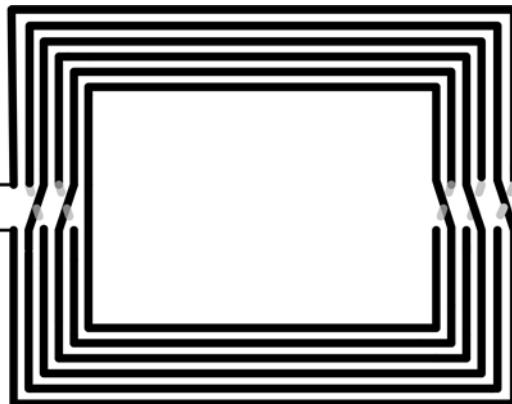


Fig. 2 6-turn demo board antenna sketch

Antenna outlines

Physical outlines of the antenna board are shown here


description	value	dimensions
size	3 x 5	cm
# turns R/W	6	
Copper width	0.05	cm
Spacing	0.05	cm
Copper height	35	μm

3. Tuning Procedure

Please follow the steps below for tuning the antenna. The antenna is matched without powering the PN544 IC. A detailed description of each step will follow after this chapter.

Step 1: At first the antenna has to be matched to the PN544 as described in chapter 4. In this phase C2b is not assembled.

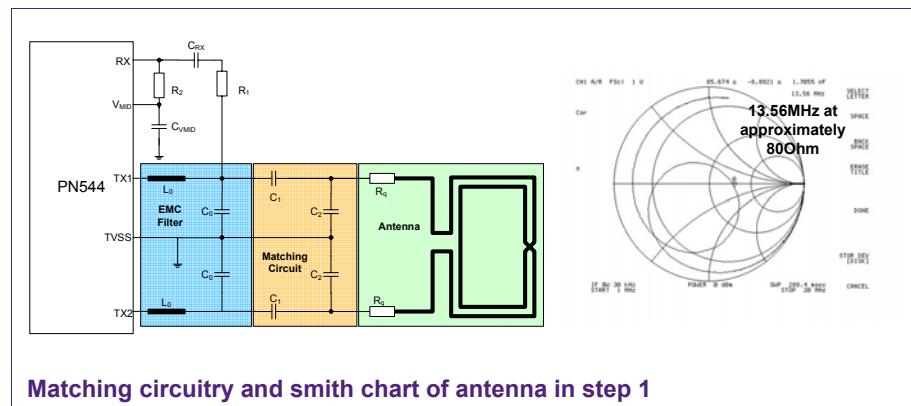
Outcome: Basic tuning with resonance frequency of 13.56MHz at 80Ohm



Step 2: After tuning the antenna, C2b needs to be assembled to connect to ANT1 and ANT2 pins. The C2 value is therefore split-up. This means if C2 is calculated and assembled with 47pF in Step 1, then this value is split up into 20pF for C2a and 27pF for C2b (see chapter Step 4 – Card mode tuning).


Outcome: C2 splits into C2a and C2b. (By assembling C2b, the matching circuit is now configured for card mode)

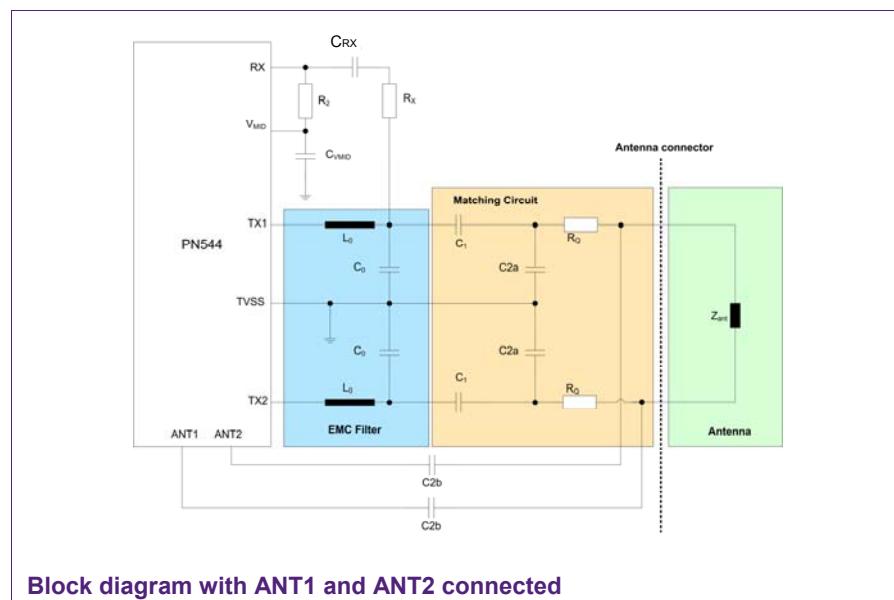Note: The resonance frequency of the card mode is measured contactless as described in Appendix B



Step 3: This step includes the validation of the Reader/Writer matching, which is simulated by shortening the two C2b capacitors with a 10 Ohm resistor. An asymmetric impedance curve with $R_{match}=80\text{Ohm}$ at 13.56Mhz shall be seen on the network analyzer. Further details on fine-tuning can be found in chapter 6.

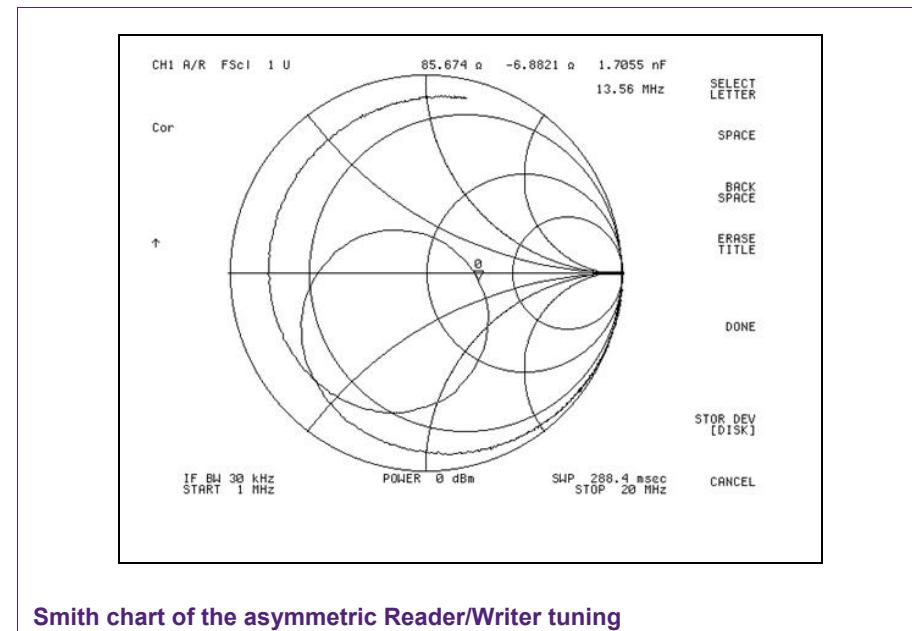Outcome: Asymmetric Reader/Writer tuning at 13.56MHz with $R_{match}=80\text{Ohm}$



Step 4: By removing the 10Ohm resistor, the matching circuit is configured for card mode. The PN544 has to be powered and configured as card. The resonance frequency should be in the range of 14.5 to 16Mhz. Further details on tuning can be found in chapter 7.

Outcome: Card tuning in between 14.5MHz to 16MHz measured with impedance analyzer.

Attention

Step 3 and Step 4 may be repeated to find a good compromise between Reader/Writer and card mode tuning. The target of the tuning is to find component values such that in

- Reader/Writer mode -> $R_{match}=80\text{Ohm}$ at 13.56Mhz
- Card mode -> $f_{res} = 14.5 - 16 \text{ MHz}$

4. Step 1 – Antenna Matching

The **RF block diagram** shows the circuitry design with all relevant components required to connect an antenna to the PN544. It also ensures the transmission of energy and data to the target device as well as the reception of a target device answer.

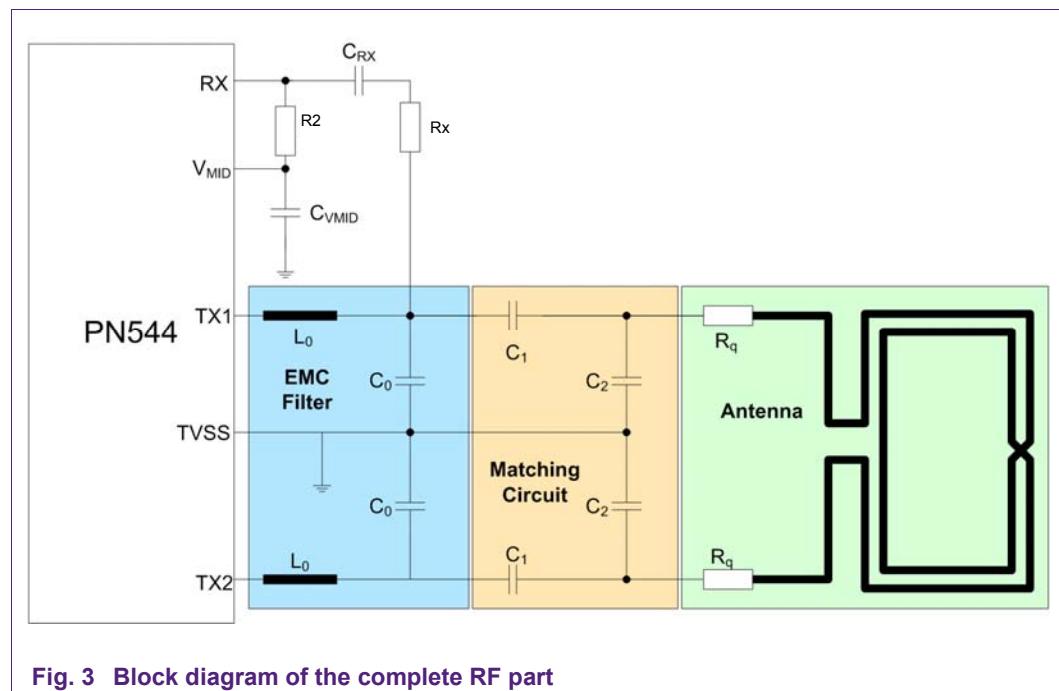


Fig 6 shows only the RF part. For a proper operation the supplies and the host interface have to be connected

The **EMC filter** reduces 13.56MHz harmonics and performs an impedance transformation.

The **Matching Circuit** acts as an impedance transformation block and joins the antenna to the EMC-filter.

The **Antenna** coil itself generates the magnetic field

The **RX** path provides the signal to the PN544 internal receiving stage

4.1 Equivalent circuit

The following subchapters describe the matching procedure. It starts with the determination of the antenna parameters and ends with a fine tuning of the antenna circuitry.

4.1.1 Determination of series equivalent circuit

The antenna loop has to be connected to an impedance or network analyzer to measure the series equivalent components.

The equivalent circuit (see Fig 7) must be determined under final environmental conditions especially if the antenna will be operated in metal environment or a ferrite will be used for shielding.

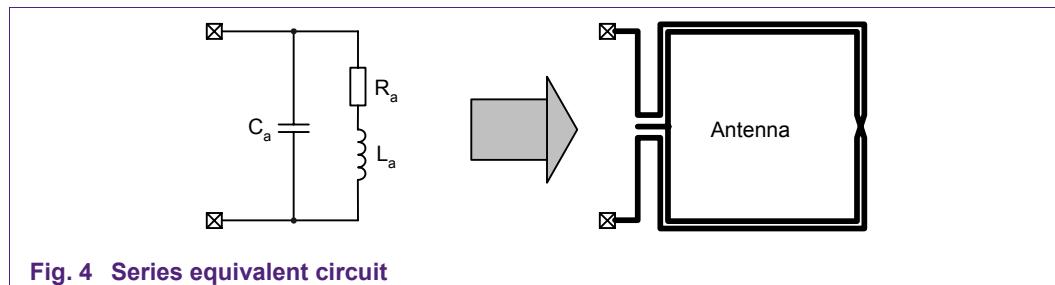


Fig. 4 Series equivalent circuit

Typical values:

$$L_a = 0.3 \dots 3 \mu\text{H}$$

$$C_a = 3 \dots 30 \text{ pF}$$

$$R_a = 0.3 \dots 8 \Omega$$

f_{ra} = self-resonance frequency of the antenna

The antenna capacitance C_a can be calculated with:

$$C_a = \frac{1}{(2 \cdot \pi \cdot f_{ra})^2 L_a} \quad (1)$$

The antenna parasitic capacitance C_a should be kept low to achieve a self-resonance frequency $> 35 \text{ MHz}$.

4.1.2 Calculation of damping resistor RQ

The quality factor of the antenna is calculated with

$$Q_a = \frac{\omega \cdot L_a}{R_a}$$

If the calculated value of Q_a is higher than the target value of 35, an external damping resistor R_Q has to be inserted on each antenna side to reduce the Q-factor to a value of **35 ($\pm 10\%$)**.

The value of R_Q (each side of the antenna) is calculated by

$$R_Q = 0.5 \cdot \left(\frac{\omega \cdot L_a}{35} - R_a \right)$$

4.1.3 Determination of parallel equivalent circuit

The parallel equivalent circuit of the **antenna together with the added external damping resistor R_Q** has to be measured. The quality factor should be checked again to be sure to achieve the required value of $Q=35$.

The equivalent circuit (Fig 8) must be determined under final environmental conditions especially if the antenna will be operated in metal environment or a ferrite will be used for shielding.

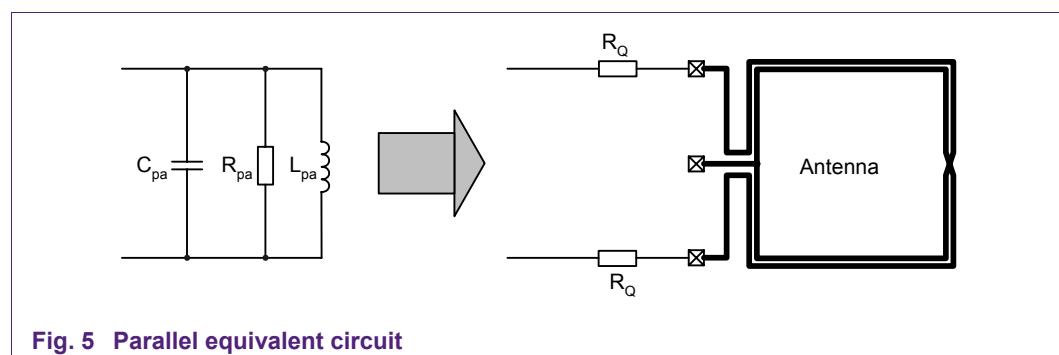


Fig. 5 Parallel equivalent circuit

The following formula applies

$$L_{pa} \hat{=} L_a$$

$$C_{pa} \hat{=} C_a$$


$$R_{pa} \hat{=} \frac{(\omega \cdot L_a)^2}{R_a + 2 \cdot R_Q}$$

4.2 EMC filter design

The EMC filter circuit for the PN544 fulfills two functions: the filtering of the signal and impedance transformation block. The main properties of the impedance transformation are:

Decreasing the amplitude rise time after a modulation phase
Increasing the receiving bandwidth

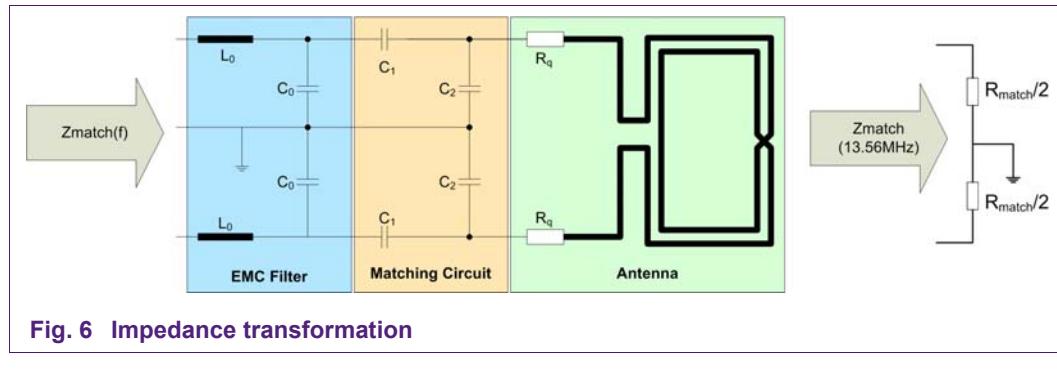
The EMC filter and the matching circuit must transform the antenna impedance to the required TX matching resistance $Z_{\text{match}}(f)$ at the operating frequency of $f = 13.56$ MHz.



The measured $Z_{\text{match}}(f)$ can be remodeled in an equivalent circuit loading each TX pin with $R_{\text{match}/2}$.

When cutting the circuitry after the EMC filter the precondition $R_{\text{match}/2}$ needs to be introduced to calculate the remaining components.

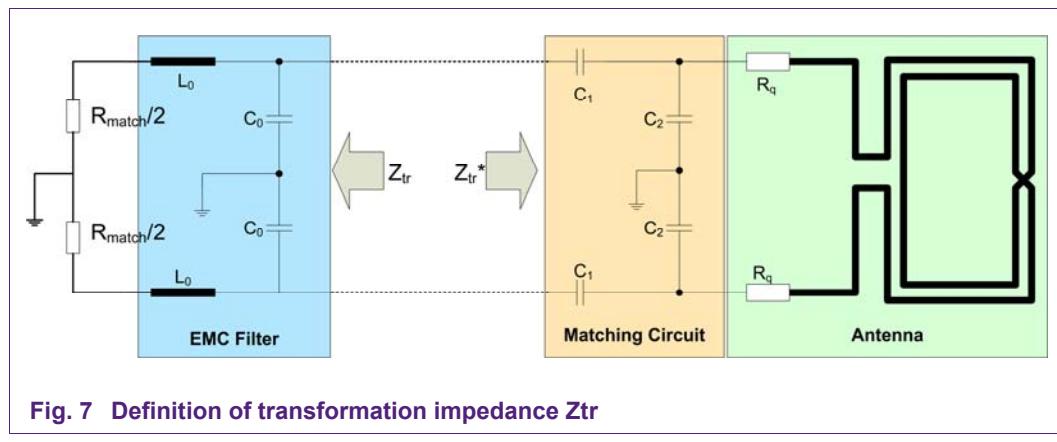Note, that $R_{\text{match}/2}$ does not reflect the driver resistance!



$$Z_{tr} = R_{tr} + jX_{tr}$$

$$Z_{tr}^* = R_{tr} - jX_{tr}$$

EMC filter general design rules:

$$L_0 = 390\text{nH} - 1\mu\text{H}$$

Filter resonance frequency $f_{r0} = 15.5\text{MHz} \dots 16\text{MHz} \Rightarrow C_0$

$$C_0 = \frac{1}{(2 \cdot \pi \cdot f_{r0})^2 L_0}$$

The EMC filter resonance frequency f_{r0} has to be higher than the upper sideband frequency determined by the highest data rate (848 kHz sub carrier) in the system.

Example:

$$L_0 = 560\text{nH}$$

$$f_{r0} = 15.5\text{MHz}$$

$$C_0 = 188.3\text{pF} \rightarrow \text{chosen: } 180\text{pF}$$

A recommended value of 560nH for L_0 is chosen to calculate the capacitance C_0 . The following formulas apply for $Z_{\text{ant}} = \text{Re}(Z_{\text{ant}}) + \text{Im}(Z_{\text{ant}})$ and are needed to calculate the matching components.

$$R_{tr} = \frac{R_{\text{match}}}{(1 - \omega^2 \cdot L_0 \cdot C_0)^2 + \left(\omega \cdot \frac{R_{\text{match}}}{2} \cdot C_0 \right)^2}$$

$$X_{tr} = 2 \cdot \omega \cdot \frac{L_0 \cdot (1 - \omega^2 \cdot L_0 \cdot C_0) - \frac{R_{\text{match}}^2}{4} \cdot C_0}{(1 - \omega^2 \cdot L_0 \cdot C_0)^2 + \left(\omega \cdot \frac{R_{\text{match}}}{2} \cdot C_0 \right)^2}$$

4.2.1 Capacitive tuning of antenna

Due to detuning effects in close distance between reader and card antennas a capacitive tuning is recommended.

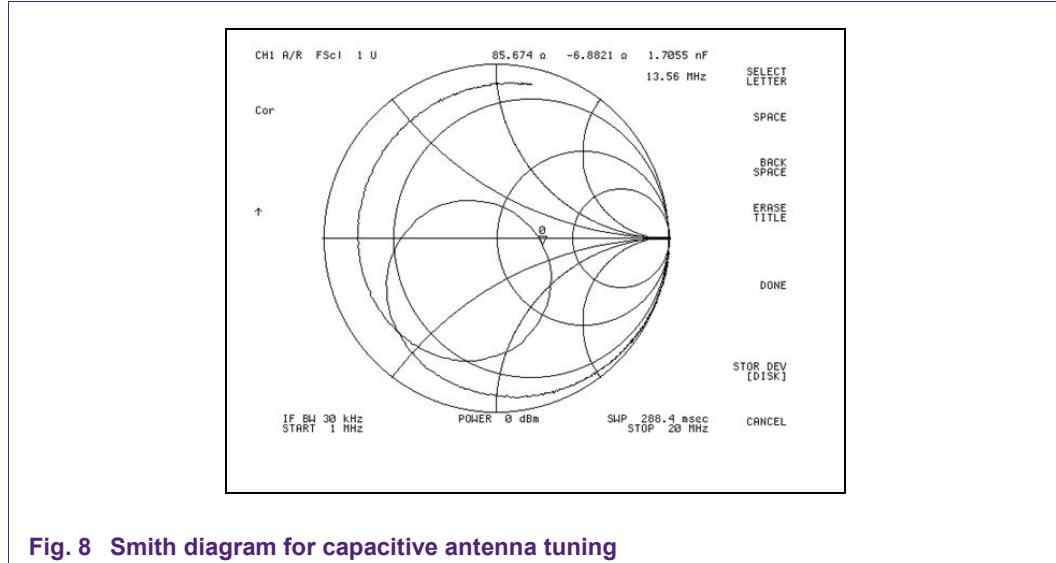


Fig. 8 Smith diagram for capacitive antenna tuning

It is accomplished by lowering C0 compared to the design guidelines given for the first generation NFC devices.

The reason for the higher cut-off frequency is a higher stability with close coupling devices in reader mode: less detuning effect. Minimum field strength of 1.5A/m can be provided also with close coupling devices.

4.3 Matching circuit design

4.3.1 Component calculation

The following formulas apply for the series and parallel matching capacitances:

$$C_1 \approx \frac{1}{\omega \cdot \left(\sqrt{\frac{R_{tr} \cdot R_{pa}}{4}} + \frac{X_{tr}}{2} \right)}$$

$$C_2 \approx \frac{1}{\omega^2 \cdot \frac{L_{pa}}{2}} - \frac{1}{\omega \cdot \sqrt{\frac{R_{tr} \cdot R_{pa}}{4}}} - 2 \cdot C_{pa}$$

Finally, a fine tuning of the matching circuit is often necessary, since the calculated values are based on simplified equations and the equivalent circuit values contain some errors as well.

4.4 Tuning procedure

The matching circuit elements C_1 and C_2 must be tuned to get the required matching resistance R_{match} ($X_{\text{match}} = 0$) at the PN544 TX pins. The matching impedance $Z_{\text{match}} = R_{\text{match}} + jX_{\text{match}}$ is measured with an impedance or network analyzer. The Z_{match} point between TX1 and TX2 as shown in Fig 12 is the probing point for the network/impedance analyzer.

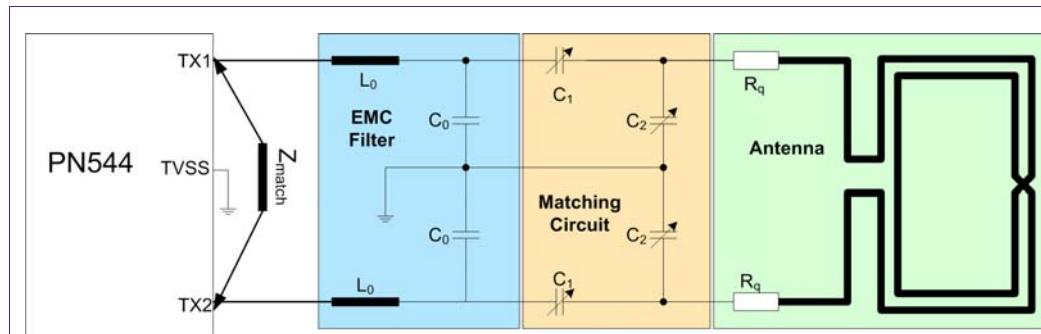


Fig. 9 Measurement of matching impedance

Fig 13 shows the smith chart simulation for $Z_{\text{match}} / 2$:

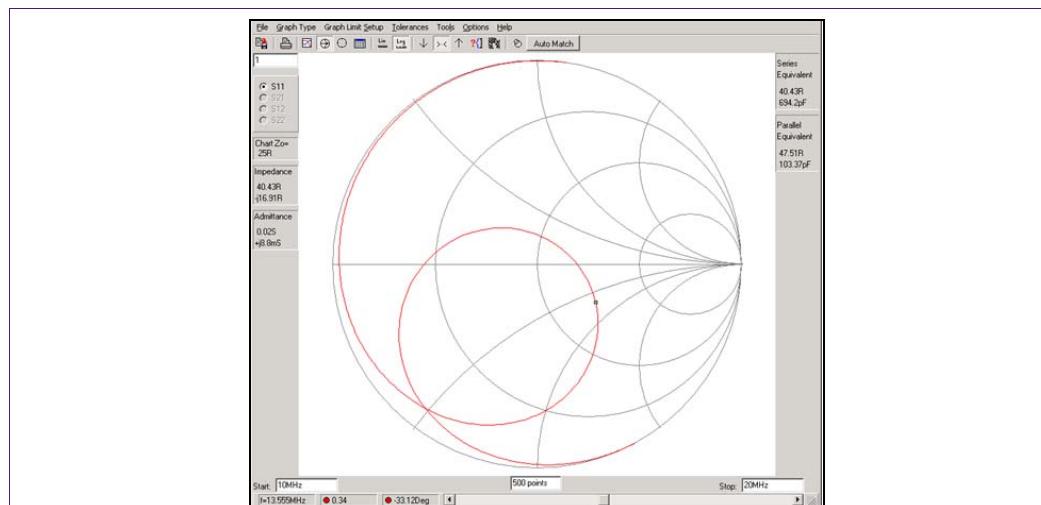


Fig. 10 Smith chart for matching impedance

All tuning and measurement of the NFC antenna has to be performed at the final mounting position to consider all parasitic effects like metal which influences the quality factor, the inductance and parasitic capacitance.

4.4.1 Transmitter matching resistance R_{match}

The transmitter (TX) matching resistance R_{match} defines the equivalent resistance at the operating frequency present between the transmitter output pins TX1 and TX2 of the PN544. Different equivalent resistive loads lead to different transmitter supply currents.


An optimum tuning R_{match} for PN544 is 80Ohm

4.5 Impact of the tuning capacitors visualized on Smith chart

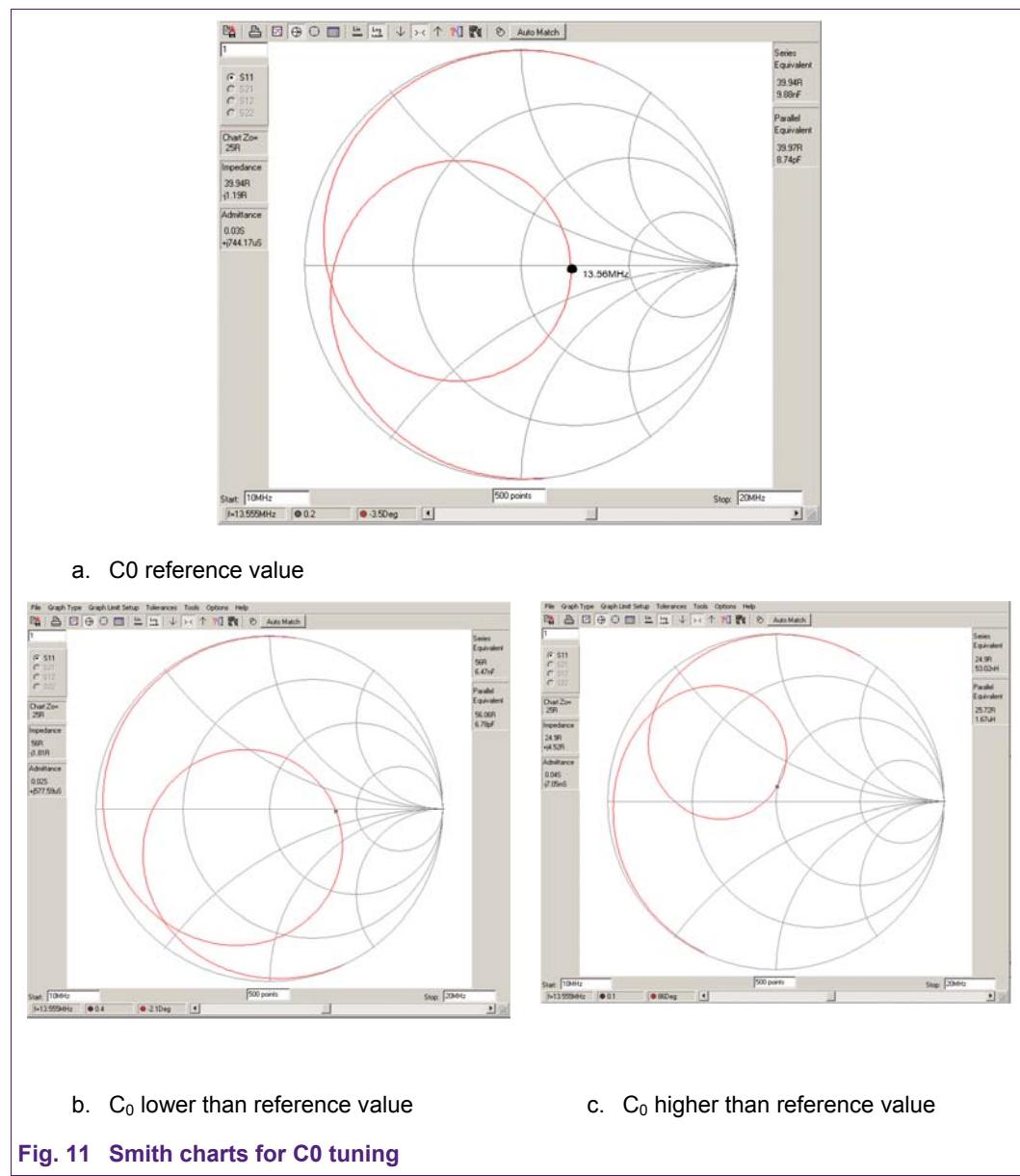4.5.1 EMC capacitance C_0

The following diagrams show the effect to the impedance curve by changing C_0 .


The smith charts show the matching impedance $Z_{\text{match}} / 2$ vs. frequency.



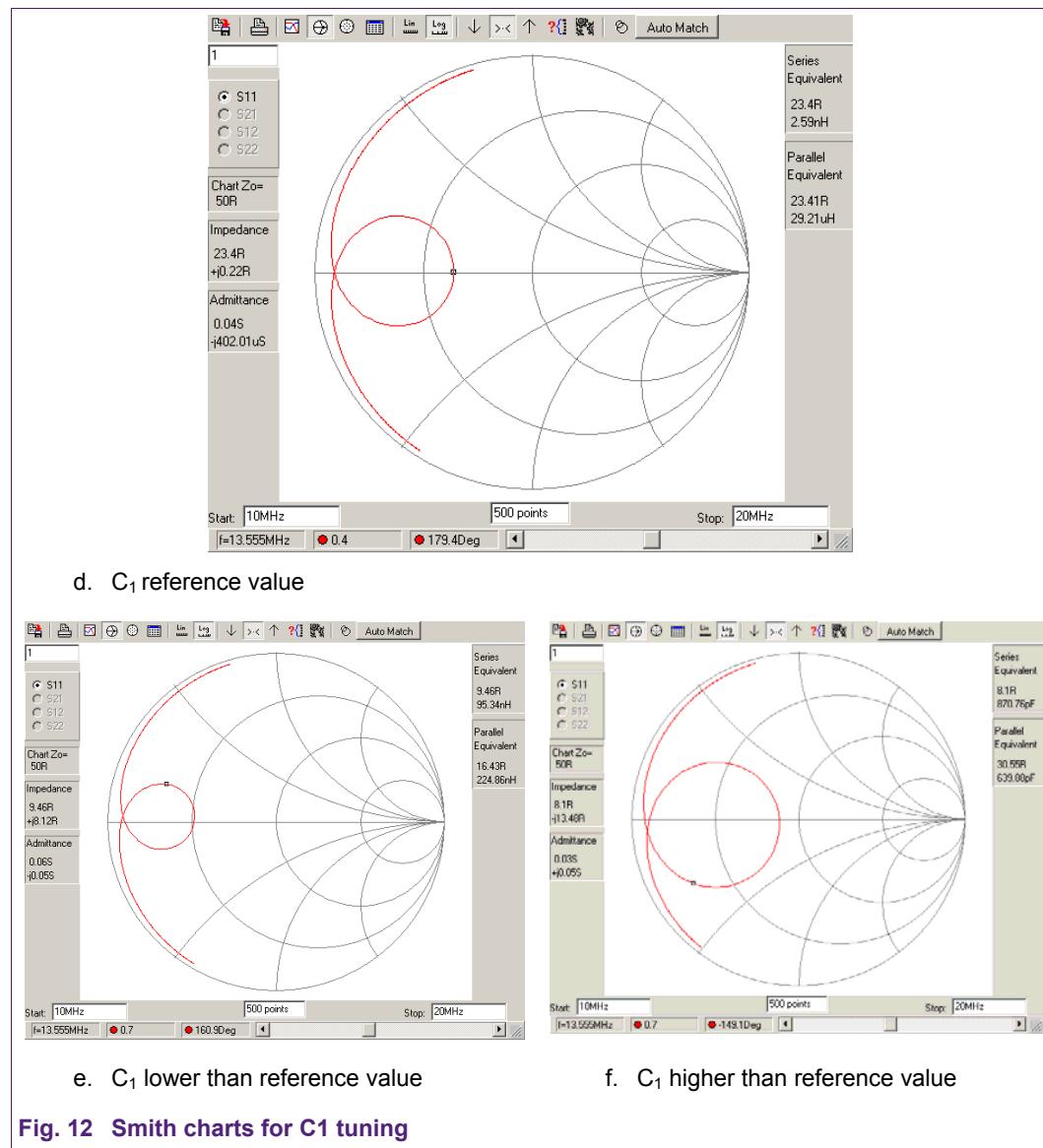4.5.2 Series capacitance C1

The following diagrams show the effect to the impedance curve by changing C1.

The smith charts in Fig 15 show the matching impedance $Z_{\text{match}}/2$ vs. frequency.




C₁ changes the magnitude of the matching impedance. After changing C₁ the imaginary part of Z_{match} must be compensated by adjusting C₂ as well.

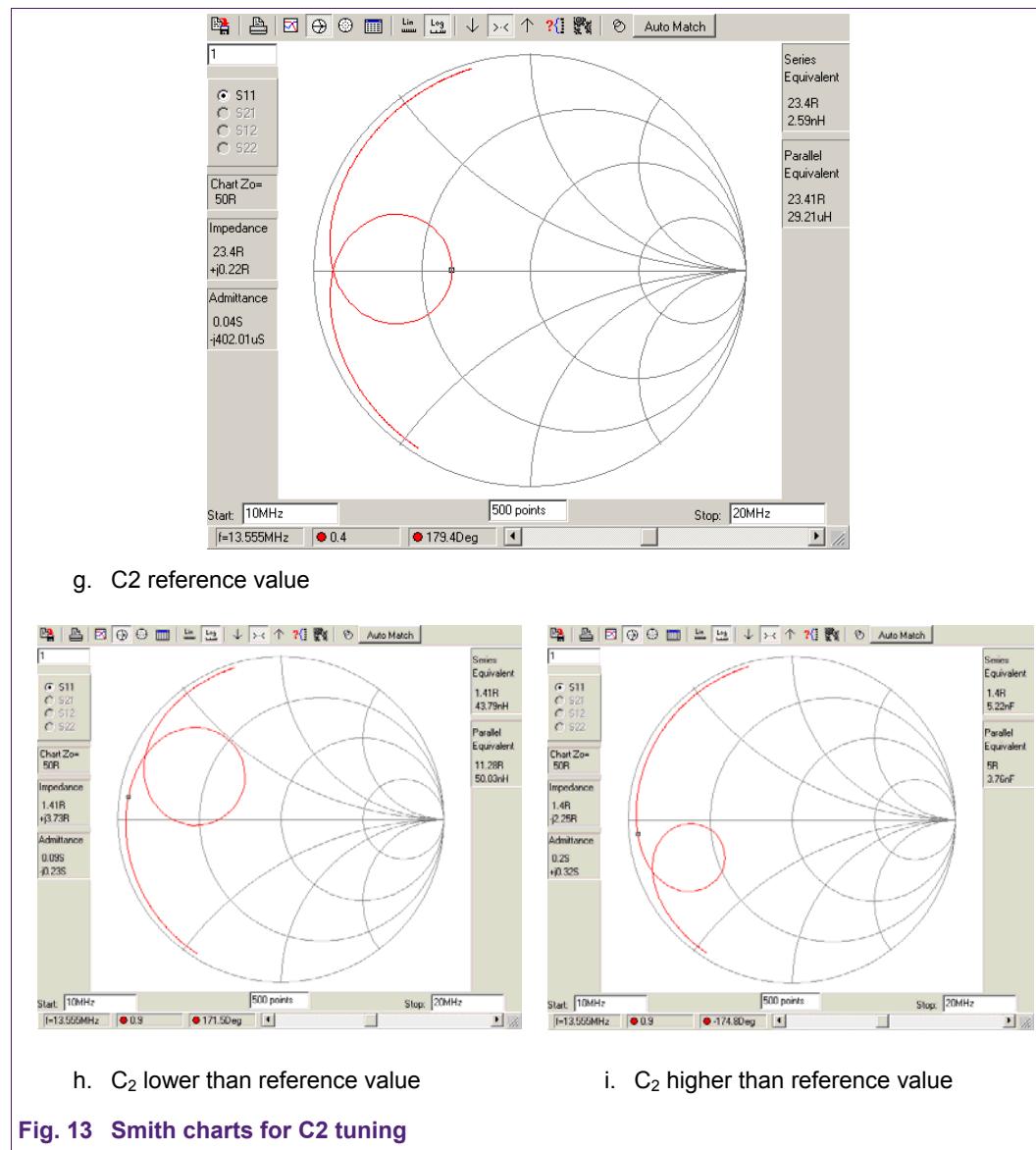4.5.3 Parallel matching capacitance C2

The following diagrams show the effect to the impedance curve by changing C2.

The smith charts show the matching impedance $Z_{\text{match}} / 2$ vs. frequency.



C_2 changes mainly the imaginary part of Z_{match} .

4.6 Receiver circuit design

Next step, after matching and tuning the Reader/Writer antenna, is the design and tuning of the receiver circuit. The investigations need to be carried out for initiator and target mode.


Fig 17 shows the relevant components for the receiver circuit. R_X and R_2 form a voltage divider which has to be adjusted according to the incoming voltage levels at U_{RX} and U_{C0} . Both, Initiator and Target mode of the NFC device have to be investigated, since detuning effects on the RX path behave differently.

The voltage on RX pin U_{RX} must be measured with a low capacitance probe (< 2 pF) for continuous transmitting mode

The voltage U_{RX} must not exceed the maximum value $U_{RXmax}=1.7V$ even when the antenna is detuned by a target or passive card

Hence, the RX-point must be checked under following conditions:

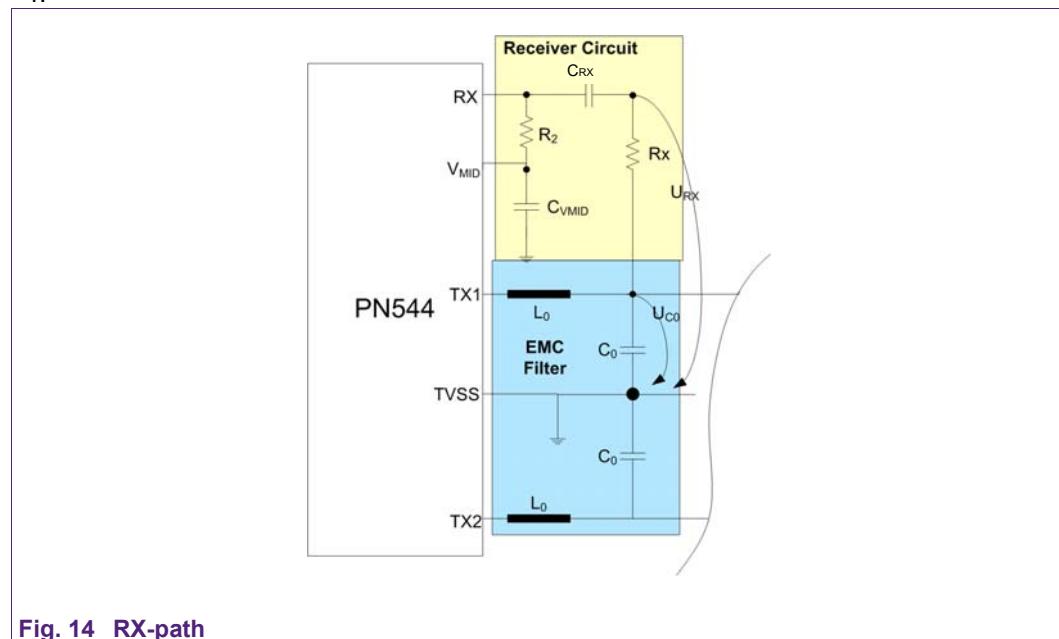1. PN544 antenna not detuned
2. PN544 antenna detuned with a card
3. PN544 in card/target mode and $U_{RX} < U_{RXmax}$ for $H \leq 7.5 \text{ A/m}$
- 4.



4.7 Example

The antenna of the PN544 evaluation board will be matched to the PN544 transmitter output.

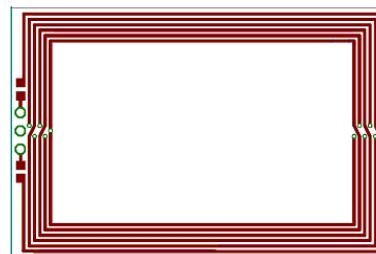


Fig. 15 PN544 evaluation board antenna

Recommended $R_{\text{match}} \approx 80\text{Ohm}$

The series equivalent circuit of the antenna results to:

$$R_a = 1.3\text{Ohm}$$

$$C_a = 11\text{pF}$$

$$L_a = 3.09\mu\text{H}$$

The calculation for the external damping resistor results to $R_Q = 2.5\text{Ohm}$. The chosen value for R_Q is 2.2Ohm and results in a Q-factor of about 30.

The parallel equivalent circuit of the antenna including quality factor damping resistors $R_Q = 2.2\text{Ohm}$ is determined with the following values:

$$R_{\text{pa}} = 20\text{kOhm}$$

$$C_{\text{pa}} = 11\text{pF}$$

$$L_{\text{pa}} = 3.09\mu\text{H}$$

The EMC filter is determined with:

$$L_0 = 560\text{nH}$$

$$C_0 = 180\text{pF}$$


Calculation of Z_{tr} :

$$R_{\text{tr}} = 112\text{Ohm}$$

$$X_{\text{tr}} = -95\text{Ohm}$$

Calculation of the matching parts C_1, C_2 $C_1 = 19.73\text{pF} \rightarrow 18\text{pF}$ normalized value $C_2 = 52.55\text{pF} \rightarrow 47\text{pF}$ normalized value

Simulation result:

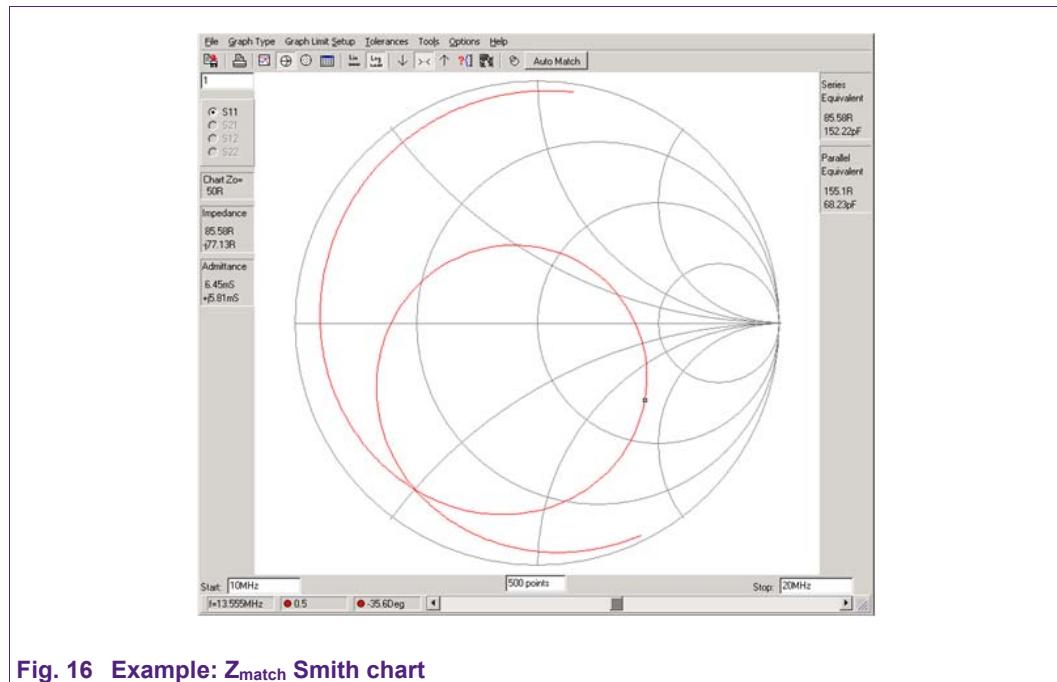**Fig. 16 Example: Z_{match} Smith chart**

It can be seen from Fig 19 that the resonance point (13.56MHz) is in the capacitive part and would need a fine-tuning of the circuit to bring it to $R_{\text{match}}=80\text{Ohm}$.

5. Step 2 – Connecting ANT1 and ANT2 pins

In step 1 we successfully tuned the matching circuit to a resonance frequency at 13.56 MHz at around 80Ohm. The circuit of step one is again outlined in Fig 20.

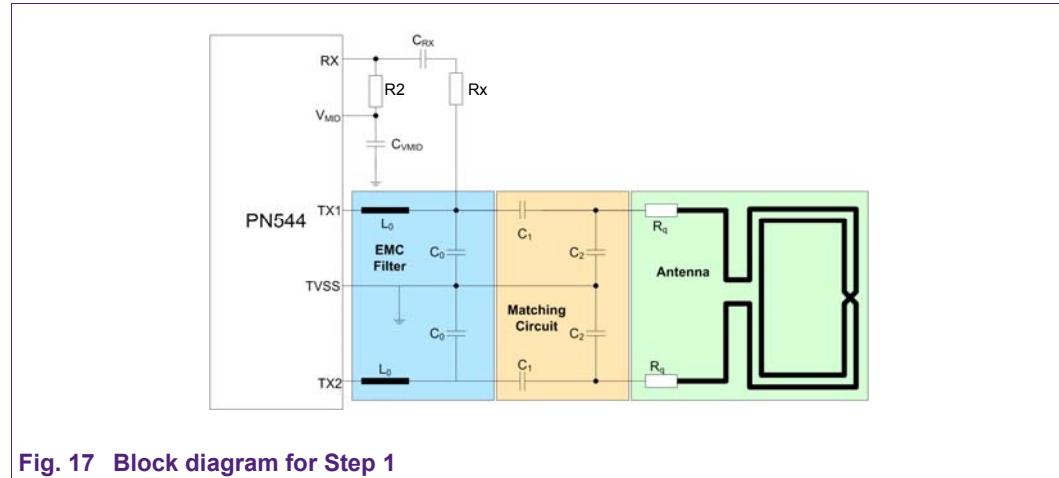


Fig. 17 Block diagram for Step 1

The goal in step 2 is now to connect the ANT1 and ANT2 pins to the matching circuit. Therefore, we decouple the signal after the damping resistors R_q with two additional capacitances. Refer also to Fig 21 for connection details.

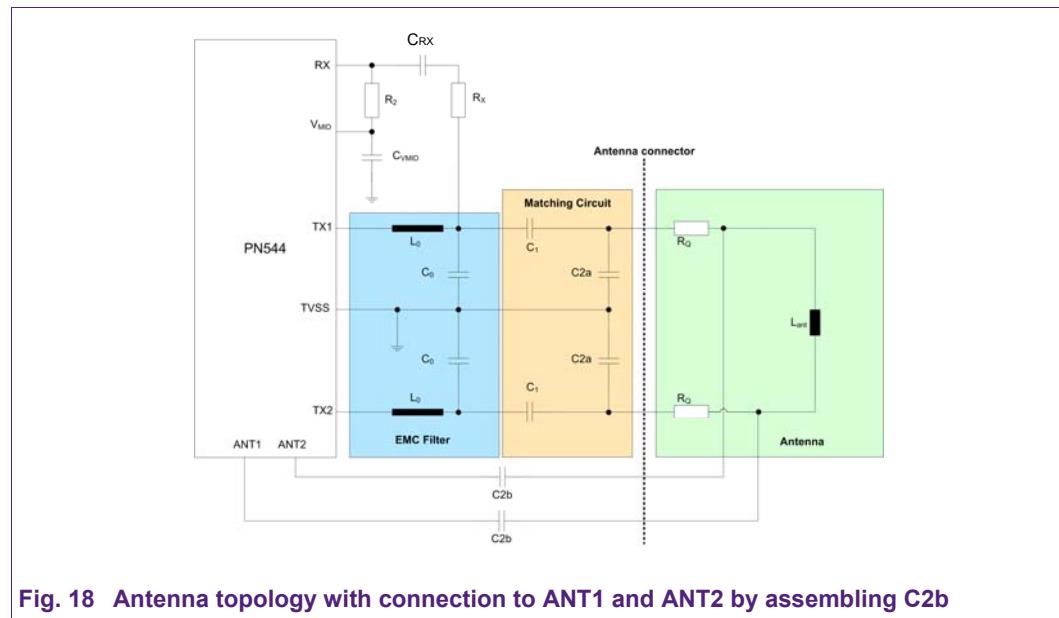


Fig. 18 Antenna topology with connection to ANT1 and ANT2 by assembling C2b

C2a and C2b are derived from the capacitor C2. The splitting ratio must be calculated.

Therefore, the resonance formula (11) is used to calculate the required capacitance for 13.56MHz in Reader/Writer and 14.5-16MHz in card mode. The inductance of the antenna has already been measured in a previous step.

$$f_{res} = \frac{1}{2 \cdot \pi \sqrt{L \cdot C}}$$

$$C_{fres} = \frac{1}{\frac{(2 \cdot \pi \cdot f_{res})^2}{L}}$$

Example for a given inductance value L=3.09uH:

$$C_{13.56\text{MHz}} = 44.66\text{pF}$$

$$C_{16\text{MHz}} = 32\text{pF}$$

$$C_{13.56\text{MHz}} - C_{16\text{MHz}} = 12.66\text{pF}$$

$$C_{shift} = 12.66\text{pF}$$

In other words, the total parallel capacitance for the reader mode needs to be 12.66pF higher than in card mode.

With this information, C2a and C2b can be calculated.

C2 is already given from the previous steps and reflects the $C_{13.56\text{MHz}}$ capacitance.

$$C2 = C2a + C2b$$

$$C2b = 2 \cdot C_{shift}$$

$$C_{shift} = 12.66\text{pF}$$

$$C2b = 25.32\text{pF} \rightarrow 27\text{pF} \text{ normalized value}$$

$$C2a = C2 - C2b = 47\text{pF} - 27\text{pF} = 20\text{pF}$$

In Step 3 and 4 the values/circuitry have to be fine-tuned, because different resonance frequencies are required in Reader/Writer and card mode and available discrete components.

6. Step 3 – Reader/Writer fine-tuning

All tuning steps for the PN544 need to be done without powering the chip.

Precondition to start measurements

In order to simulate the Reader/Writer behavior of the antenna, C2b capacitors need to be shortcut with a 10 Ohm resistor. In the final application this will be taken over by PN544 so do not forget to remove the part after finishing the tuning.

What is the effect?

When shortening C2b with 10Ohm resistance C2b acts as additional capacitance parallel to C2a and causes a frequency shift.

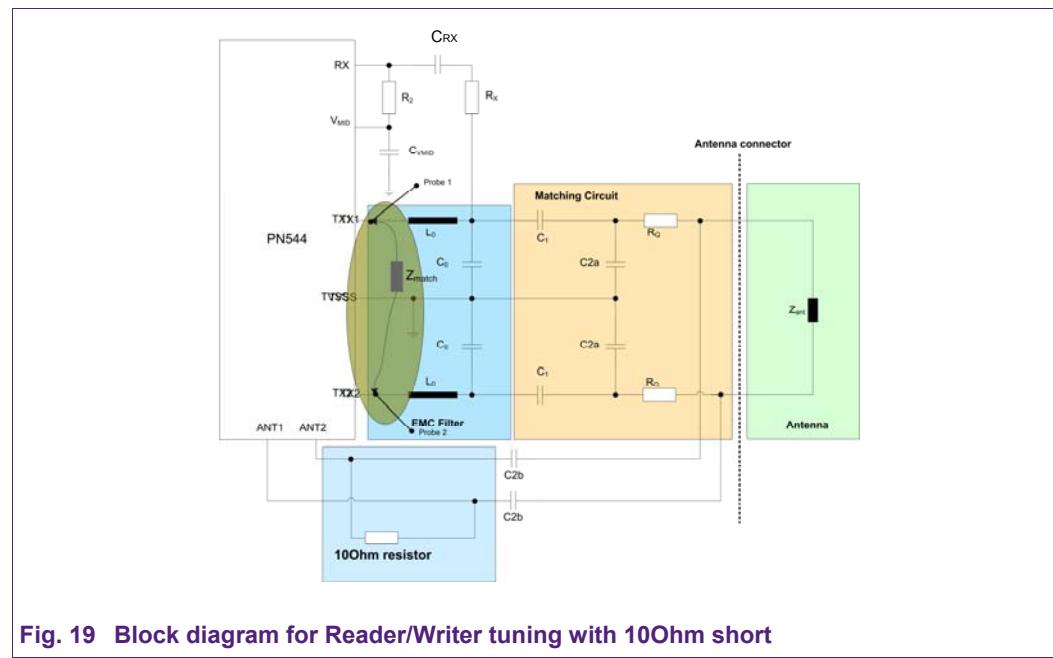


Fig. 19 Block diagram for Reader/Writer tuning with 10Ohm short

Measurement of antenna tuning

The probes of the network analyzer are connected to Probe 1 and Probe 2 as indicated in Fig 23 to verify the matching (Z_{match}).

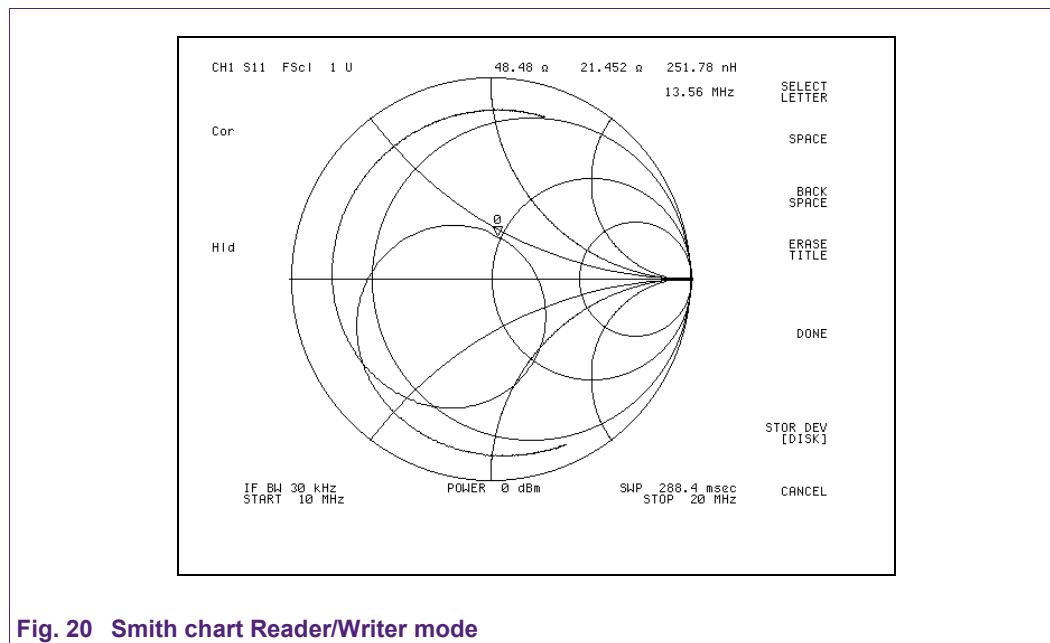


Fig. 20 Smith chart Reader/Writer mode

Adjustments on antenna

According to the results of the measurement slight modifications on C2a/C2b and C1 are needed to finally meet the Z_{match} requirements.

See section 4.5 for the impact of the antenna matching components.

7. Step 4 – Card mode tuning

The tuning steps of PN544 circuitry needs to be done without powering the chip.

After accomplishing "Step 3" we need to verify the card mode.

The 10Ohm resistor has to be removed now!

Card mode tuning is measured with the PN544 being not powered and configured as card.

5.

The resonance frequency of the card mode is measured contactless as described in Appendix B

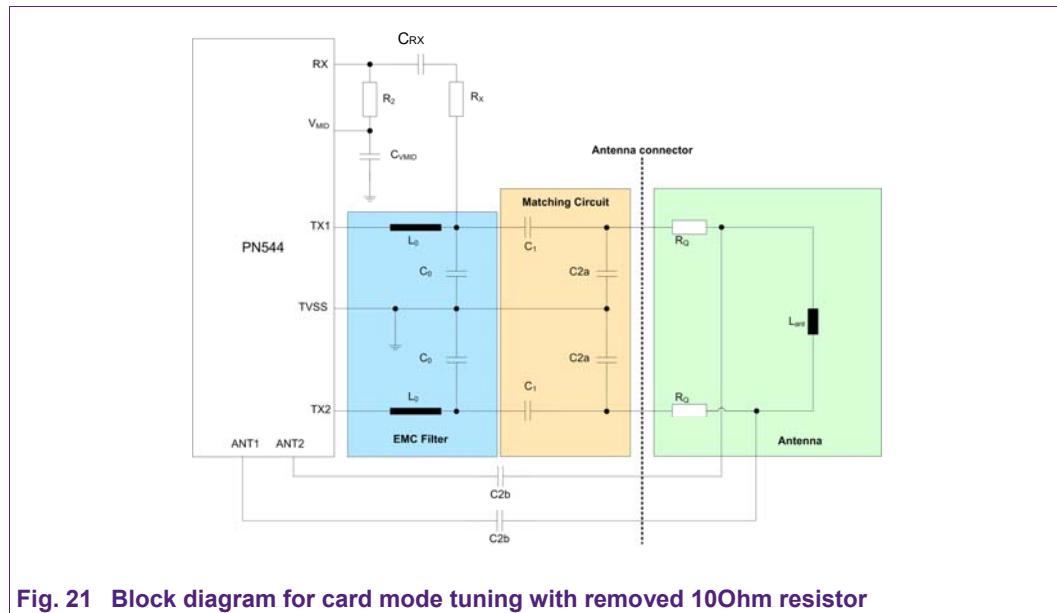


Fig. 21 Block diagram for card mode tuning with removed 100Ohm resistor

The measurement shall show a resonance in the range of 14.5MHz to 16Mhz.

Modifications if resonance frequency does not meet the requirements

1. Resonance frequency too low:

Change the split ratio of C2a and C2b. Reducing C2a by the same amount of capacitance which is added to C2b.

Explanation: C2b is not working in parallel to C2a in card mode. A lower value for C2a means a higher resonance frequency in card mode. Only C2a is working as parallel capacitance towards the antenna.

2. Resonance frequency too high:

Decrease the split ratio C2b/C2a by reducing C2b and increasing C2a by the same capacitance value.

C2a+C2b=constant!

Perform a final check: check Reader/Write and card mode tuning again

8. Appendix

8.1 Antenna design

8.1.1 Antenna inductance

The following two sub-chapters 8.1.2 and 8.1.3 show required formulas to estimate the antenna inductance in free air.

Sophisticated simulation software is required to calculate the antennas parameters to estimate antenna values in environments containing metal (such as shielding planes or batteries in devices).

8.1.2 Circular antennas

Fig 27 shows the profile a typical circular antenna.

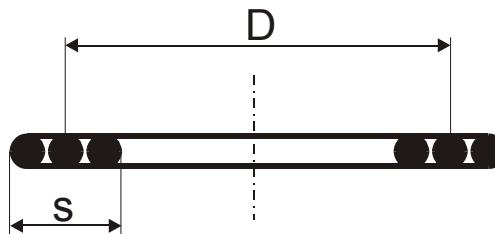


Fig. 22 Circular Antenna

The inductance can be estimated using the following formula:

$$L_a[nH] = \frac{24.6 \cdot N_a^2 \cdot D[cm]}{1 + 2.75 \cdot \frac{s[cm]}{D[cm]}}$$

D Average antenna diameter

s Antenna width

N_a Number of turns

8.1.3 Rectangular antennas

Fig 28 shows a typical rectangular antenna.

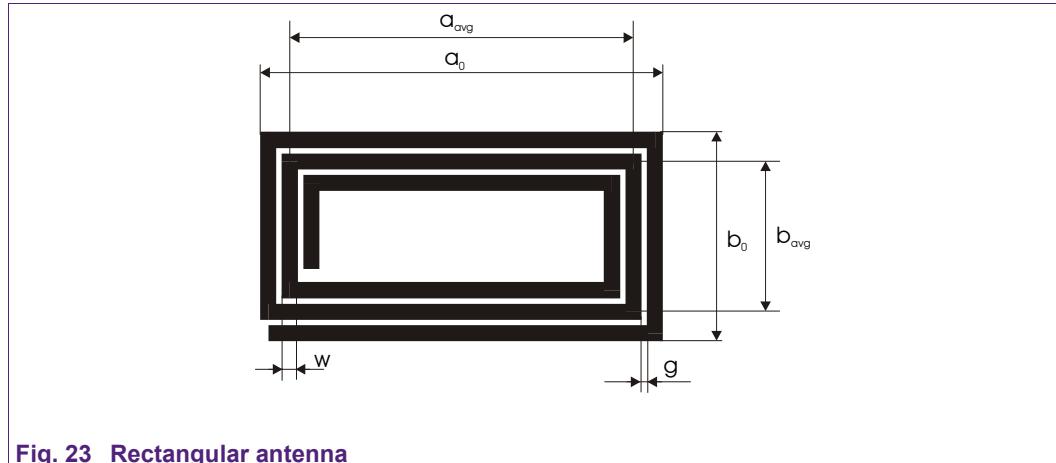


Fig. 23 Rectangular antenna

Variables:

a_0, b_0	Overall dimensions of the coil
a_{avg}, b_{avg}	Average dimensions of the coil
t	Track thickness
w	Track width
g	Gap between tracks
N_a	Number of turns
d	Equivalent diameter of the track

The inductance can be calculated by:

$$L_a = \frac{\mu_0}{\pi} \cdot [x_1 + x_2 - x_3 + x_4] \cdot N_a^{1.8}$$

With:

$$d = \frac{2 \cdot (t + w)}{\pi}$$

$$a_{avg} = a_0 - N_a \cdot (g + w)$$

$$b_{avg} = b_0 - N_a \cdot (g + w)$$

$$x_1 = a_{avg} \cdot \ln \left[\frac{2 \cdot a_{avg} \cdot b_{avg}}{d \cdot \left(a_{avg} + \sqrt{a_{avg}^2 + b_{avg}^2} \right)} \right]$$

$$x_2 = b_{avg} \cdot \ln \left[\frac{2 \cdot a_{avg} \cdot b_{avg}}{d \cdot \left(b_{avg} + \sqrt{a_{avg}^2 + b_{avg}^2} \right)} \right]$$

$$x_3 = 2 \cdot \left[a_{avg} + b_{avg} - \sqrt{a_{avg}^2 + b_{avg}^2} \right] \quad x_4 = \frac{a_{avg} + b_{avg}}{4}$$

8.1.4 Number of turns

Depending on the antenna size, the number of turns has to be chosen in a way to achieve an antenna inductance between 300 nH and 3 μ H.

The parasitic capacitance should be kept as low as possible to achieve a self-resonance frequency > 35 MHz.

A typical the number of turns will be in the range

$N_a=1 - 6$,

which is suitable for various applications and antenna sizes.

Due to the coupling coefficient, a low number of turns is preferred. The lower the numbers of turns, the lower is the influence of coupled devices (e.g. 2nd NFC device, Card, Reader) to the 1st device. This also means that the detuning effect on the 1st device is minimized when reducing the distance between the two devices. The overall performance loss due to low number of turns is negligible.

8.1.5 Antenna symmetry

The symmetry in antenna design is absolutely necessary with respect to tuning and EMC behavior (see Fig 29). Otherwise common mode currents are generated due to parasitic capacitances from the antenna to ground. These currents can cause emissions that hurt the EMV regulations

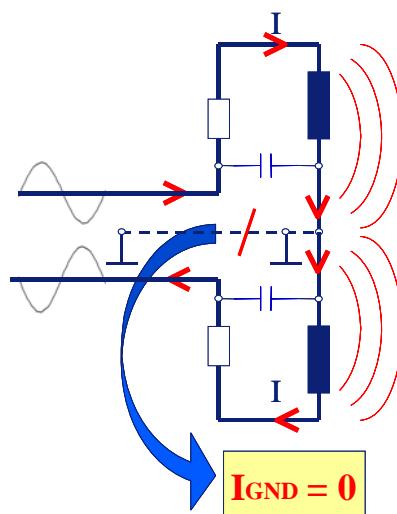


Fig. 24 Ground current compensation

Fig 30 shows an example of a symmetric 4-turn antenna design. It can be seen that the center tap of the antenna is connected to ground. Basically, we do not recommend grounding the center tap, but leaving it floating. This has the advantage of a virtual ground point which is floating to achieve symmetry of the antenna. Refer also to Fig 29 where center tap is not connected.

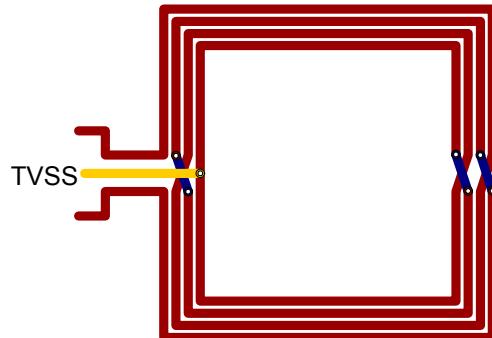


Fig. 25 Example symmetric 4-turn antenna

8.1.6 Ferrite shielding

The benefit of a ferrite is to shield an antenna against the influence of metal. A metal plane could be part of the housing of the NFC device or a ground plane of the NFC device PCB itself, which has to be connected very near to the antenna. If metal is placed very near to the antenna the alternating magnetic field generates eddy currents in the metal. These eddy currents absorb power, and lead to detuning of the antenna due to a decreased inductance and quality factor. Therefore, it is necessary to shield the antenna with ferrite for proper operation in close metallic environment.

The following examples should give estimation about the influence of ferrite to the distribution of the magnetic field.

A circular antenna has been used to simplify the simulation. A circular antenna is rotational symmetric to the x-axis. Therefore, the simulation can be reduced to a two dimensional mathematical problem. The simulation estimates the field distribution of a non-disturbed antenna. It has been assumed an antenna radius of 7.5 cm with 1 turn and a copper wire of 1mm thickness.

Fig 31 shows the two-dimensional magnetic field of the circular antenna.

The right part shows the field distribution. The highest field strength is generated in the area of the coil.

The left part shows the magnitude of the field strength H over the distance d . The minimal field strength of $H_{MIN} = 1.5$ A/m defined by ISO 14443 is marked with doted vertical line.

The shielding effect of the ferrite strongly depends on the ferrite material and the distance between antenna and influencing material. The shielding effect may be

negligible if the antenna is very near to interfering material (metal, battery) and the ferrite has low permeability (foils usually $\mu_R < 10$).

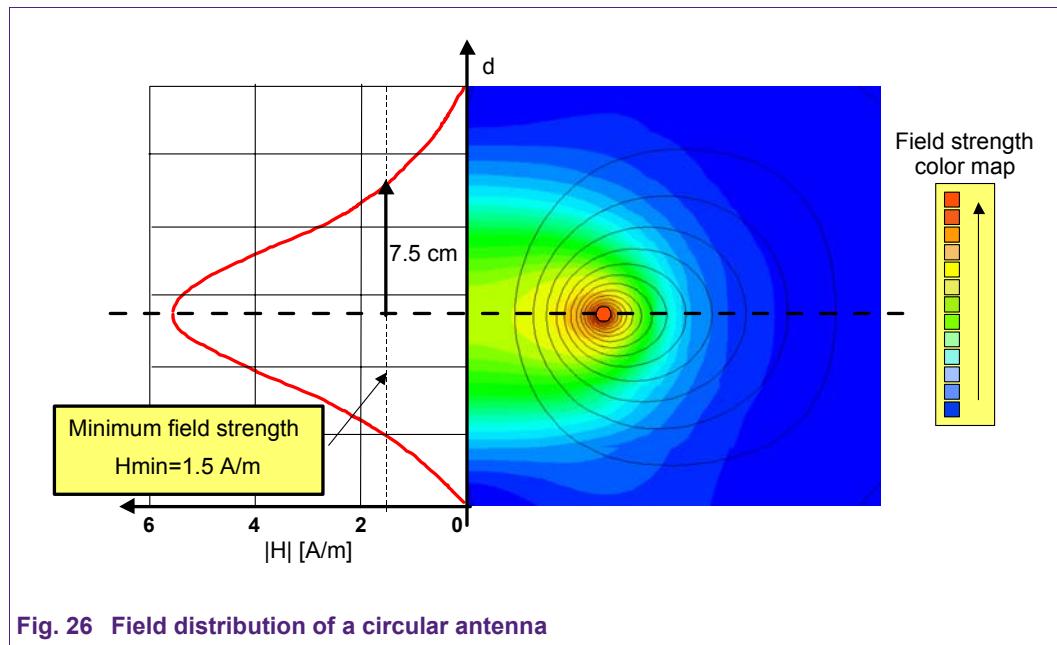


Fig. 26 Field distribution of a circular antenna

Fig 32 shows the field distribution of the defined antenna but a metal plane near to the antenna. The magnitude of the field strength has decreased compared to the disturbed field which leads to a decreased operating distance.

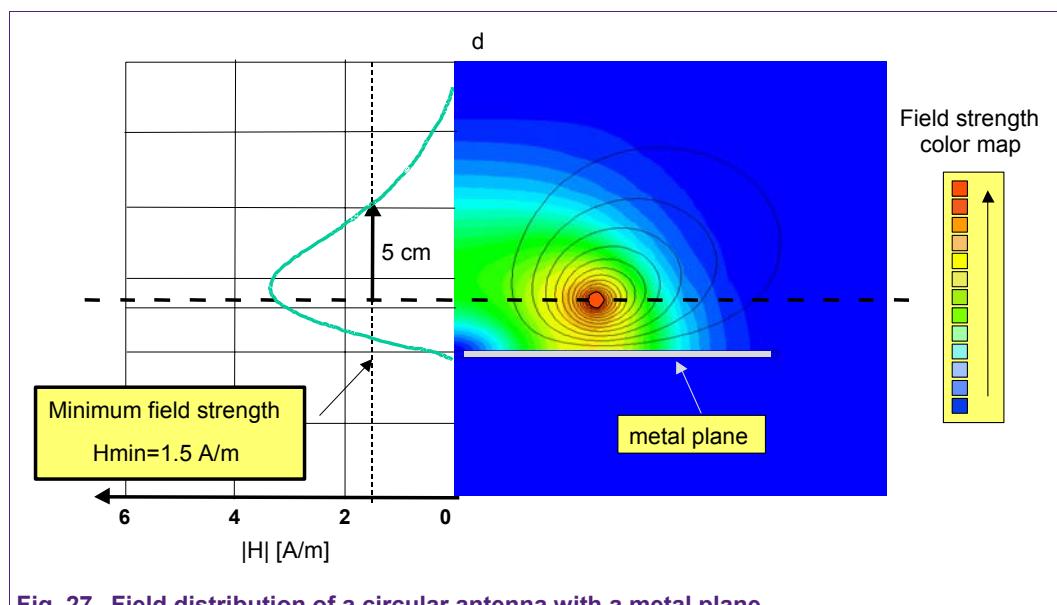


Fig. 27 Field distribution of a circular antenna with a metal plane

Fig 33 shows a ferrite plane ($\mu_R=40$) which is positioned between the metal plane and the antenna coil itself. The field strength very near to the ferrite increases, but the increasing magnitude does not necessarily result in an increase of the operating distance at H_{MIN} value (vertical dotted line).

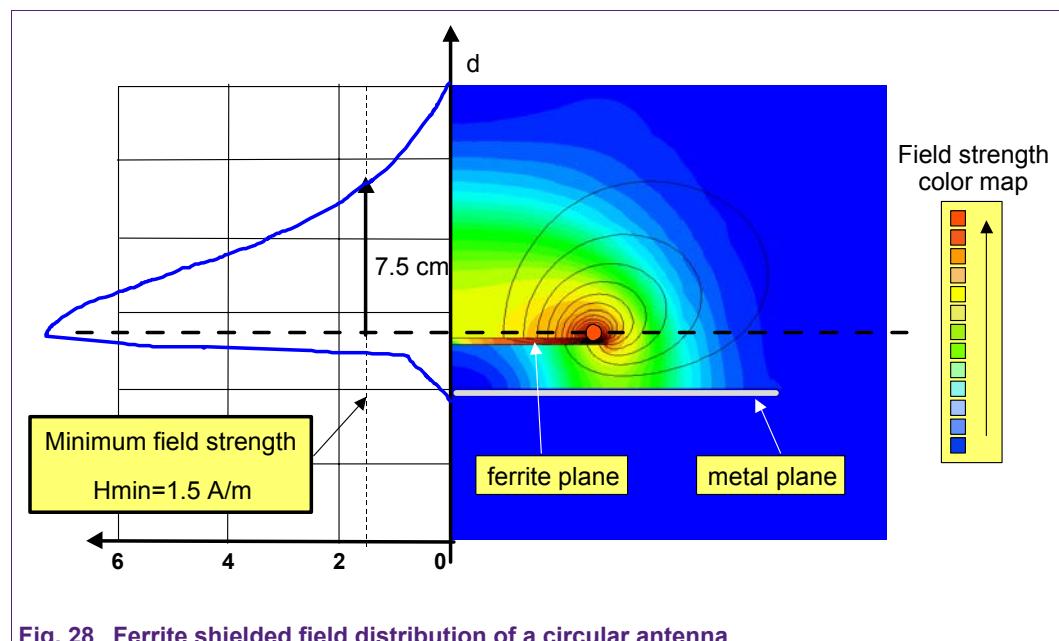


Fig. 28 Ferrite shielded field distribution of a circular antenna

The simulation shows that the use of a ferrite reduces the generated eddy currents in a metal plane. The ferrite generates an additional field component, which results in a fixed detuning of the antenna itself.

8.1.7 Antenna quality factor

The quality factor is a determining constraint to design and tune an antenna. Fig 34 shows an excerpt of a typical 100% ASK modulation. The maximum timing limit of 3us (as defined in the ISO14443) for a modulation pause is taken to calculate the quality factor.

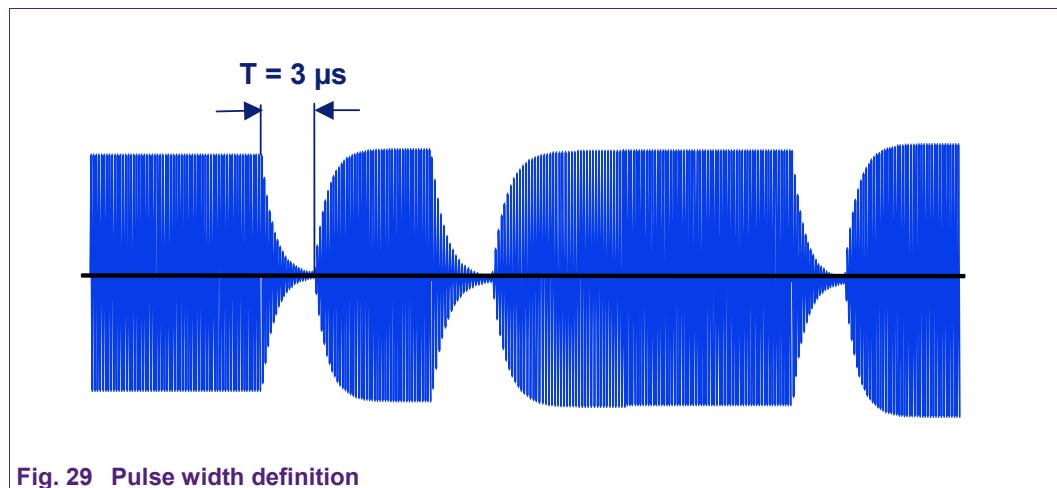


Fig. 29 Pulse width definition

The bandwidth B –pulse width T product is defined as:

$$B \cdot T \geq 1$$

With the bandwidth definition

$$B = \frac{f}{Q}$$

the $B \cdot T$ product results to

$$Q \leq f \cdot T$$

$$Q \leq 13.56 \text{MHz} \cdot 3 \mu s$$

$$Q \leq 40.68$$

The recommended antenna quality factor is $Q_a = 35$

8.2 Equivalent circuit measurement

8.2.1 Impedance analyzer with equivalent circuit calculation

Impedance analyzers like Agilent 4294A or 4395A can determine directly the series or parallel equivalent circuit by measuring the magnitude and the phase of the impedance of the connected antenna.

The antenna has to be at the final mounting position to consider all parasitic effects like metal influence on quality factor, inductance and additional capacitance.

The antenna needs to be connected to the analyzer by using an appropriate test fixture that does not influence any antenna parameters.

The analyzer has to be calibrated (open, short and load compensation at the calibration plane) and the test fixture needs to be compensated (open, short compensation at the connection points) before each measurement. Please refer to device manual on how to carry out these steps.

Settings: $|Z|$, Θ

Start frequency: 1 MHz

Stop frequency: above self-resonance frequency of the antenna (point where antenna impedance is real: pure resistance)

Advantage:

Fast and simple method

Disadvantages:

Additional equipment required

Low accuracy of the measurement which especially results from the loss resistance for high quality factor coils ($Q_{pc} > 60$).

8.2.2 Network analyzer

This section briefly describes the determination of the antenna equivalent circuit using a network analyzer without any equivalent circuit functionality.

The antenna has to be at the final mounting position to consider all parasitic effects like metal influence on quality factor, inductance and additional capacitance.

The antenna needs to be connected to the analyzer by using an appropriate test fixture that does not influence the antenna parameters.

The analyzer has to be calibrated (open, short and load compensation at the calibration plane) and the test fixture needs to be compensated (open, short compensation at the

connection points) before each measurement. Please refer to device manual on how to carry out these steps.

Settings: S11

Chart: Smith Z

Start frequency: 1 MHz

Stop frequency: above self-resonance frequency of the antenna

8.2.3 Series equivalent circuit

The following characteristic circuit elements can be determined by measurements at characteristic points (see also Fig 35 for series equivalent circuit).

R_s Equivalent resistance at $f = 1\text{MHz}$

L_a Equivalent inductance at $f = 1\text{MHz}$


R_p Equivalent resistance at the self-resonance frequency

f_{ra} Self-resonance frequency of the antenna

The antenna capacitance C_a can be calculated with:

$$C_a = \frac{1}{(2 \cdot \pi \cdot f_{ra})^2 L_a}$$

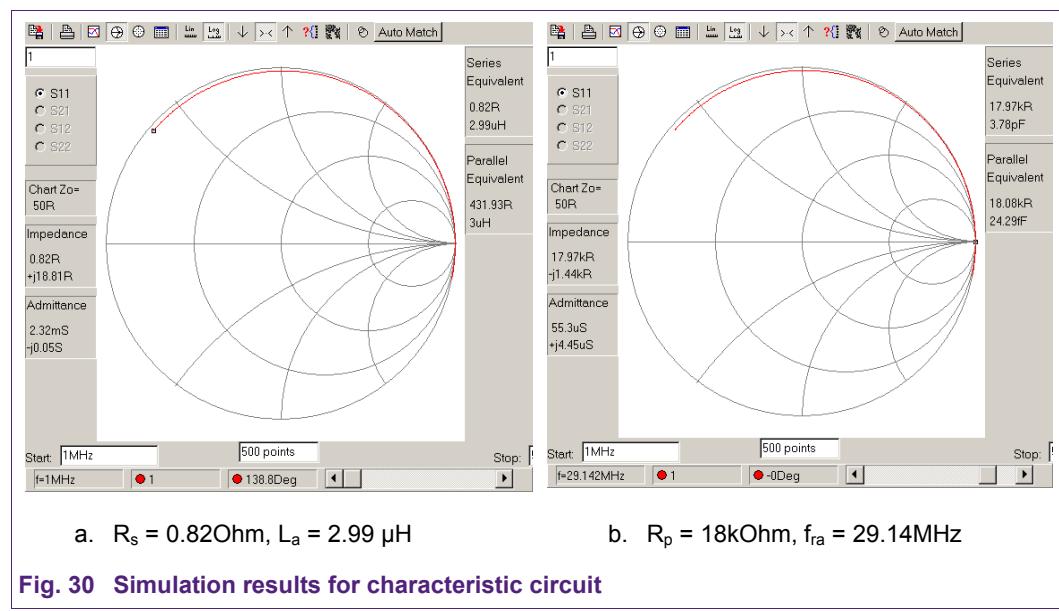The following Fig 37 shows simulation results to determine the characteristic circuit.



The series equivalent resistance of the antenna at the operating frequency $f_{op} = 13.56\text{MHz}$ can be calculated out of the characteristic circuit.

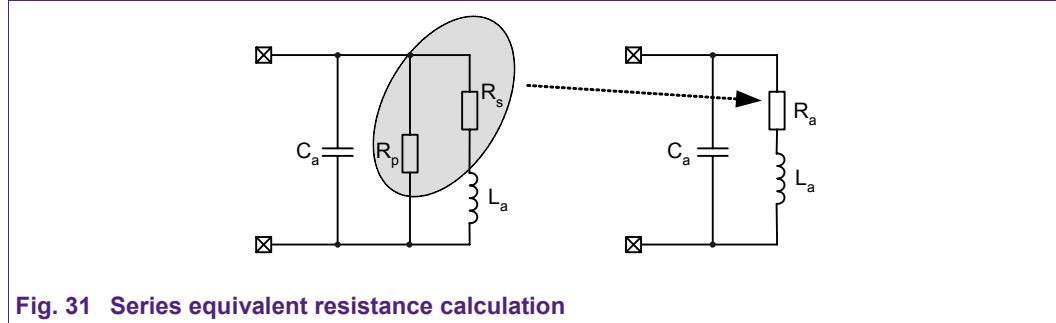


Fig. 31 Series equivalent resistance calculation

$$R_p(13.56\text{MHz}) = \frac{R_p(fres)}{\sqrt{\frac{13.56}{fres}}}$$

$$R_a = R_s + \frac{(2 \cdot \pi \cdot f_{op} \cdot L_a)^2}{R_p(13.56\text{MHz})}$$

The parallel equivalent circuit always has to be calculated by means of the series equivalent circuit using equation (19).

The parallel resistance $R_p(fres)$ obtained by measurements has to be calculated to the parallel equivalent value at 13.56MHz. This is accomplished in equation (21).

R_a in equation (22) is then calculated by using $R_p(13.56\text{MHz})$.

8.3 PULSE shape check

The following pulse shape checks are a quick way for investigating the shaping of the generated RF-field. Chapter 8.5 points out the pulse shape timings according to ISO/IEC18092:2004. Please note that always to the latest version of ISO/IEC18092 is referenced.

The correct measurement techniques needs to be carried out in ISO/IEC 22536 (NFCIP – RF Interface Test methods) and/or ISO/IEC 10373-6 (Identification cards – Test methods) and ISO/IEC14443!

The Q-factor can be checked by using the fact that the Q-factor has a direct influence on the edges of the modulation shape.

An oscilloscope with a bandwidth of at least 50MHz has to be used to carry out the module shape measurements (Fig 39).

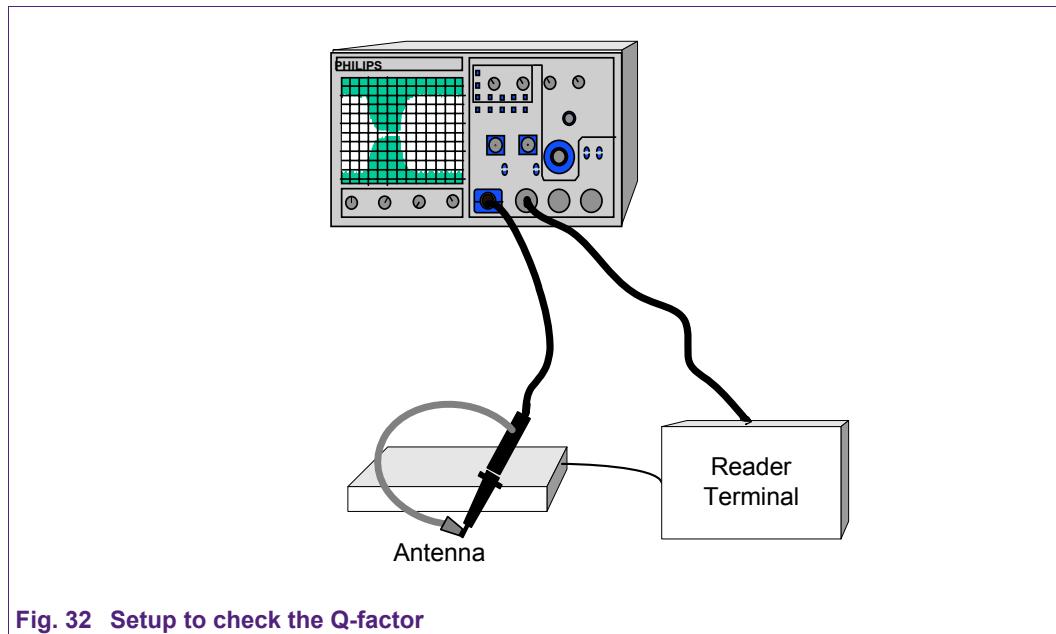


Fig. 32 Setup to check the Q-factor

CH1: Use a loop with the ground line shortcut at the probe to enable inductive signal coupling. Hold the probe loop closely above the antenna.

CH2: Used as trigger if possible

It is recommended to check the pulse shape according to the values given in Fig 40.

The absolute measured voltage in CH1 depends on the coupling (= distance) between the probe loop and the reader antenna.

The influence of the coupling on the shape can be neglected.

The complete antenna tuning and Q-checking is done without any card.

8.4 Pulse shape according to ISO 18092

8.4.1 Bit rate 106 kbps

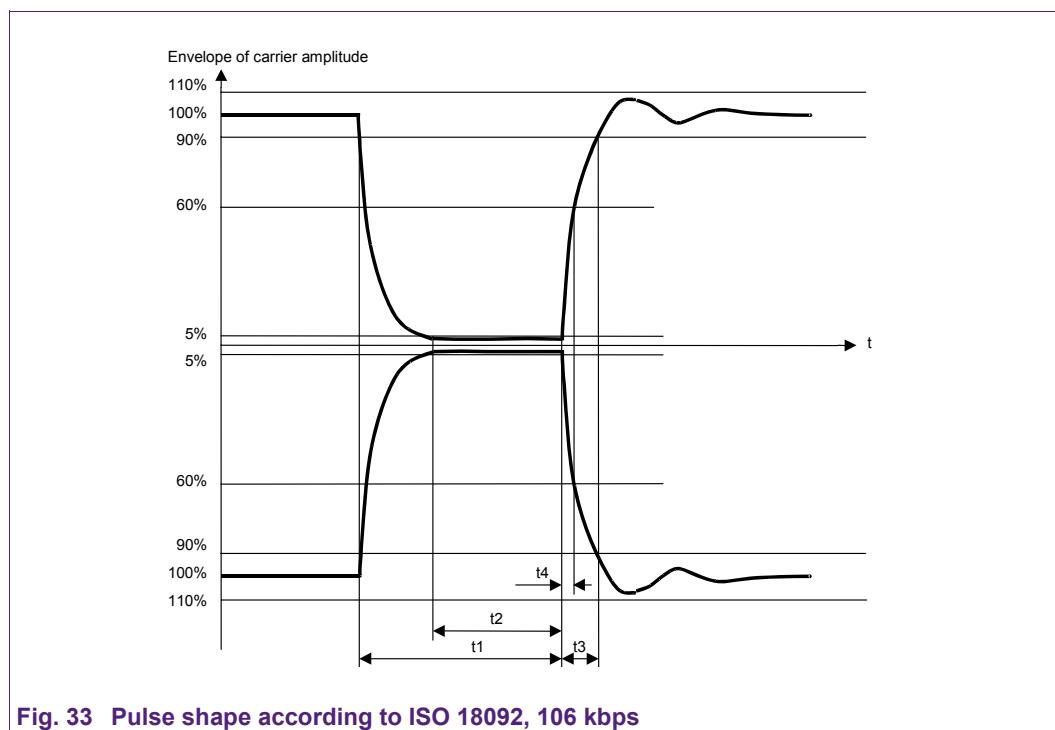


Fig. 33 Pulse shape according to ISO 18092, 106 kbps

The time t_1-t_2 describes the time span, in which the signal falls from 90% down below 5% of the signal amplitude. As the pulse length of PN544 is accurate enough, only the time t_2 has to be checked: the signal has to remain below 5% for the time t_2 .

The most critical time concerning rising carrier envelope is t_4 . It must be checked that the carrier envelope at the end of the pause reaches 60% of the continuous wave amplitude within $0.4\mu\text{s}$.

Pulse shape definitions according to ISO18092, 106 kbps

Pulse length (Condition)	t_1 [μs]	t_2 [μs]	t_3 [μs]	t_4 [μs]
Maximum	3,0	t_1	1,5	0,4
Minimum	2,0	0,7	0,5	0,0

8.4.2 Bit rate 212 kbps and 424 kbps

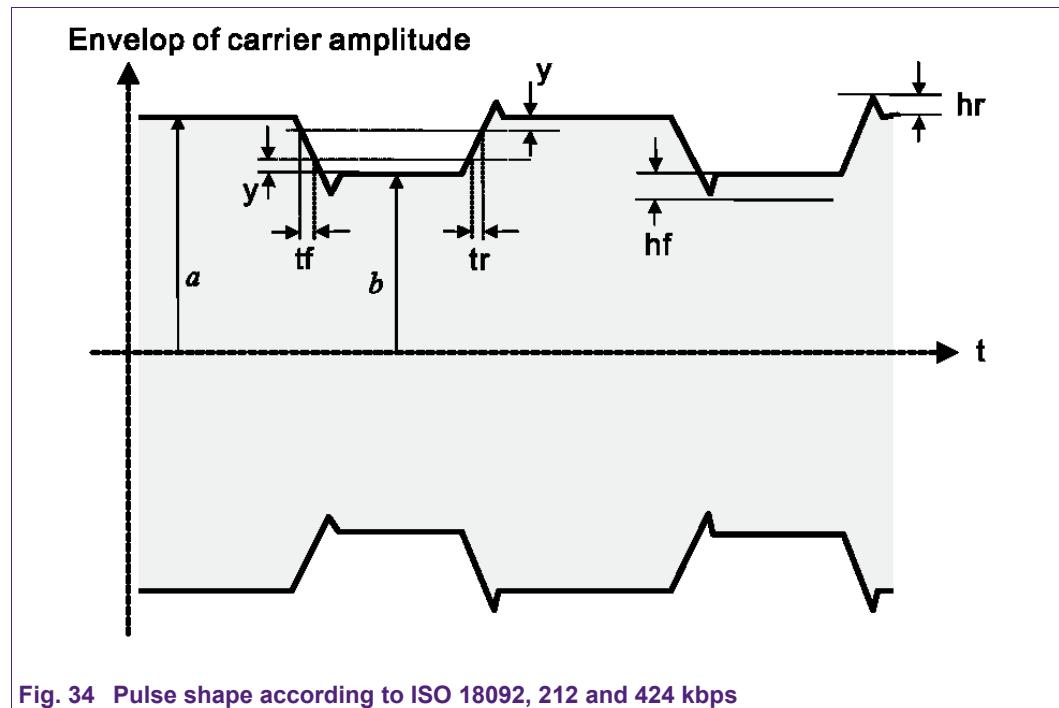


Table 8-1: Pulse shape definitions according to ISO18092, 212 and 424 kbps

	212 kbps	424 kbps
tf	2,0 μ s max	1,0 μ s max
tr	2,0 μ s max	1,0 μ s max
y	0,1 (a-b)	0,1 (a-b)
hf, hr	0,1 (a-b) max	0,1 (a-b) max

9. Appendix B

9.1 How to measure card mode resonance frequency

The card-mode resonance frequency and quality factor depends on the H-field strength. As a matter of fact, the chip input resistance and capacitance have a dependency on the antenna voltage. It is recommended to measure the resonance frequency of the DUT in an unloaded condition, keeping the applied field strength very low, so that the chip can not power up. Below an antenna voltage of $\sim 0.3\text{Vpp}$ the chip input impedance stays constant over a wide range and the Q-factor has the highest value allowing accurate resonance frequency measurements.

Basically, the resonance frequency is measured contact less on an impedance analyzer with a pickup coil defined in the ISO10373-6. A non-conductive distance holder of 1cm thickness shall be put in-between DUT and pickup coil.

9.2 Calibration and measurement procedure

The following steps guide through the configuration and calibration setup for the Agilent 4395A:

1. Switch on Agilent 4395A and configure as Impedance Analyzer
2. Choose frequency range from 10MHz to 20MHz
 - a. Start \rightarrow 10MHz
 - b. Stop \rightarrow 20MHz
 - c. Number of points \rightarrow 801
3. Calibrate the instrument
 - a. Cal \rightarrow Cal Kit \rightarrow 3.5mm \rightarrow Return
 - b. Cal \rightarrow Calibrate Menu
 - c. Connect the calibration kit and calibrate to Open, Short and Load \rightarrow Done
 - d. Connect the calibration kit with the 50Ohm Load and check the calibration
 - e. Scale Ref \rightarrow Autoscale
 - f. *A horizontal run of the curve should be seen now, otherwise repeat the calibration procedure*
4. Fixture compensation
 - a. Cal \rightarrow Fixture Compen \rightarrow Compen Menu
 - b. *Connect pickup coil*
 - c. \rightarrow Short
 - d. *Control the horizontal run of the curve again*
5. \rightarrow Source \rightarrow Power \rightarrow -10dbm
6. *Place DUT on top of pickup coil, search for maximum peak and read resonance frequency*

10. Abbreviations

EMC	Electromagnetic compatibility
R/W	Reader/Writer
RX	Receiver
PCB	Printed Circuit Board
R_{match}	Transmitter matching resistance
TX	Transmitter
Z_{match}	Transmitter matching impedance

11. Legal information

11.1 Disclaimers

General — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in medical, military, aircraft, space or life support equipment, nor in applications where failure or malfunction of a NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of

NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is for the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

11.2 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

MIFARE ® — is a trademark of NXP B.V.

12. Contents

1. INTRODUCTION	3
1.1 PURPOSE AND SCOPE.....	3
2. PN544 TOPOLOGY.....	4
3. TUNING PROCEDURE	6
4. STEP 1 – ANTENNA MATCHING.....	8
4.1 EQUIVALENT CIRCUIT.....	9
4.1.1 Determination of series equivalent circuit	9
4.1.2 Calculation of damping resistor RQ.....	9
4.1.3 Determination of parallel equivalent circuit	
10	
4.2 EMC FILTER DESIGN	10
4.2.1 Capacitive tuning of antenna.....	13
4.3 MATCHING CIRCUIT DESIGN.....	13
4.3.1 Component calculation.....	13
4.4 TUNING PROCEDURE	14
4.4.1 Transmitter matching resistance R_{match} ..	15
4.5 IMPACT OF THE TUNING CAPACITORS VISUALIZED ON	
SMITH CHART	16
4.5.1 EMC capacitance C0	16
4.5.2 Series capacitance C1	17
4.5.3 Parallel matching capacitance C2	18
4.6 RECEIVER CIRCUIT DESIGN.....	19
4.7 EXAMPLE	20
5. STEP 2 – CONNECTING ANT1 AND ANT2 PINS	22
6. STEP 3 – READER/WRITER FINE-TUNING	23
7. STEP 4 – CARD MODE TUNING.....	25
8. APPENDIX	27
8.1 ANTENNA DESIGN	27
8.1.1 Antenna inductance	27
8.1.2 Circular antennas.....	27
8.1.3 Rectangular antennas.....	28
8.1.4 Number of turns	29
8.1.5 Antenna symmetry.....	29
8.1.6 Ferrite shielding	30
8.1.7 Antenna quality factor	32
8.2 EQUIVALENT CIRCUIT MEASUREMENT	34
8.2.1 Impedance analyzer with equivalent circuit	
calculation.....	34
8.2.2 Network analyzer	34
8.2.3 Series equivalent circuit.....	35
8.3 PULSE SHAPE CHECK	36
8.4 PULSE SHAPE ACCORDING TO ISO 18092	38
8.4.1 Bit rate 106kbps.....	38
8.4.2 Bit rate 212 kbps and 424 kbps	39
9. APPENDIX B	40
9.1 HOW TO MEASURE RESONANCE FREQUENCY	40
9.2 CALIBRATION AND MEASUREMENT PROCEDURE	40
10. ABBREVIATIONS	41
11. LEGAL INFORMATION	42
11.1 DISCLAIMERS	42
11.2 TRADEMARKS.....	42
12. CONTENTS	43

射 频 和 天 线 设 计 培 训 课 程 推 荐

易迪拓培训(www.edatop.com)由数名来自于研发第一线的资深工程师发起成立，致力并专注于微波、射频、天线设计研发人才的培养；我们于 2006 年整合合并微波 EDA 网(www.mweda.com)，现已发展成为国内最大的微波射频和天线设计人才培养基地，成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程，广受客户好评；并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书，帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司，以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表：<http://www.edatop.com/peixun/rfe/129.html>




射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材；旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习，能够让学员完全达到和胜任一个合格的射频工程师的要求…

课程网址：<http://www.edatop.com/peixun/rfe/110.html>

ADS 学习培训课程套装

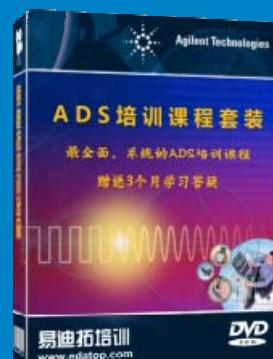该套装是迄今国内最全面、最权威的 ADS 培训教程，共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解，并多结合设计实例，由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS，迅速提升个人技术能力，把 ADS 真正应用到实际研发工作中去，成为 ADS 设计专家…



课程网址：<http://www.edatop.com/peixun/ads/13.html>



HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程，是迄今国内最全面、最专业的 HFSS 培训教程套装，可以帮助您从零开始，全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装，更可超值赠送 3 个月免费学习答疑，随时解答您学习过程中遇到的棘手问题，让您的 HFSS 学习更加轻松顺畅…

课程网址：<http://www.edatop.com/peixun/hfss/11.html>

CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出, 是最全面、系统、专业的 CST 微波工作室培训课程套装, 所有课程都由经验丰富的专家授课, 视频教学, 可以帮助您从零开始, 全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装, 还可超值赠送 3 个月免费学习答疑…



课程网址: <http://www.edatop.com/peixun/cst/24.html>



HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书, 课程从基础讲起, 内容由浅入深, 理论介绍和实际操作讲解相结合, 全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程, 可以帮助您快速学习掌握如何使用 HFSS 设计天线, 让天线设计不再难…

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程, 培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合, 全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作, 同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习, 可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试…



详情浏览: <http://www.edatop.com/peixun/antenna/116.html>

我们的课程优势:

- ※ 成立于 2004 年, 10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养, 更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授, 结合实际工程案例, 直观、实用、易学

联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>